

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, Dec.2018/Jan.2019
Logic Design

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting
atleast TWO questions from each part.**

PART – A

- 1
 - a. Express the given expression in standard SOP form; $f[A,B,C] = AC + AB + BC$. (03 Marks)
 - b. Express the given expression in standard POS form; $f[A,B,C] = (A + B)(B + \bar{C})(A + C)$. (03 Marks)
 - c. A combinational logic circuit has 3 inputs, the output will be low only when majority of inputs are high ;
 - i) Derive truth table
 - ii) Write the POS expression
 - iii) Convert the POS equation to SOP form
 - iv) Simplify the expression using k-map and implement it using only NAND gates. (14 Marks)
- 2
 - a. Design an odd parity bit generator using gates for the decimal digits 0 to 9 represented in 8421 BCD. Give the necessary truth table and the logic diagram with the explanation. (10 Marks)
 - b. Simply the following 5 variable Boolean function using Quine –McCluskey method :
 $f = \Sigma m(0, 1, 9, 15, 24, 29, 30) + d(8, 11, 31)$. (10 Marks)
- 3
 - a. Describe a 4-bit priority encoder with the help of truth table and k-map simplification for outputs, draw the logic circuit. (10 Marks)
 - b. Implement the following two output function using 74LS138 and external gates
 $F_1(A,B,C) = \Sigma m(1,2,6,7)$
 $F_2(A,B,C) = \pi M(1,3,6,7)$. (04 Marks)
 - c. Design a keypad interface to a digital system using ten line BCD encoder 74LS147. (06 Marks)
- 4
 - a. Implement the following Boolean function using 8 : 1 multiplexer
 $F(A,B,C,D) = \Sigma m(0, 1, 3, 4, 8, 9, 15)$. (06 Marks)
 - b. State the applications of multiplexers. (04 Marks)
 - c. Design a full adder with the help of truth table and implement it with basic gates. (10 Marks)

PART – B

- 5
 - a. Distinguish between combinational circuit and sequential circuits with an example to each. (04 Marks)
 - b. Explain the operation of master-slave J-K flip-flop with NAND gate circuit and input output waveforms. (10 Marks)
 - c. Explain the working of switch debouncers using S-R latch. (06 Marks)
- 6
 - a. Describe the different modes of operation of shift registers. (04 Marks)
 - b. What are the applications of shift register? (04 Marks)
 - c. Describe a 4-bit synchronous binary counter with a block diagram and timing diagram. (12 Marks)

- 7 a. Describe a Moore model with an example. (06 Marks)
 b. Design a synchronous mod-6 counter using JK flip-flop with the excitation table and k-map simplification, determine the transition table. (14 Marks)
- 8 a. A sequential circuit has one input and one output. The state diagram is shown in Fig.Q8(a). Design a sequential circuit with D-flip-flop. (12 Marks)

 


Fig.Q8(a)

- b. State the steps for the design of a clocked synchronous sequential circuit. (08 Marks)
