

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, January 2013

Logic Design

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART – A

- 1 a. Design a minimum two level gate combinational network that detects the presence of six illegal code group (decimal 10 to 15) in a 4 bit that represent BCD code by providing a logic 0 and lighting a red LED. (08 Marks)
- b. Simplify the following expressions using Karnaugh map. Implement the simplified circuit using the gates as indicated.
 - i) $f(w, x, y, z) = \sum m(1, 5, 7, 9, 10, 13, 15) + d(8, 11, 14)$ using NAND gates.
 - ii) $f(A, B, C, D) = \pi m(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$ using NOR gates. (12 Marks)
- 2 a. Simplify using Quine McCluskey minimization technique
 $Y(A, B, C, D) = \sum m(0, 1, 2, 3, 6, 7, 8, 9, 14, 15)$ (12 Marks)
- b. Simplify the following Boolean function using variable entered map technique of taking z as the map entered variable:
 $f(w, x, y, z) = \sum m(3, 5, 6, 7, 8, 9, 10) + dc(4, 11, 12, 14, 15)$ (08 Marks)
- 3 a. Design a 4 to 16 decoder using 2 to 4 decoders with active low enable and active low outputs. (08 Marks)
- b. Design a keypad interface to a digital system using ten line to four line encoder. (06 Marks)
- c. Design a binary full subtractor using basic gates. (06 Marks)
- 4 a. Implement the expression $s = ad + b\bar{c} + bd$ using 4:1 mux. Choose b and d as select lines. (10 Marks)
- b. Design a combinational circuit that accepts two unsigned 2-bit binary number and provides 3 outputs.
 Input : word A = A_1A_0 word B = B_1B_0
 Output : A = B, A > B, A < B. (10 Marks)

PART – B

- 5 a. Explain the working of Master-Slave JK flip-flop with functional table and timing diagram. Show how race around condition is overcome. (08 Marks)
- b. Explain switch debouncing and its elimination using SR latch. (06 Marks)
- c. Obtain characteristic equations of JK and SR flip-flops. (06 Marks)
- 6 a. Explain the operation of Ring counter and twisted ring counter using shift register with the help of diagram. (08 Marks)
- b. Design a synchronous mod 6 counter using clocked JK flip-flop. (sequence 0, 2, 3, 6, 5, 1, 0) (12 Marks)

- 7 a. With block diagram, write the two distinct models used in designing synchronous sequential logic circuit. (06 Marks)
- b. Give output function, excitation table, transition table, state table and state diagram by analyzing the sequential circuit shown in Fig.Q7(b). (14 Marks)

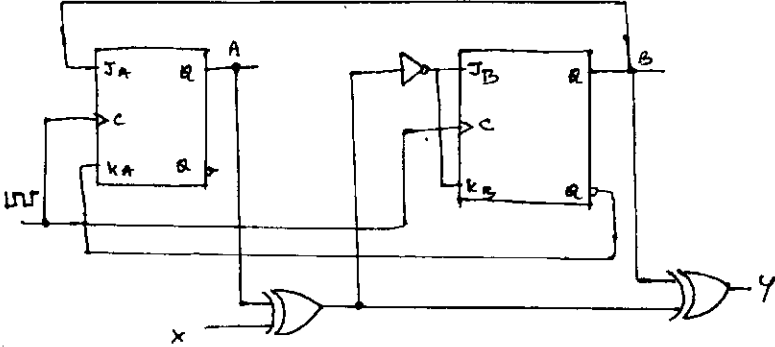


Fig.Q7(b)

- 8 a. Construct a mealy state diagram that will detect a serial sequence of 10110 when the input polttron has been detected cause an output z to be asserted high. (08 Marks)
- b. Design a clocked sequential circuit that operates according to the state diagram shown IN Fig.Q8(b). Implement the circuit using T flip-flop. (12 Marks)

 


Fig.Q8(b)
