

Third Semester B.E. Degree Examination, Jan./Feb. 2021

Logic Design

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, selecting atleast TWO questions from each part.


PART - A

- 1 a. Using K – map technique, simplify the following and implement using gates :
 - i) $f(a b c d) = \Sigma m(1, 3, 7, 11, 15) + \Sigma d(0, 2, 4)$.
 - ii) $f(a b c d) = \Pi m(0, 3, 4, 7, 8, 10, 12, 14) + d(2, 6)$. (10 Marks)
- b. The input to a control circuit is a 4 – bit binary number $x_3 x_2 x_1 x_0$. Design a logic circuit with minimum number of gates if
 - i) Output $y_1 = 1$ if input binary number is ≤ 5 .
 - ii) Output $y_2 = 1$ if input binary number is ≥ 9 . (10 Marks)
- 2 a. Using Quine – Mc Cluskey method, simplify :
 $f(a b c d) = \Sigma m(0, 1, 3, 7, 8, 9, 11, 15)$ and determine essential prime implicants. (10 Marks)
- b. What are the advantages of Map – Entered Variable (MEV) method? Illustrate MEV method for $f = \Sigma m(0, 1, 4, 7)$. Verify your answer using 3 – variable K – map method. (10 Marks)
- 3 a. Explain the General structure of a decoder. Construct 4×16 line decoder using 3×8 decoder. Explain its working. (12 Marks)
- b. Design and implement an octal to binary encoder using minimum number of gates. (08 Marks)
- 4 a. Implement the following function using 4×1 MUX : $f(a, b, c, d) = \Sigma m(0, 1, 2, 4, 6, 9, 12, 14)$. (08 Marks)
- b. Construct 1×8 demultiplexer using 1×4 demultiplexer. (05 Marks)
- c. Design a BCD adder using 4 bit binary adder. Draw the logic circuit. (07 Marks)

PART - B

- 5 a. Compare combinational circuit with sequential circuit. (05 Marks)
- b. Explain the principle of Bistable element. (05 Marks)
- c. Explain the master slave JK flip flop with input and output waveforms. (10 Marks)
- 6 a. What is a Shift Register? Explain the working of the serial – in – serial – out shift register. (10 Marks)
- b. Design a mod – 6 counter using clocked SR flip flop. (10 Marks)
- 7 a. Explain the principle of Moore model and Mealy model. (10 Marks)
- b. Analyse the synchronous sequential circuit shown in fig. Q7(b). (10 Marks)

Fig.Q7(b)

 

- 8 a. Design a synchronous decade counter using T – Flip - Flops. Draw the timing diagram also. (10 Marks)
- b. Design a sequence detector circuit to detect serial input sequence of 101 using Mealy model. (10 Marks)
