



Third Semester B.E. Degree Examination, June/July 2011
Logic Design

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions selecting at least TWO from each Part.

PART A

- 1
 - a. Staircase light is controlled by two switches, one is at the top of the stair and other at the bottom of the stairs
 - i) Make a truth table for this system
 - ii) Write the logic equations in the SOP form
 - iii) Realize the circuit using basic gates
 - iv) Realize the circuit using minimum number of NAND gates. (08 Marks)
 - b. Simplify by using Karnaugh map and realize the circuit using basic gates (08 Marks)
 $f(a, b, c, d) = \pi(2, 3, 4, 6, 7, 10, 11, 12)$
 - c. Show that $ab + ac + a\bar{b}c(ab + c) = 1$ (04 Marks)

- 2
 - a. Simplify using Quine Mecluskey tabulation algorithm and find out the number of prime implicants. (10 Marks)
 $f(a, b, c, d) = \Sigma(2, 3, 4, 5, 13, 15) + d(8, 9, 10, 11)$
 - b. Simplify using MEV technique and implicant using basic gates (10 Marks)
 $Y = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}BC\bar{D} + \bar{A}BCD$

- 3
 - a. With the aid of block diagram clearly distinguish between a decoder and encoder. (05 Marks)
 - b. Design a single decode BCD adder and explain the methodology in detail. (10 Marks)
 - c. Implement a full subtractor using a decoder and two NAND gates. (05 Marks)


- 4
 - a. Implement $f(a, b, c, d) = \Sigma m(10, 1, 5, 6, 7, 9, 10, 15)$ using
 - i) 8 : 1 MUX with a, b, c as select line (08 Marks)
 - ii) 4 : 1 MUX with a, b, as select lines (07 Marks)
 - b. What is comparator? Design a two bit binary comparator. (07 Marks)
 - c. Design a full adder using multiplexer (05 Marks)
 For a full adder
 $S = \Sigma m(1, 2, 4, 7)$
 $C = \Sigma m(7, 5, 6, 7)$

PART B

- 5
 - a. Explain the operation of a simple S-R flip flop using NAND gates. (10 Marks)
 - b. What is sequential circuit? Discuss the different types of sequential circuit. (06 Marks)
 - c. Give the logic diagram
 - i) Master slave J-K flip flop
 - ii) Master slave S-R flip flop (04 Marks)

- 6
 - a. Describe the block diagram of a mod 7 twisted ring counter and explain its operation. Give the count sequence table and the decoding logic used to identify the various states. (10 Marks)
 - b. Design a mod-5 synchronous binary counter using clocked J-K flip flops. (10 Marks)

 - 7 a. Construct the excitation table, transition table and state diagram for the Moore sequential circuit given below (10 Marks)



- b. Compare Moore and Mealy models. (04 Marks)
 c. Explain the Mealy model of a clocked synchronous sequential network. (06 Marks)

- 8 Write short notes on : (20 Marks)
- Working of switch debouncer using SR latch
 - Working of universal shift register
 - Shift registers
 - Race around condition in flip flops.
