

USN

--	--	--	--	--	--	--	--	--	--

10ES33

Third Semester B.E. Degree Examination, June/July 2014
Logic Design

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, selecting
atleast TWO questions from each part.**

PART – A

1.
 - a. $A_8A_4A_2A_1$ is an 8421 BCD input to a logic circuit whose output is a 1 when $A_8 = 0$, $A_4 = 0$ and $A_2 = 1$, or when $A_8 = 0$ and $A_4 = 1$. Design the simplest possible logic circuit. **(08 Marks)**
 - b. Simplify the given function using K-MAP
 $\Sigma m(0, 2, 3, 10, 11, 12, 13, 16, 17, 18, 19, 20, 21, 26, 27)$. **(06 Marks)**
 - c. Design a three-input, one-output minimal two-level gate combinational circuit which has an output equal to 1 when majority of its inputs are at logic 1 and has an output equal to 0 when majority of its inputs are at logic 0. **(06 Marks)**

2.
 - a. Find a minimal sum for the following Boolean function using decimal Quine-Moclusky method and prime implicant table reduction $F = \Sigma(1, 2, 3, 5, 6, 7, 8, 9, 12, 13, 15)$. **(10 Marks)**
 - b. For the given Boolean function, determine a minimal sum using MEV techniques using a, b, c as the map variables $f = \Sigma(3, 4, 5, 6, 7, 8, 9, 12, 13, 15)$. **(05 Marks)**
 - c. Find a minimal sum for the following Boolean function using MEV technique with a, b and c as the map variables $f(\alpha, \beta, a, b, c) = \alpha\bar{a}\bar{b}c + \alpha\bar{a}bc + \alpha a\bar{b}c + \beta a\bar{b}c + \beta a\bar{b}\bar{c} + \bar{a}bc + a\bar{b}\bar{c}$. **(05 Marks)**

3.
 - a. Develop the logic diagram of a 2 to 4 decoder with the following specifications:
i) Active low enable input; ii) Active high encoded outputs. Draw the IEEE symbol. **(06 Marks)**
 - b. Design a combinational circuit to convert BCD to excess – 3. **(08 Marks)**
 - c. Write the condensed truth table for 0, 4, to 2 line priority encoder with a valid output where the highest priority is given to the highest bit position or input with highest index and obtain the minimal sum expressions for the outputs. **(06 Marks)**

4.
 - a. How does the look-ahead carry adder speed up the addition process? **(10 Marks)**
 - b. Implement a 12-bit comparator using IC7485. **(04 Marks)**
 - c. Implement $u = ad + \bar{b}c + bd$, using and 4 – 1 MUX using ab as select inputs. **(06 Marks)**

PART – B

5.
 - a. Explain the working of pulse-triggered JK flip-flop with typical JK flip-flop waveforms. **(08 Marks)**
 - b. Explain switch debouncer using S-R latch with waveforms associated with switch debouncer. **(08 Marks)**
 - c. How do you convert J-K flip-flop to S-R flip-flop? **(04 Marks)**

- 6 a. Explain the working of universal shift register with the help of logic diagram and mode control table. (10 Marks)
- b. Design a synchronous counter to count from 0000 to 1001 using JK flip-flops. (10 Marks)
- 7 a. A sequential circuit has two flip-flop A and B, two inputs x and y, and an output Z. The flip-flop input function and the circuit output functions are as follows:
 $J_A = xB + \overline{yB}$; $K_A = x\overline{yB}$; $J_B = x\overline{A}$; $K_B = x\overline{y} + A$; $Z = xyA + \overline{xy}B$. Obtain the logic diagram, state-table and state equations, also state diagram. (10 Marks)
- b. Realize the system represented by the state diagram shown in Fig.Q.7(a). Using D-flip-flop. (10 Marks)

 


Fig.Q.7(a)

- 8 a. Design and implement a synchronous 3 bit up/down counter using J-K flip flops. (10 Marks)
- b. What do you mean by the Moore model and Melay model of the state diagram? (04 Marks)
- c. Draw the state diagram of a Mealy machine to detect as input sequence 10110 with overlap. An output 1 is to be generated when the sequence is detected. (06 Marks)
