

USN

--	--	--	--	--	--	--	--	--	--

10ES33

Third Semester B.E. Degree Examination, June/July 2017
Logic Design

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting
at least TWO questions from each part.**

PART – A

- 1 a. Define the following (i) POS (ii) Truth table (iii) Karnaugh map. (06 Marks)
b. Find the minimal SOP of,
(i) $f(w, x, y, z) = \sum m(0, 1, 2, 3, 4, 9, 13) + dc(5, 10, 11, 14)$
(ii) $f(w, x, y, z) = \pi M(0, 3, 4, 11, 13) + dc(2, 6, 8, 9, 10)$ (07 Marks)
c. Find the minimal sum and minimal product of,
 $f(a, b, c, d) = \pi M(0, 2, 6, 11, 13, 15) + dc(1, 9, 10, 14)$ (07 Marks)
- 2 a. Obtain SOP using Quine-Mc Clusky method of,
 $f(w, x, y, z) = \sum m(7, 9, 12, 13, 14, 15) + dc(4, 11)$ (12 Marks)
b. Simplify the function using VEM technique by considering a, b and c are map variables,
 $f(a, b, c, d) = \sum m(2, 3, 4, 10, 13, 14, 15) + dc(7, 9, 11)$ (08 Marks)
- 3 a. Using AND decoder realize full adder with its truth table, output function and decoder of suitable type. (06 Marks)
b. Design 8 : 3 higher order priority encoder. Mention its advantage. (08 Marks)
c. Construct 16 : 1 MUX using 4 : 1 MUX. (06 Marks)
- 4 a. Design 2 bit magnitude comparator with its truth table, simplified output equations and logic circuit. (10 Marks)
b. Realize and implement using 8 : 1 MUX where w, x, y appear as S_2, S_1 and S_0 of
 $f(w, x, y, z) = \sum m(0, 4, 6, 8, 9, 11, 13, 14)$ (10 Marks)
Also realize by 4 : 1 MUX where w, x appears as S_1, S_0 .

PART – B

- 5 a. Briefly explain sequential logic circuit. Explain TFF and JK Master Slave FF with their logic symbol, truth table, logic diagram and timing diagram. (10 Marks)
b. Explain race around condition and how it is over come. (04 Marks)
c. Explain the working of a SR latch as a switch debouncer with necessary circuit and timing diagram. (06 Marks)
- 6 a. Derive the characteristics equation of JK-FF and D-FF. (06 Marks)
b. With a neat diagram of 4-bit Universal Shift Register (USB) explain its working with the help of mode table. (08 Marks)
c. Design mod-10 asynchronous counter using clocked T-FFs. (06 Marks)

- 7 a. Explain 4-bit ring counter with a neat diagram. (06 Marks)
 b. Explain the triggering of flipflops and its types. (04 Marks)
 c. Design and implement a synchronous counter for the sequence 2 – 0 – 7 – 4 – 1 using negative edge clocked JK flip flop. (10 Marks)
- 8 a. Bring out the differences between Mealy and Moore machine models. (08 Marks)
 b. Construct the excitation table, transition table, state table and state diagram for Moore circuit shown in Fig. Q8 (b). (12 Marks)

 


Fig. Q8 (b)

* * * * *