

USN

--	--	--	--	--	--	--	--	--	--

10ES33

Third Semester B.E. Degree Examination, June/July 2018
Logic Design

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting
atleast TWO questions from each part.**

PART – A

- 1 a. Reduce the following function using K-Map technique and implement using gates :
 $J = f(A, B, C, D, E) = \sum_m (4, 5, 6, 7, 9, 11, 13, 15, 25, 27, 29, 31)$
 $G = f(A, B, C, D) = \pi M(0, 4, 5, 7, 8, 9, 11, 12, 13, 15).$ (12 Marks)
- b. Fig.Q1(b) shows a BCD counter that produces a 4-bit output representing the BCD code for the number of pulses that have been applied to the counter input. The counter resets to "0000" on the tenth pulse and starts recounting. Design the logic circuit that produces a "High" output whenever the count is 2, 3, or 9. Use K-Mapping and implement the logic circuit using NAND gates. (08 Marks)

 


Fig.Q1(b)

- 2 a. Convert the given Boolean function $f(x, y, z) = [x + \bar{x}\bar{z}(y + \bar{z})]$ into maxterm canonical form and hence highlight the importance of canonical formula. (06 Marks)
- b. Simplify using Quine Mc Cluskey tabulation algorithm.
 $v = f(a, b, c, d) = \sum(2, 3, 4, 5, 13, 15) + \sum d(8, 9, 10, 11).$ (14 Marks)
- 3 a. Implement a full subtractor using decoder and write the truth table. (10 Marks)
- b. What are the problems associated with the basic encoder? Explain how they can be overcome by priority encoder, considering 8 input lines. (10 Marks)
- 4 a. Design a combinational circuit that accepts two unsigned, 2-bit binary number $A = A_1 A_0$ and $B = B_1 B_0$ and provide 3 outputs corresponding to $A = B$, $A > B$ and $A < B$. (08 Marks)
- b. Implement $f(a, b, c, d) = \sum m(0, 1, 5, 6, 7, 9, 10, 15)$ using :
 i) 8 : 1 MUX with a, b, c as select line
 ii) 4 : 1 MUX with a, b as select lines. (08 Marks)
- c. Explain the terms :
 i) Ripple-carry propagation
 ii) Look-ahead carry. (04 Marks)

PART – B

- 5 a. What is a flip-flop? Discuss the working principle of S-R flip-flop with its truth table. Also explain the role of S-R latch in switch debouncer circuit. (08 Marks)
- b. With neat schematic diagram of master slave JK-FF, discuss its operation. Mention the advantages of JK-FF over master slave SR-FF. (12 Marks)

- 6 a. Design a 4-bit universal shift register using positive edge triggered D-flip-flops to operate as shown in table below Table Q6(a). (12 Marks)

Select line		Data line selected	Register Operation
S ₁	S ₀		
0	0	I ₀	Hold
0	1	I ₁	Shift right
1	0	I ₂	Shift left
1	1	I ₃	Parallel load

Table Q6(a)

- b. Explain the working of a 4-bit asynchronous DeCade counter using JKFF in toggle mode. (08 Marks)

- 7 a. Explain mealy and Moore sequential circuit models. (04 Marks)

- b. For the state machine M₁ shown in Fig.Q7(b) obtain,
 i) State table
 ii) Transition table
 iii) Excitation table for T flip-flop
 iv) Logic circuit for T excitation realization. (16 Marks)

 


Fig.Q7(b)

- 8 a. Construct Moore and Mealy state diagram that will detect input sequence 10110, when input pattern is detected Z is asserted high. Give state algorithms for each state. (10 Marks)
 b. Design a cyclic Mod6, synchronous binary counter using J-K flip-flop. Give the state diagram, transition table and excitation table. (10 Marks)
