

USN

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

10ES33

Third Semester B.E. Degree Examination, June/July 2015
Logic Design

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, selecting
atleast TWO questions from each part.**

PART – A

- 1 a. Express the following Boolean function in canonical min term form :

$$F(A, B, C) = \overline{A} \overline{B} + C. \quad (04 \text{ Marks})$$
- b. Express the following Boolean function in canonical max term form :

$$F(A, B, C, D) = \overline{A} B + C \overline{D}. \quad (08 \text{ Marks})$$
- c. Simplify the following Boolean function using four variable 'k' map. Realize the simplified expression using NAND gates.

$$F(A, B, C, D) = \sum m(1, 5, 6, 7, 11, 12, 13, 15). \quad (08 \text{ Marks})$$

- 2 a. Simplify the following Boolean function using Quine -- Moclusky's minimization technique.

$$F(A, B, C, D) = \sum m(6, 7, 9, 10, 13) + d(1, 4, 5, 11, 15). \quad (10 \text{ Marks})$$
- b. Consider the following Boolean equation :

$$F(A, B, C, D) = \sum m(1, 3, 7, 11, 15) + \sum d(0, 2, 5).$$
 Simplify the function F using a 3 variable MEV k – map. Assign the variable D to be the MEV. (10 Marks)

- 3 a. Implement the Boolean functions :

$$F_1(x, y, z) = X \overline{Y} + YZ$$

$$F_2(x, y, z) = \sum m(0, 3, 5)$$
 Using a 3 – 8 line decoder IC 74138 with active low outputs. (08 Marks)
- b. Interface a 10 key keypad to a digital system using a IC 74147 which is a 10 line to BCD priority encoder. Draw the logic diagram and explain the operation with the truth table. (12 Marks)

- 4 a. Implement the Boolean function :

$$F(A, B, C, D) = \sum m(0, 1, 2, 4, 5, 7, 8, 9)$$
 Using a 8 to 1 multiplexer. Draw the logic diagram and explain the operation. Additional gates can be used if required. (08 Marks)
- b. Explain the operation of a full subtractor with the help of a truth table and Boolean expressions for the outputs. Implement the full subtractor using two numbers of
 - i) 4 to 1 multiplexers
 - ii) 2 to 1 multiplexers.
 Additional gates if required can be used. (08 Marks)
- c. Design a one bit binary comparator. (04 Marks)

PART - B

- 5 a. Explain the operation of a gated SR latch with a logic diagram and a truth table. (06 Marks)
 b. Explain the operation of a positive edge triggered 'D' flip-flop with the help of a logic diagram and truth table. Also draw the relevant waveforms. (04 Marks)
 c. Draw the output waveforms Q_M and Q_S the outputs of the master and the slave respectively, if the inputs to a master slave JK flip-flop one as indicated below. (10 Marks)

 


Fig. Q5(c)

- 6 a. Design a 4 bit binary ripple up counter using negative edge triggered JK flip-flops. Draw the timing diagram with respect to the input clock pulses. Explain the operation. (10 Marks)
 b. Design a synchronous counter using clocked JK flip-flop for the counting sequence shown below :

| Q_2 | Q_1 | Q_0 |
|-------|-------|-------|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 0 | 1 | 1 |
| 1 | 1 | 0 |
| 1 | 0 | 1 |
| 0 | 0 | 1 |
| 0 | 0 | 0 |

(10 Marks)

- 7 a. Explain mealy and Moore models of a clocked synchronous sequential circuit. (08 Marks)
 b. Design a synchronous circuit using positive edge triggered JK flip-flops to generate the following sequence :

0 - 1 - 2 - 0 is input $x = 0$ and

0 - 2 - 1 - 0 is input $x = 1$

Provide an output which goes high to indicate the non - zero states in the 0 - 1 - 2 - 0 sequence. (12 Marks)

- 8 Construct the excitation table, transition table, state table and state diagram for the sequential circuit shown in Fig. Q8. (20 Marks)

 


Fig. Q8
