

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, December 2010 Network Analysis

Time: 3 hrs.

Max. Marks:100

- Note: 1. Answer any FIVE full questions, selecting at least TWO questions from each part.
2. Standard notations are used.
3. Missing data may be suitably assumed.**

PART – A

- 1 a. Use the node analysis and find the value of V_x in the circuit shown in Fig.Q1(a), such that the current through the impedance $(2 + j3)\Omega$ is zero. (10 Marks)

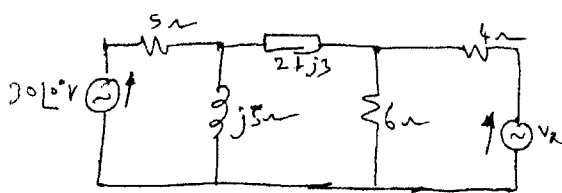


Fig.Q1(a)


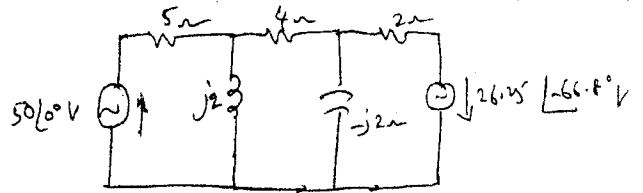


Fig.Q1(b)

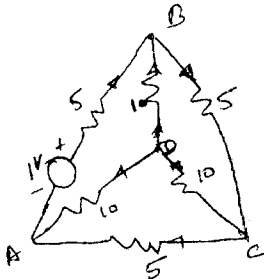- b. Find the current through the 4Ω resistor, using the loop current method, in the circuit shown in Fig.Q1(b). (10 Marks)

- 2 a. Explain the following terms with reference to network topology :
 i) Tree ii) Branch iii) Cut set matrix iv) Tie set matrix (08 Marks)
 b. For the given resistance network, write a tie set schedule and obtain equilibrium equations on current basis. Calculate the values of branch voltages. Assume inner branches as tree branches. [Refer Fig.Q2(b)] (12 Marks)



All resistances in ohms
Fig.Q2(b)

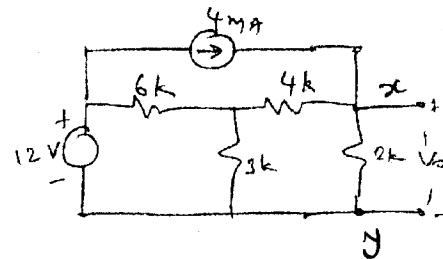


Fig.Q3(b)

- 3 a. State and explain the Thevenin's theorem. (06 Marks)
 b. Obtain the Thevenin's equivalent of the network shown in Fig.Q3(b) between the terminals x and y. Also find V_0 . (06 Marks)
 c. Using Worton's theorem, find the current through the load impedance Z_l in Fig.Q3(c). (08 Marks)

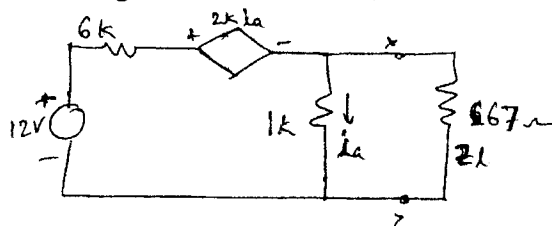


Fig.Q3(c)

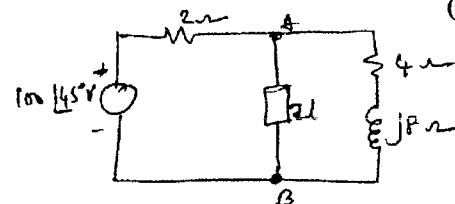


Fig.Q4(b)



- 4 a. Derive the condition or maximum power transfer across a load from a source as applied to a simple A.C. circuit. Assume a suitable circuit for your mathematical derivation. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.



- 4 b. Find the load impedance to be connected across the terminals AB for the maximum power transfer. The network is shown in Fig.Q4(b). Also find the maximum power delivered to the load. (06 Marks)
- c. Write a note on superposition theorem as applied to a dc circuit. (06 Marks)

PART – B

- 5 a. Show that a two branch parallel resonant circuit is resonant at all the frequency, if $R_L = R_C = \sqrt{\frac{L}{C}}$ where R_L = resistance in the inductor branch, R_C = capacitor in the capacitor branch. (08 Marks)
- b. Derive for a resonant circuit, the resonant frequency $f_0 = \sqrt{f_1 f_2}$, where, f_1 and f_2 are the two half power frequencies. (08 Marks)
- c. An RLC series circuit has $R = 1 \text{ K}\Omega$, $L = 100 \text{ mH}$, $C = 10\mu\text{F}$. If a voltage of 100 V is applied across series combination, determine :
 i) Resonant frequency ii) Q-factor and iii) Half power frequencies. (04 Marks)
- 6 a. What is the significance of initial conditions? Write a note on initial conditions in basic circuit elements. (04 Marks)
- b. How is time constant of an RL circuit is defined? Explain its importance in transient analysis, with a suitable example. (08 Marks)
- c. In the circuit shown in Fig.Q6(c), the switch K is changed from position 1 to position 2 at $t = 0$, the steady state having been reached before switching. Find the values of i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0$. (08 Marks)

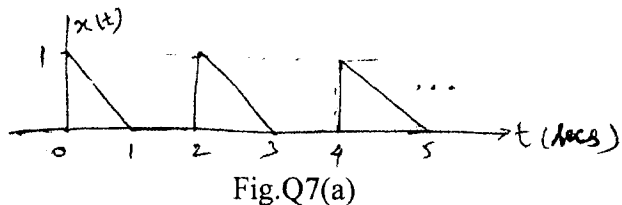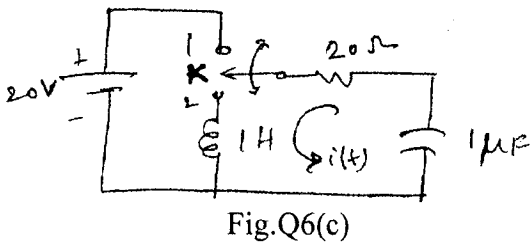

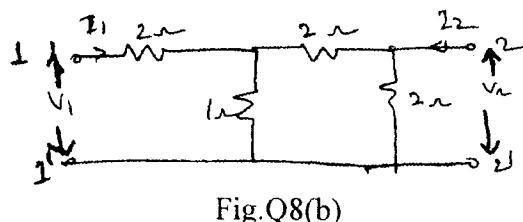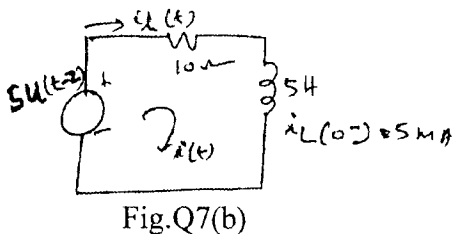- 7 a. Find the Laplace transform of the periodic signal $x(t)$ shown in Fig.Q7(a). (06 Marks)
- b. Determine the response current $i(t)$ in the circuit shown in Fig.Q7(b) using Laplace transform. (06 Marks)



- c. Find the convolution of $h(t) = t$ and $f(t) = e^{-at}$ for $t > 0$, using Laplace transform techniques. (08 Marks)
- 8 a. Obtain the relationship between 'h' and 'y' parameters of a two port network. (10 Marks)
- b. Determine the z parameters for the circuit shown in Fig.Q8(b). (06 Marks)
- c. Write a note on ABCD parameters. (04 Marks)
