

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, December 2011 Network Analysis

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting atleast TWO questions from each part.

PART – A

- 1 a. For the network shown in Fig. Q1(a), determine the voltage 'V' using source shift and /or source transformation techniques only. (06 Marks)

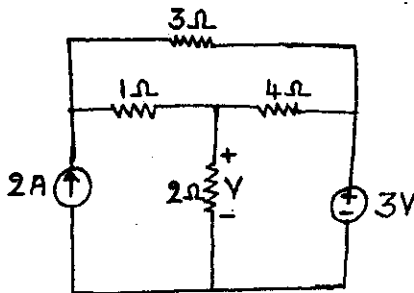


Fig. Q1(a)

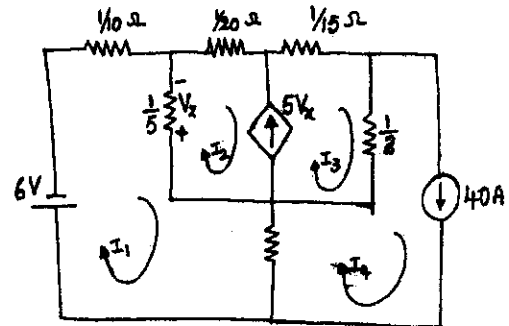


Fig. Q1(b)

- b. Find I_1, I_2, I_3 and I_4 using mesh analysis in the network shown in Fig. Q1(b). (07 Marks)
 c. Find the voltages at nodes 1, 2, 3 for the network shown in Fig. 1(c), using nodal analysis. (07 Marks)

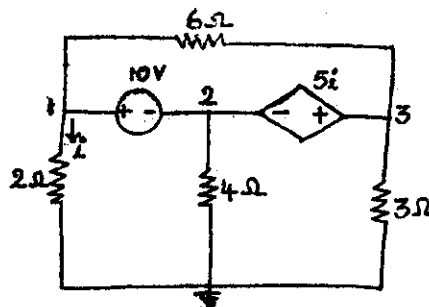


Fig. Q1(c)

- 2 a. Define with examples :
 i) Oriented graph ii) Tree iii) Fundamental cut – set iv) Fundamental tie – set. (06 Marks)
 b. For the network shown in Fig. Q2(b), write the graph of the network and obtain the tie – set schedule considering J_1, J_2, J_5 as tree branches. Calculate all the branch currents. (07 Marks)

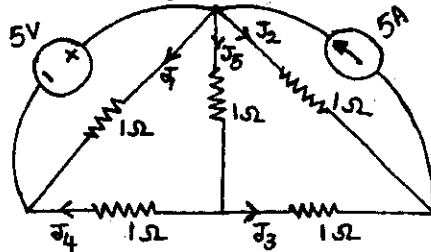


Fig. Q2(b)

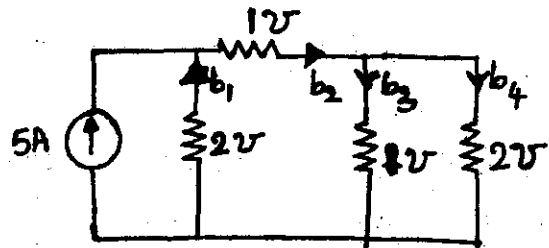


Fig. Q2(c)

- c. For the network given in Fig. Q2(c), write the f – cutest matrix considering branches b_1 and b_3 as tree branches and hence, obtain the equilibrium equation on node basis and calculate the node voltages. (07 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- 3 a. State and prove the reciprocity theorem. (06 Marks)
 b. Using the superposition theorem, obtain the response I for the network shown in Fig. 3(b). (07 Marks)

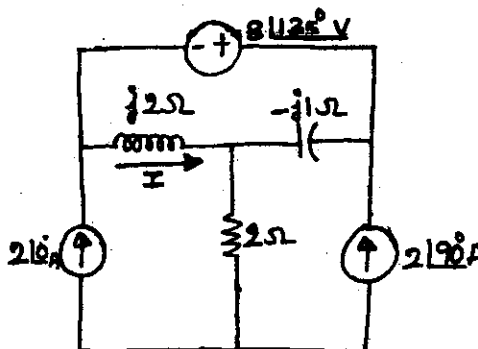


Fig. Q3(b)

- c. Find the Thevenin's equivalent circuit across A, B using Millman's theorem and find the current through the load $(5 + j5) \Omega$, shown in Fig. 3(c). (07 Marks)

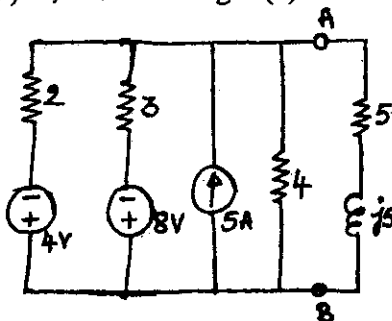


Fig. Q3(c)

- 4 a. State and prove Thevenin's theorem. (06 Marks)
 b. Find the Thevenin's equivalent of the network shown in Fig. Q4(b). (07 Marks)

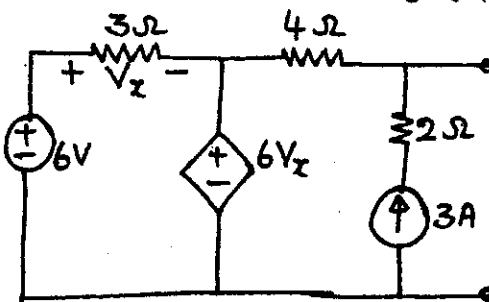


Fig. Q4(b)

- c. What will be the value of R_L to get maximum power delivered to it? What is the value of this power? Refer the network shown in Fig. Q4(c). (07 Marks)

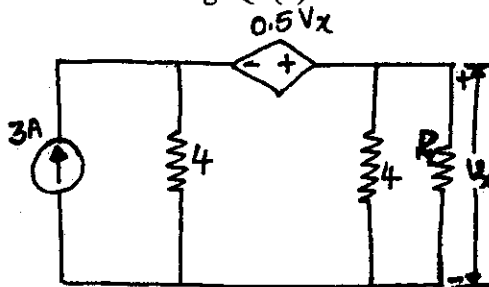


Fig. Q4(c)

PART - B

- 5 a. A series resonant circuit includes $1\mu\text{F}$ capacitor and a resistance of 16Ω . If the BW is 500 rad/sec , determine : i) W_r ii) Q iii) L . (06 Marks)
- b. Derive the expression for parallel resonance circuit, containing resistance in both the branches. Also show that the circuit will resonate at all frequencies if $R_L = R_C = \sqrt{\frac{L}{C}}$. (10 Marks)
- c. Give the comparison between the series resonance and parallel resonance. (04 Marks)
- 6 a. In the network shown in Fig. Q6(a), the switch is moved from position '1' to position 2 at $t = 0$, the steady - state having reached before switching. Calculate i , $\frac{di}{dt}$, and $\frac{d^2i}{dt^2}$ all at $t = 0^+$. (10 Marks)
- b. In the network shown in Fig. 6(b), a steady state is reached with the switch K open. At $t = 0$, the switch K is closed. Obtain the initial values of
i) i ii) i_2 iii) v_c iv) $\frac{di_1}{dt}$ v) $\frac{di_2}{dt}$ and $\frac{di_1}{dt}$ at $t = \infty$. (10 Marks)

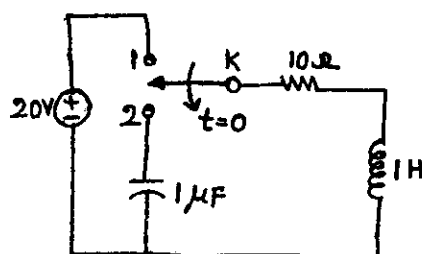


Fig. Q6(a)

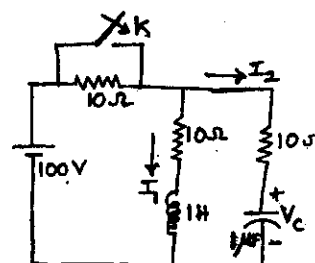


Fig. Q6(b)

- 7 a. In the circuit of Fig. Q7(a), the source voltage is $v(t) = 50 \sin 250 t$. Using Laplace transforms, determine the current, when switch K is closed at $t = 0$. (10 Marks)
- b. In the network shown in Fig. 7(b), the switch K is closed and the steady state is reached. At $t = 0$, the switch is opened. Find the expression for the current in the inductor using Laplace transform. (10 Marks)

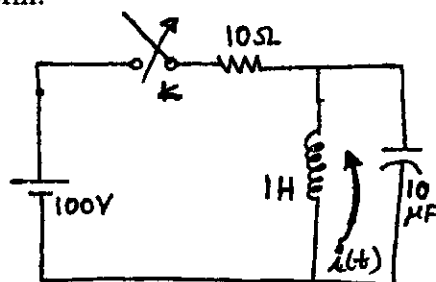


Fig. Q7(a)

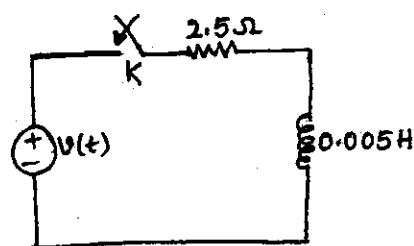


Fig. Q7(b)

- 8 a. Derive Y - parameters and transmission parameters in terms of Z - parameters. (10 Marks)
- b. Find the transmission parameters for the given R - C network shown in Fig. 8(b). (10 Marks)

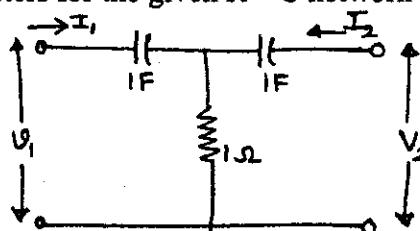


Fig. Q8(b)
