

--	--	--	--	--	--	--	--	--	--

**Third Semester B.E. Degree Examination, December 2012**

**Network Analysis**

Time: 3 hrs.


Max. Marks:100

**Note: Answer FIVE full questions, selecting at least TWO questions from each part.**

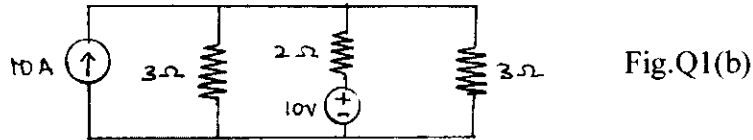
**PART – A**

- 1 a. Define and distinguish the following network elements:
  - i) Linear and non-linear
  - ii) Active and passive
  - iii) Lumped and distributed
  - iv) Ideal and practical current sources

(08 Marks)
- b. Write the mesh equation for the circuit shown in Fig.Q1(b) and determine mesh currents using mesh account analysis. (06 Marks)





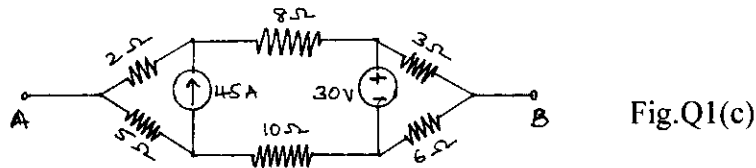- c. Reduce the network shown in Fig.Q1(c) to a single voltage source in series with a resistance using source shift and source transformations. (06 Marks)




- 2 a. Define the following terms with reference to network topology. Give examples.
  - i) Tree
  - ii) Graph
  - iii) Sub-graph
  - iv) Tie-set
  - v) Cut-set

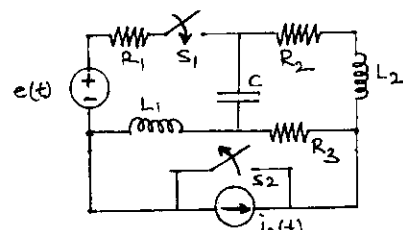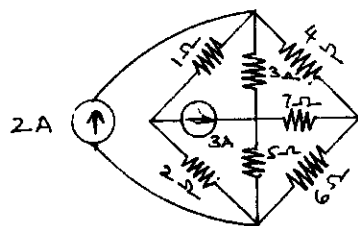(10 Marks)
- b. Construct a tree for the network shown in Fig.Q2(b) so that all loop currents pass through 7Ω. Write the corresponding the set matrix. (06 Marks)



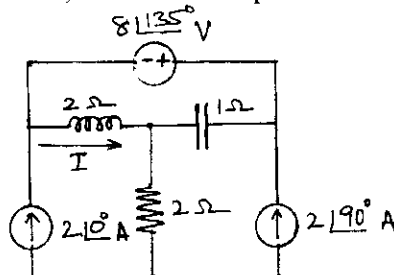- c. What are dual networks? Draw the dual of the circuit shown in Fig.Q2(c). (04 Marks)

- 3 a. Using superposition theorem, obtain the response I for the network shown in Fig.Q3(a).



(08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- 3 b. Verify reciprocity theorem for the circuit shown in Fig.Q3(b).

(06 Marks)

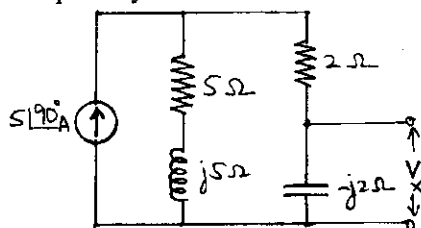


Fig.Q3(b)

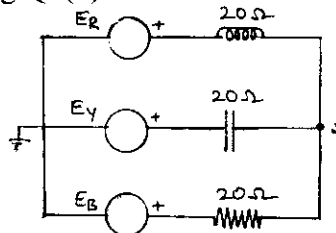


Fig.Q3(c)

- c. Use Millman's theorem to determine the voltage  $V_S$  of the network shown in Fig.Q3(c), given that  $E_R = 230 \angle 0^\circ$  V ;  $E_Y = 230 \angle -120^\circ$  V and  $E_B = 230 \angle 120^\circ$  V .

(06 Marks)

- 4 a. For the network shown in Fig.Q4(a), obtain the Thevenin's equivalent as seen from the terminals p and q.

(08 Marks)

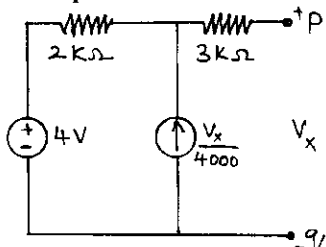


Fig.Q4(a)

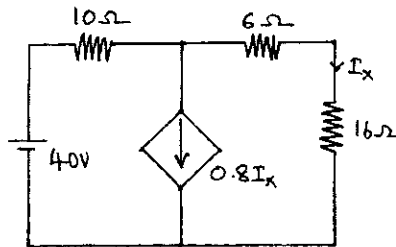


Fig.Q4(b)

- b. State Norton's theorem and find the current through 16Ω resistor using Norton's theorem in Fig.Q4(b).
- c. For the network shown in Fig.Q4(c), determine the impedance  $Z_X$  such that maximum power is transferred from the source to the load of impedance  $Z_X$ .

(06 Marks)

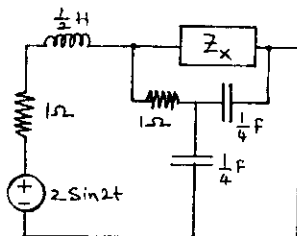


Fig.Q4(c)

(06 Marks)

**PART - B**

- 5 a. Define the following terms with reference to resonant circuit:  
 i) Resonance    ii) Q-factor    iii) Selectivity    iv) Bandwidth    (06 Marks)
- b. A series RLC circuit has  $R = 10\Omega$ ,  $L = 0.01H$  and  $C = 0.01\mu F$  and it is connected across 10 mV supply. Calculate: i)  $f_0$  ; ii)  $Q_0$  ; iii) Bandwidth ; iv)  $f_1$  and  $f_2$  ; v)  $I_0$     (10 Marks)
- c. Determine  $R_L$  and  $R_C$  for which the circuit shown in Fig.Q5(c) resonates at all frequencies.

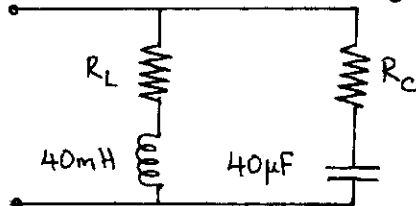


Fig.Q5(c)

(04 Marks)

- 6 a. Explain the transient behaviour of resistance, inductance and capacitance. Also explain the procedure for evaluating transient behaviour.

(10 Marks)

- 6 b. In the network shown in Fig.Q6(b), 'K' is changed from position 'a' to 'b' at  $t = 0$ . Solve for  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ , if  $R = 1000 \Omega$ ,  $L = 1H$  and  $C = 0.1\mu F$  and  $V = 100V$ . Assume that the capacitor is initially uncharged. (10 Marks)

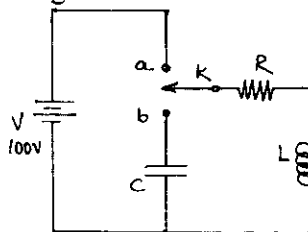


Fig.Q6(b)

- 7 a. Assuming that the staircase waveform of Fig.Q7(a) is not repeated, find its Laplace transform. If this voltage wave is applied to a RL series circuit with  $R = 1\Omega$  and  $L = 1H$ , find the current  $i(t)$ . (10 Marks)

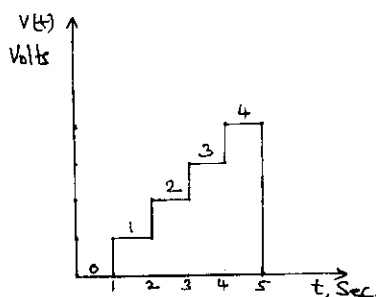


Fig.Q7(a)

- b. The network shown in Fig.Q7(b) was in steady state before  $t = 0$ . The switch is opened at  $t = 0$ . Find  $i(t)$  for  $t > 0$ , using Laplace transform. (10 Marks)

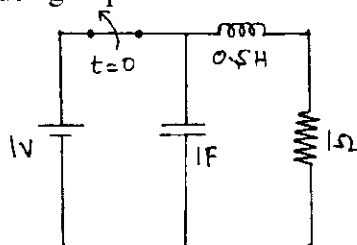


Fig.Q7(b)

- 8 a. Obtain the h-parameters for the network shown in Fig.Q8(a). (10 Marks)

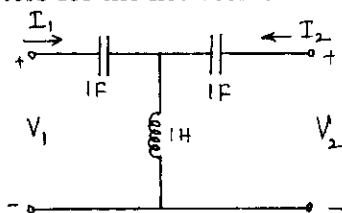


Fig.Q8(a)

- b. Obtain ABCD parameters in terms of z-parameters and hence show that  $AD - BC = 1$ . (10 Marks)

\*\*\*\*\*

