

Third Semester B.E. Degree Examination, Dec.2013/Jan.2014
Network Analysis

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART – A

- 1 a. Using star-delta transformation reduce the given network shown in Fig.Q1(a) and determine the total current supplied by the source. (04 Marks)

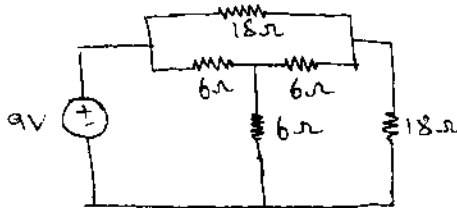


Fig.Q1(a)

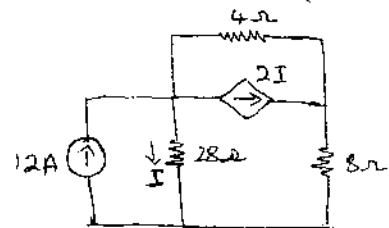


Fig.Q1(b)

- b. Use mesh analysis to calculate the current I in the circuit shown in Fig.Q1(b). (10 Marks)
 c. Find the node voltages in the network shown in Fig.Q1(c) (06 Marks)

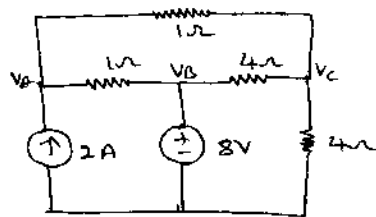


Fig.Q1(c)

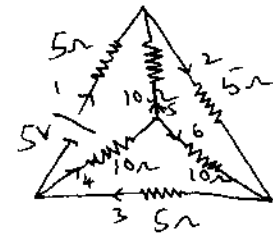


Fig.Q2(b)

- 2 a. Explain the following terms with example as applied to network topology: (i) Oriented graph (ii) Planar and non-planar graph (iii) Tree (iv) Tie-set (v) Cut-set. (10 Marks)
 b. Write the oriented graph for the circuit shown in Fig.Q2(b), taking branches 4, 5, 6 as tree obtain tie-set schedule and using this tie-set schedule obtain equilibrium connection on loop current basis. (10 Marks)
- 3 a. State and prove reciprocity theorem. (05 Marks)
 b. Find the current through 2Ω resistor in the network shown in Fig.Q3(b), using super position theorem. (08 Marks)

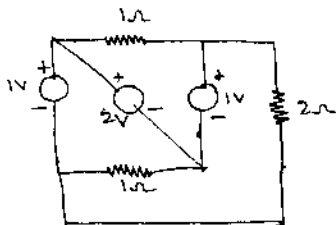


Fig.Q3(b)

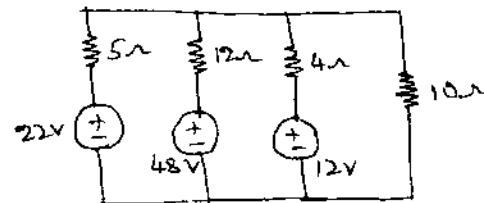


Fig.Q3(c)

- c. Using Millman's theorem find the current through 10Ω resistor in the network shown in Fig.Q3(c). (07 Marks)
- 4 a. State and prove maximum power transfer theorem for DC circuit. (06 Marks)
 b. Determine the Norton's equivalent circuit across terminals ab in the network shown in Fig.Q4(b). (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42-8-50, will be treated as malpractice.

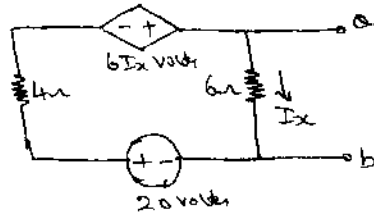


Fig.Q4(b)

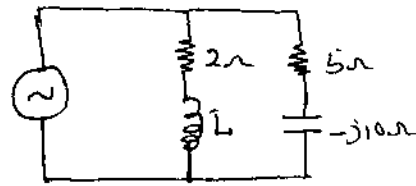


Fig.Q5(c)

- c. A linear time invariant network when terminated with (i) $R = 1\Omega$ the current is $5 \angle -45^\circ$ A (ii) $X_c = 1\Omega$, the current is $10 \angle -45^\circ$ A. Find the Thevenin's equivalent of the network. What will be the current if it is terminated with $X_L = 1\Omega$. (08 Marks)

PART – B

- 5 a. Show that in a series resonant circuit the resonant frequency is the geometric mean of half-power frequencies. (06 Marks)
 b. A series resonant circuit includes $1\mu\text{F}$ capacitor and a resistance of 16Ω , if the bandwidth is 500 rad/sec . Determine (i) W_r (ii) Q (iii) L . (06 Marks)
 c. Find the value of L for which the circuit shown in Fig.Q5(c) is resonate at a frequency of $W = 500\text{ rad/sec}$. (08 Marks)
- 6 a. Explain the behavior of circuit elements Resistor, Inductor and Capacitor during switching conditions. (06 Marks)
 b. In the circuit shown in Fig.Q6(b), the switch is closed at $t=0$. Find i_L , i_C , $\frac{di_L}{dt}$ and $\frac{di_C}{dt}$ at $t = 0^+$. (08 Marks)

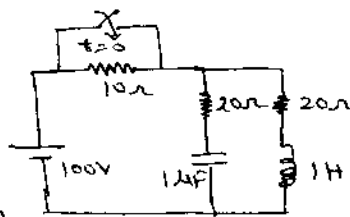


Fig.Q6(b)

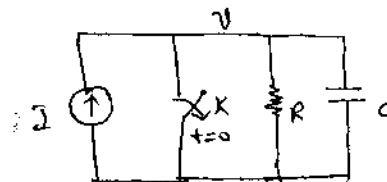


Fig.Q6(c)

- c. In the network shown in Fig.Q6(c), switch 'K' is opened at $t = 0$. Solve for v , $\frac{dv}{dt}$ and $\frac{d^2v}{dt^2}$ at $t = 0^+$, if $I = 10\text{ A}$, $R = 1000\Omega$, $C = 1\mu\text{F}$. (06 Marks)
- 7 a. State and prove initial value theorem and final value theorem. (08 Marks)
 b. Find the Laplace transform of the waveform shown in Fig.Q7(b). (06 Marks)

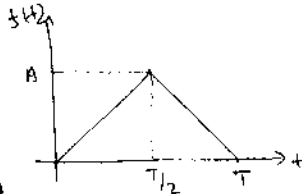


Fig.Q7(b)

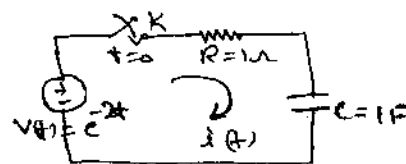


Fig.Q7(c)

- c. Find $i(t)$ for $t > 0$ in the network shown in Fig.Q7(c) using Laplace transformation. Assume $V_C(0^-) = 0\text{ V}$. (06 Marks)
- 8 a. Derive expression for Z-parameters in terms of Y parameters. (08 Marks)
 b. Obtain ABCD parameters in terms of impedance [Z] parameters and hence show that $AD - BC = 1$ (08 Marks)
 c. For a certain two port network V_1 and V_2 are given by

$$\begin{aligned} V_1 &= 60I_1 + 20I_2 \\ V_2 &= 20I_1 + 40I_2 \end{aligned}$$

Find Y – parameters of the network.

(04 Marks)
