

Third Semester B.E. Degree Examination, January 2013
Network Analysis

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART – A

- 1 a. Find the equivalent voltage source across AB in network shown in Fig.Q.1(a) using source transformation. (07 Marks)
- b. Compute the power delivered to the 4Ω resistor in Fig.Q.1(b) using loop current analysis. (07 Marks)
- c. Find V_{CD} in Fig.Q.1(c) using nodal technique. (06 Marks)

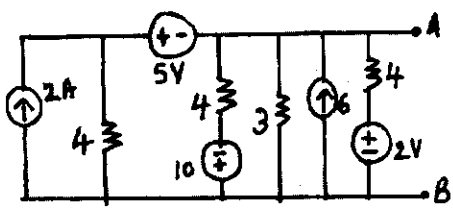


Fig.Q.1(a)

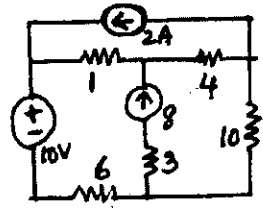


Fig.Q.1(b)

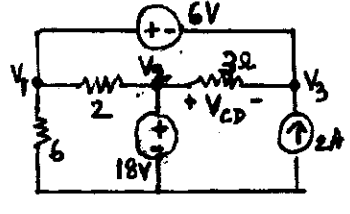


Fig.Q.1(c)

- 2 a. For the network shown in Fig.Q.2(a), draw a graph, an oriented graph, a tree, a connected graph and an unconnected graph. (04 Marks)
- b. Obtain the dual of the circuit shown in Fig.Q.2(b) verify the results by formulating equilibrium equations. (05 Marks)
- c. Formulate the tie-set matrix for the network shown in Fig.Q.2(c). Use 1, 2, 3 as tree branches and hence list the resulting f-loops. (06 Marks)
- d. Develop the fundamental cut-set matrix for the network shown in Fig.Q.2(d). Use 1, 3, 4 as tree branches. (05 Marks)

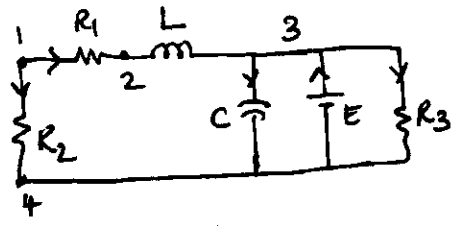


Fig.Q.2(a)

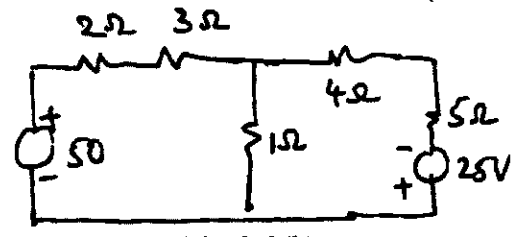


Fig.Q.2(b)

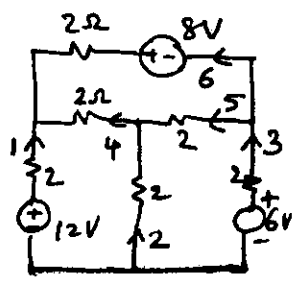


Fig.Q.2(c)

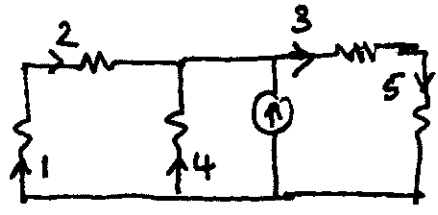


Fig.Q.2(d)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

- 3 a. Using superposition theorem find the voltage 'V' across 3Ω in Fig.Q.3(a). (09 Marks)
 b. State and explain reciprocity theorem. (05 Marks)
 c. State and prove Millman's theorem for current sources in series. (06 Marks)

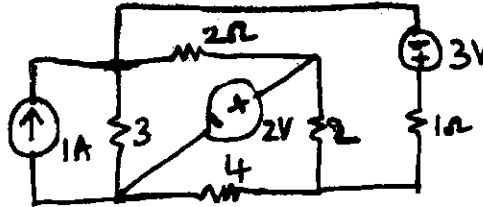


Fig.Q.3(a)

- 4 a. Applying Thevenin's theorem find current in 2_L in Fig.Q.4(a). (06 Marks)
 b. Find I_L in Fig.Q.4(b) using Norton's theorem. (07 Marks)
 c. What is the value of R_L for maximum power transfer in Fig.Q.4(c)? Also find the maximum power. (07 Marks)

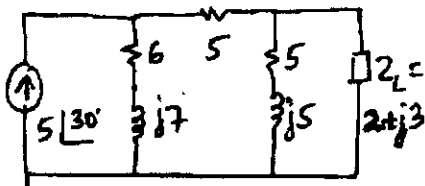


Fig.Q.4(a)

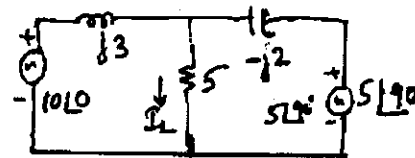


Fig.Q.4(b)

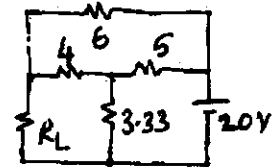


Fig.Q.4(c)

PART - B

- 5 a. A series RLC circuit has a bandwidth of 600Hz and quality factor of 10. If the value of L is 0.05H, find the value of C. (04 Marks)
 b. For a two branch RL-RC parallel resonant circuit, determine the expression for resonant frequency. In this circuit for $L = 0.4H$ and $C = 40\mu F$, obtain resonant frequency for the following values of R_L and R_C i) $R_L = R_C = 80\Omega$; ii) $R_L = 100$ and $R_C = 80$. (08 Marks)
 c. Find band width of the antiresonant circuit shown in Fig.Q.5(c), with following conditions i) Q of the inductive branch = 100; ii) Frequency of unity power factor = 1MHz; iii) $L = 100\mu H$ and iv) Internal resistance of generator $R_g = 10\Omega$. (08 Marks)

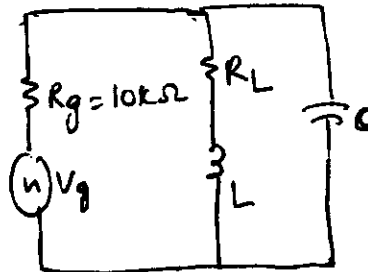


Fig.Q.5(c)

- 6 a. In the network shown in Fig.Q.6(a), the switch K is changed from position 1 to position 2 at $t = 0$, steady - state being established at position 1. Find : $i, \frac{di}{dt}, \frac{d^2i}{dt^2}$ at $t = 0+$. (08 Marks)

- b. The switch K is closed at $t = 0$ in Fig.Q.6(b). At $t = 0^-$ all capacitor voltages and inductor currents are zero. Three node to datum voltages are identified as V_1, V_2 and V_3 . Find $V_1, V_2, V_3, \frac{dv_1}{dt}, \frac{dv_2}{dt}, \frac{dv_3}{dt}$ and $\frac{d^2v_3}{dt^2}$ at $t = 0^+$. (12 Marks)

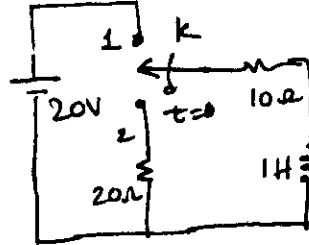


Fig.Q.6(a)

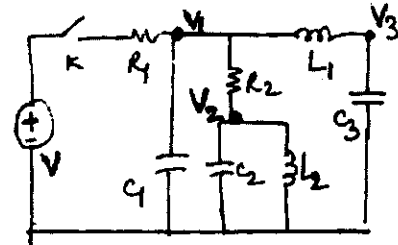


Fig.Q.6(b)

- 7 a. Find the Laplace transform of $x(t)$ shown in Fig.Q.7(a). (06 Marks)
 b. In Fig.Q.7(b), switch K is opened at $t = 0$, steady-state reached at $t = 0^-$. Using Laplace transform, find $I_L(s)$ and hence $i_L(t)$. Also find the value of $i_L(t)$ at $t = 0.5$ seconds. (10 Marks)
 c. Find the initial and final values of $f(t)$ when $F(s) = \frac{9s + 10}{S(s + 2)}$. (04 Marks)

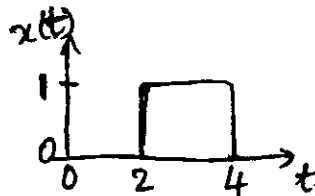


Fig.Q.7(a)

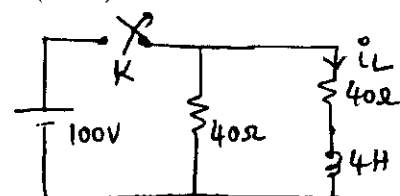


Fig.Q.7(b)

- 8 a. Compute V_1 and V_2 in Fig.Q.8(a) with admittance matrix $[y] = \begin{bmatrix} 0.3 & -0.1 \\ -0.1 & 0.15 \end{bmatrix}$. (08 Marks)
 b. Obtain the open-circuit impedance parameters for the network shown in Fig.Q.8(b). (08 Marks)
 c. Obtain T-parameters in terms of z-parameters. (04 Marks)

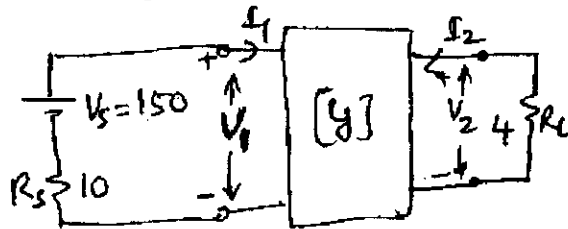


Fig.Q.8(a)

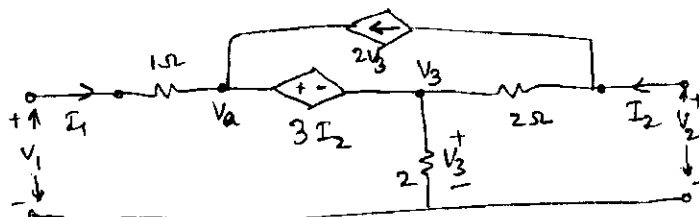


Fig.Q.8(b)

