

USN

--	--	--	--	--	--	--	--	--	--

15EC34

Third Semester B.E. Degree Examination, July/August 2022 Network Analysis

Time: 3 hrs.


Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1


- 1 a. Find the current 'I' in 5Ω using Mesh analysis for Fig. Q1(a). (08 Marks)

Fig. Q1(a)

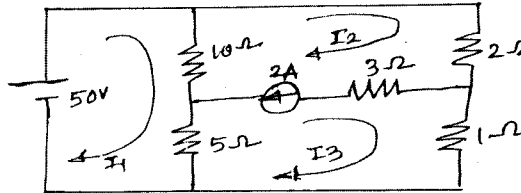

- b. Find the voltage V_x using Node Analysis for Fig. Q1(b). (08 Marks)


Fig. Q1(b)

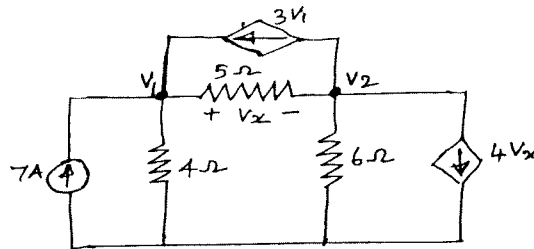

OR


- 2 a. Determine the resistance between A and B using Δ to Y conversion for Fig. Q2(a). (04 Marks)

Fig. Q2(a)

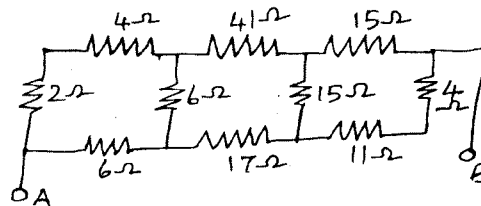


- b. Find the current I_1, I_2 using Mesh Analysis for Fig. Q2(b). (06 Marks)

Fig. Q2(b)

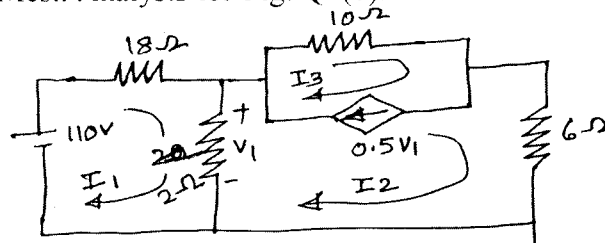

- c. Calculate I_1, I_2, I_3, V_a, V_b using Node analysis for Fig. Q2(c). (06 Marks)

Fig. Q2(c)

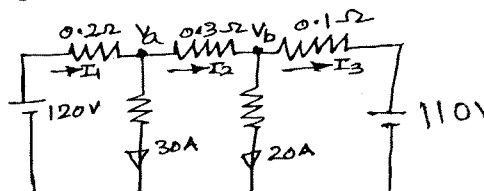


Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42-8 = 50, will be treated as malpractice.

Module-2


- 3 a. State and prove Thevenin's theorem. (05 Marks)
 b. Find I_x using Super position theorem for Fig. Q3(b). (05 Marks)

Fig. Q3 (b)

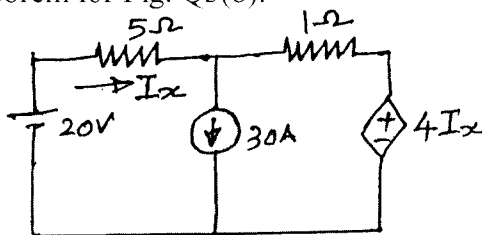

- c. Verify the Reciprocity theorem for the circuit in Fig. Q3(c). (06 Marks)


Fig. Q3 (c)

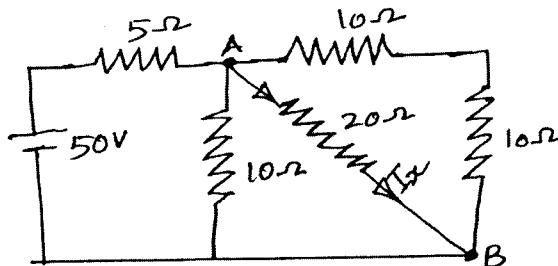

OR


- 4 a. State and prove Milliman's theorem. (05 Marks)
 b. Determine I through 8Ω using Norton's theorem for Fig. Q4(b). (05 Marks)

Fig. Q4 (b)

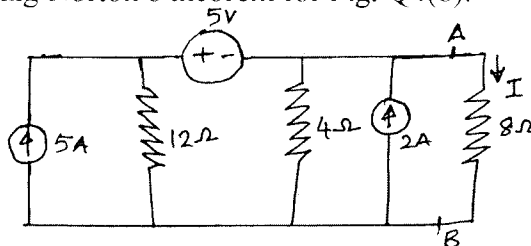

- c. Find the value of R_L and Maxi Power delivered to R_L using Maxi Power theorem for Fig. Q4(c). (06 Marks)


Fig. Q4 (c)

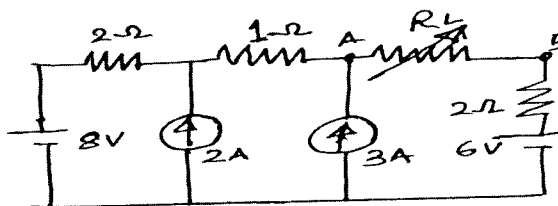

Module-3


- 5 a. S – opened at $t = 0$ for the circuit Fig. Q5(a). Calculate $V(0^+)$
 $\frac{dv(0^+)}{dt}$, $\frac{d^2v(0^+)}{dt^2}$. (05 Marks)

Fig. Q5(a)

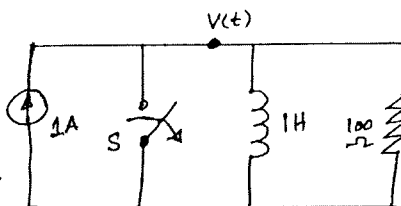

- b. S – is moved from 1 to 2 at $t = 0$ find $I(0^+)$, $\frac{dI(0^+)}{dt}$, $\frac{d^2I(0^+)}{dt^2}$ for the circuit in Fig. Q5(b).

Fig. Q5 (b)

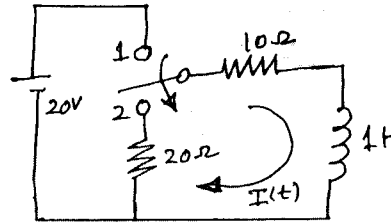


(05 Marks)

- c. S – is moved from 1 to 2 at $t = 0$. Determine $I(t)$ using Laplace Transformation for $t > 0$ in the circuit Fig. Q5(c).

(06 Marks)


Fig. Q5 (c)

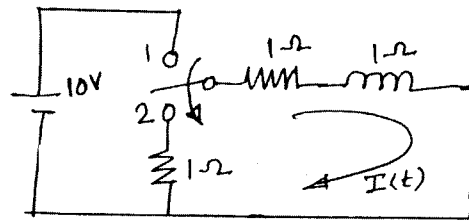

OR

- 6 a. Find Inverse Laplace Transform of $\frac{1}{s(s+1)}$. (04 Marks)
- b. S – is changed from 1 to 2 at $t = 0$, find $I(t)$ for $t > 0$ in the circuit Fig. Q6(b). (06 Marks)

Fig. Q6 (b)

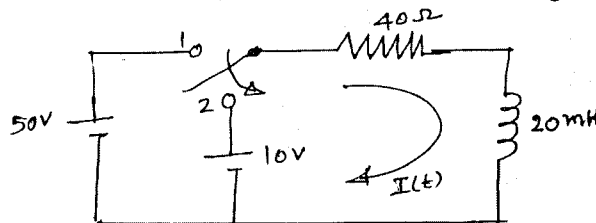

- c. A series R, L circuit with initial current I_0 in inductor is connected to a D.C voltage V at $t = 0$. Derive an expression for $I(t)$ through the inductor for $t > 0$. (06 Marks)

Module-4


- 7 a. Show the resonance frequency $f_0 = \sqrt{f_1 f_2}$ for series resonance circuit. (05 Marks)
- b. Derive an expression for resonance frequency f_0 in case of parallel resonance circuit when inductor L resistance R_L is considered. (05 Marks)
- c. A series resonance circuit $C = 1\mu\text{F}$ and its inductor L resistance is 16Ω . If the Bandwidth is 500rad/sec . Determine f_0 , Q, L. (06 Marks)

OR

- 8 a. Define Q – factor, Bandwidth, selectivity of series resonance circuit. (06 Marks)
- b. Determine the frequency ω_c , when the voltage across the capacitor is maximum in case of series resonance circuit. (05 Marks)

- c. The inductor value $L = 0.1\text{H}$ for the circuit Fig. Q8(c) and its Q value is 5. The resonance frequency of the circuit is 500rad/sec . Determine the values of capacitance C and R. (05 Marks)


Fig. Q8 (c)

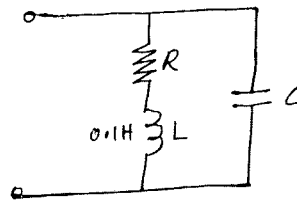

Module-5


- 9 a. Determine Z – parameters for the circuit Fig. Q9(a). Using interrelationship between parameters, find Y parameters. (08 Marks)

Fig. Q9 (a)

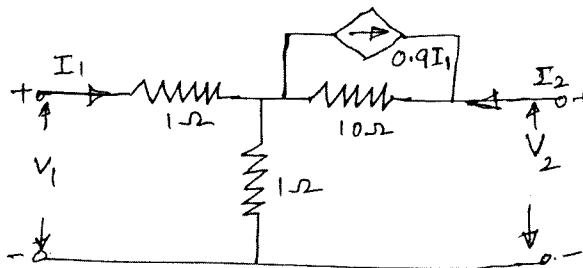

- b. Determine the h – parameters for the circuit Fig. Q9(b). (08 Marks)

Fig. Q9 (b)

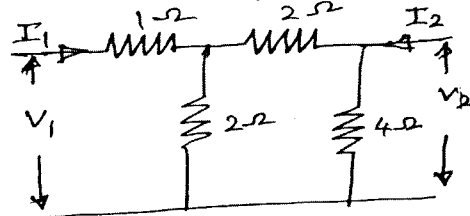

OR

- 10 a. Define Z – parameters and obtain the condition for symmetry. (08 Marks)
 b. Determine Z – parameters, using Interrelationship between parameters, determine h parameters for the circuit Fig. Q10(b). (08 Marks)

Fig. Q10 (b)

