

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, June 2012
Network Analysis

Time: 3 hrs.

Max. Marks: 100

Note: 1. Answer FIVE full questions, selecting at least TWO questions from each part.
2. Missing data, if any, may suitably be assumed.

PART – A

- 1 a. Find the equivalent resistance at AB using Y - Δ transformation technique in Fig. Q1(a). (05 Marks)
- b. Find the current I in 28 Ω resistor by Mesh analysis in Fig. Q1(b). (05 Marks)
- c. Find the power dissipated in 10 Ω resistor by node voltage method in Fig. Q1(c). (10 Marks)

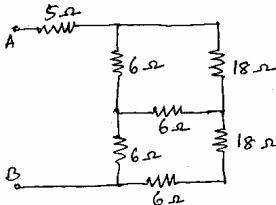


Fig. Q1(a)

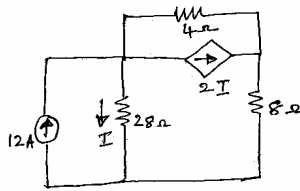


Fig. Q1(b)

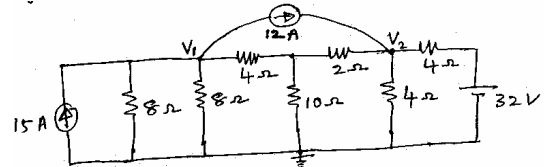


Fig. Q1(c)

- 2 a. Write the oriented graph of the network shown in Fig. Q2(a). The numerical values of resistances also indicate the branch numbers. Select a tree with branches 1, 2, 3 as the tree branches, write tieset and cutset schedule. (10 Marks)
- b. For the network shown in Fig. Q2(b), draw the dual network and write the node equations. (10 Marks)

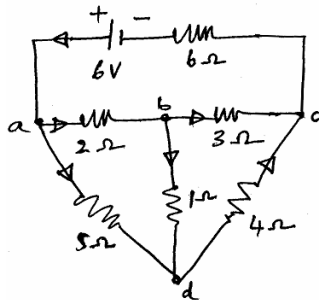


Fig. Q2(a)

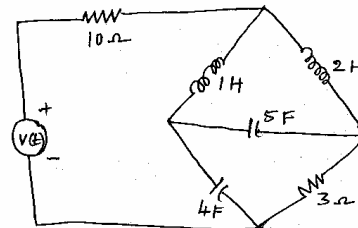


Fig. Q2(b)

- 3 a. Determine the current through 10 Ω resistance of the network shown in Fig. Q3(a), using superposition theorem. (10 Marks)
- b. State Milliman's theorem. Using Milliman's theorem, find I_L through R_L for the network shown in Fig. Q3(b). (10 Marks)

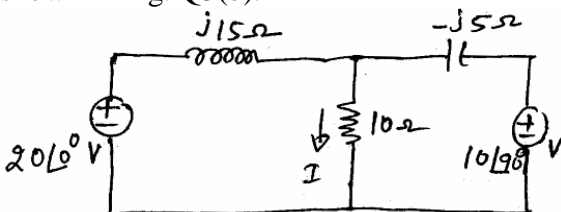


Fig. Q3(a)

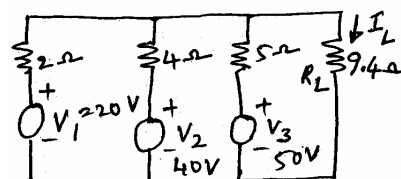


Fig. Q3(b)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- 4 a. State Thevenin's theorem. For the circuit shown in Fig. Q4(a), find the current through R_L using Thevenin's theorem. (10 Marks)
- b. State maximum power transfer theorem. For the circuit shown in Fig. Q4(b), find the value of Z_L for which maximum power transfer occurs. Also find P_{max} . (10 Marks)

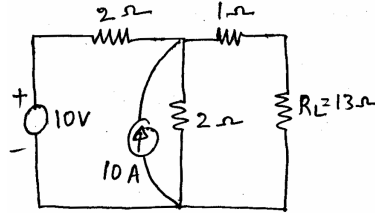


Fig. Q4(a)

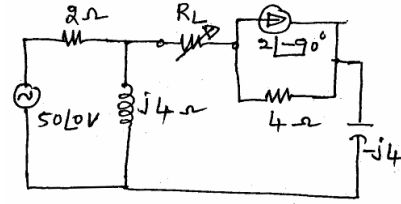


Fig. Q4(b)

PART - B

- 5 a. Define quality factor and bandwidth. Also establish the relationship between quality factor and bandwidth in a series resonance circuit and thereby prove that $Q = \frac{f_0}{BW}$, where f_0 is the resonance frequency. (10 Marks)
- b. A series RLC circuit with $R = 10 \Omega$, $L = 10\text{mH}$ and $C = 1\mu\text{F}$ has an applied voltage of 200 V at resonant frequency. Calculate the resonant frequency f_0 , the current in the circuit at resonance, voltage across the elements at resonance. Also find quality factor and bandwidth. (10 Marks)

- 6 a. Determine : i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t=0+$ when the switch is closed at $t = 0$ in Fig. Q6(a). (10 Marks)
- b. Determine : i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0 +$ when the switch K is moved from position 1 to 2 at $t = 0$ in the network shown in Fig. Q6(b), steady state having reached before switching. (10 Marks)

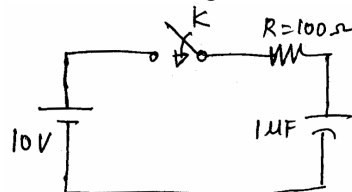


Fig. Q6(a)

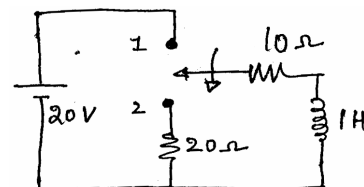


Fig. Q6(b)

- 7 a. Find the expression for the resultant current $i(t)$ when switch K is closed at $t = 0$ in Fig. Q7(a). (10 Marks)
- b. Find the Laplace transform of the given function $f(t) = 5 + 4e^{-2t}$. (04 Marks)
- c. Find the L.T of the saw tooth waveform in Fig. Q7(c). (06 Marks)

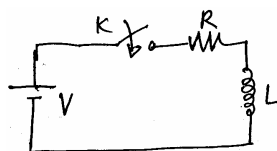


Fig. Q7(a)

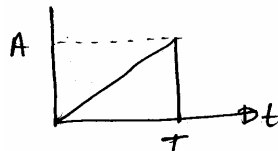


Fig. Q7(c)

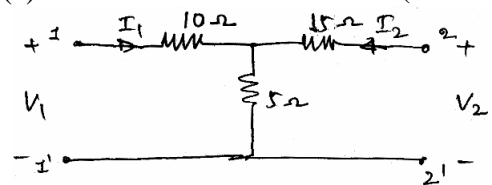


Fig. Q8(a)

- 8 a. Find the Z-parameters for the network shown in Fig. Q8(a). (10 Marks)
- b. The Z-parameters of a two port network are $Z_{11} = 20 \Omega$, $Z_{22} = 30 \Omega$, $Z_{12} = Z_{21} = 10\Omega$. Find Y and ABCD parameters of the network. (10 Marks)
