

USN

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

06ES34

Third Semester B.E. Degree Examination, June/July 2011
Network Analysis

Time: 3 hrs.

Max. Marks:100

Note: 1. Answer any FIVE full questions selecting at least TWO questions from each part.
2. Missing data may be suitably assumed.

PART - A

- 1 a. Using source transformation and source shifting techniques, find voltage across 2Ω resistor in Fig.Q1(a). (06 Marks)
- b. Find equivalent resistance at AB terminals in Fig.Q1(b). (06 Marks)
- c. Find current in 2Ω resistors by Mesh analysis in Fig.Q1(c). (08 Marks)

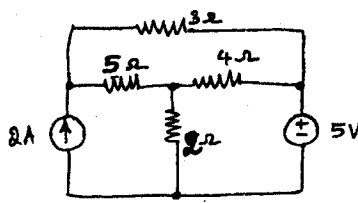


Fig.Q1(a)

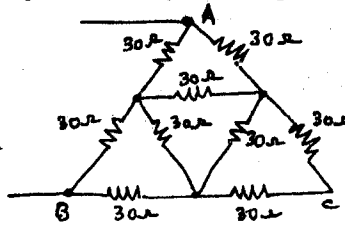


Fig.Q1(b)

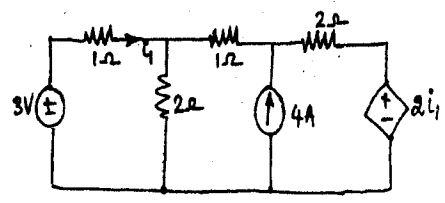


Fig.Q1(c)

- 2 a. Define the terms (i) graph, (ii) branch, (iii) node, (iv) tree, (v) link as referred to network topology. (04 Marks)
- b. Write a tie-set schedule and then find all the branch currents for the circuit shown in Fig.Q2(b). (08 Marks)
- c. Write the dual network for the network shown in Fig.Q2(c). Write the equations governing the given network and for its dual as well. (08 Marks)

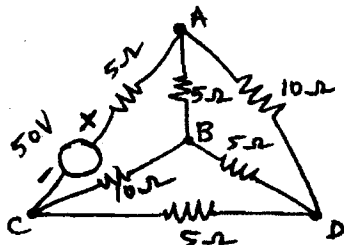


Fig.Q2(b)

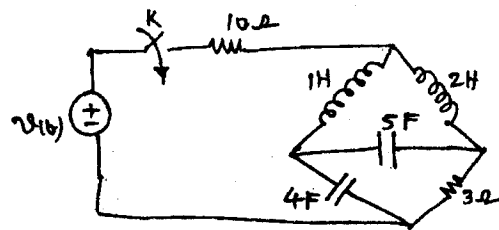


Fig.Q2(c)

- 3 a. Find V using the principle of superposition in network. State superposition theorem in Fig.Q3(a). (10 Marks)
- b. State reciprocity theorem. Find i_x and hence verify reciprocity theorem for the network in Fig.Q3(b). (10 Marks)

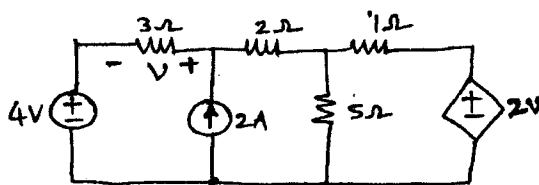


Fig.Q3(a)


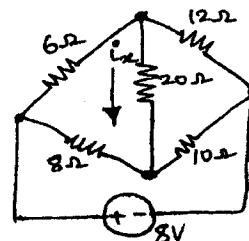
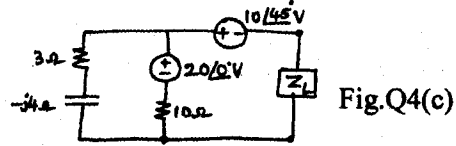


Fig.Q3(b)



Important Note : 1. On completing your answers(impulsorily draw diagonal cross lines on the remaining by pages. 2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

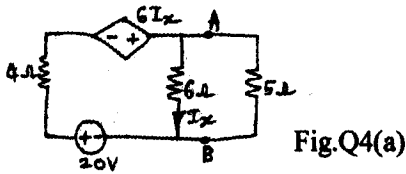- 4 a. State Norton's theorem. Determine the Norton's equivalent circuit across AB terminals in the network of Fig.Q4(a). Hence determine current in 5Ω resistor. (10 Marks)
 b. State maximum power transfer theorem for a variable impedance Z_L as load and prove the same. (05 Marks)
 c. Find the value of Z_L for which maximum power transfer occurs in the circuit given in Fig.Q4(c). (05 Marks)





PART - B

- 5 a. Explain the properties of RLC series resonant circuit. (04 Marks)
 b. Find the resonant frequency in a series resonant circuit having an inductance of 50 mH and a condenser of $5\mu\text{F}$. Find the resistance of the circuit if the circuit draws a current of 10 mA at resonance with a supply voltage of 50V. Also find the quality factor of the circuit. (06 Marks)
 c. Explain in brief bandwidth and selectivity in series resonant circuit. A series RLC circuit has $R = 2\Omega$, $L = 2\text{mH}$ and $C = 10\mu\text{F}$. Calculate Q factor, the bandwidth, the resonant frequency and the half power frequencies f_1 and f_2 . (10 Marks)
- 6 a. Explain the behaviour of R, L, C elements at the time of switching, at $t = 0$ both at $t = 0+$ and $t = \infty$. (06 Marks)
 b. Determine i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0+$ when the switch K is moved from position 1 to 2 at $t = 0$ in the network shown in Fig.Q6(b). (07 Marks)
 c. Determine V , $\frac{dV}{dt}$ and $\frac{d^2V}{dt^2}$ at $t = 0+$ when the switch K is opened at $t = 0$ in Fig.Q6(c). (07 Marks)

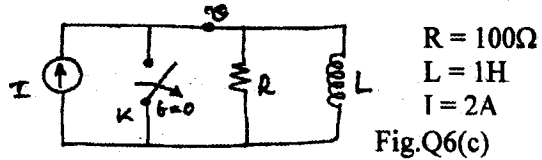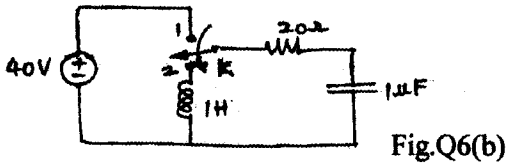

- 7 a. Find the current $i(t)$ when switch K is opened at $t = 0$ with the circuit having reached steady state before the switching in Fig.Q7(a). Find current at $t = 0.5$ sec. (10 Marks)
 b. Find the current $i(t)$ assuming zero initial conditions when switch K is closed at $t = 0$; The excitation $V(t)$ is a pulse of magnitude 10V and duration of 2 sec. Consider $R = 10\Omega$, $C = 2\text{F}$. Refer Fig.Q7(b). (10 Marks)

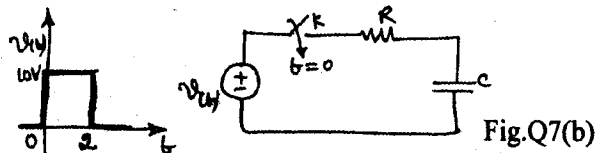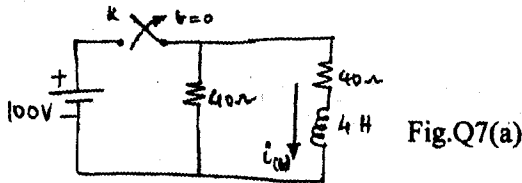

- 8 a. Define Z parameters. Determine Z parameters for the network shown in Fig.Q8(a). (10 Marks)
 b. Define transmission parameters. Determine the transmission parameters for the network shown in Fig.Q8(b). (10 Marks)

