

# CBCS Scheme

USN

15EC34

## Third Semester B.E. Degree Examination, June/July 2017

### Network Analysis



Time: 3 hrs.

Max. Marks: 80

**Note:** Answer any FIVE full questions, choosing ONE full question from each module.

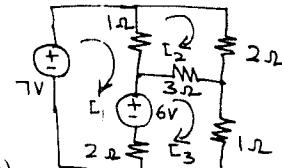
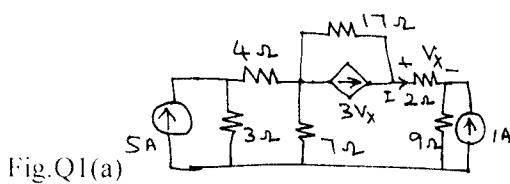
#### Module-1

- 1 a. Calculate the current through  $2\Omega$  resistor for the circuit shown in Fig.Q1(a) using source transformation. (08 Marks)
- b. Use mesh analysis to determine the three mesh currents  $I_1$ ,  $I_2$  and  $I_3$  in the circuit shown in Fig.Q1(b). (08 Marks)



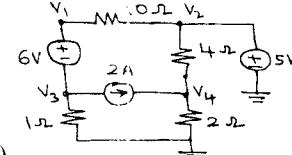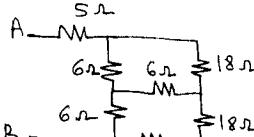**OR**


- 2 a. Find the equivalent resistance  $R_{AB}$  using star and delta transformation for network shown in Fig.Q2(a). (08 Marks)



- b. For the circuit shown in Fig.Q2(b), determine all node voltages. (08 Marks)
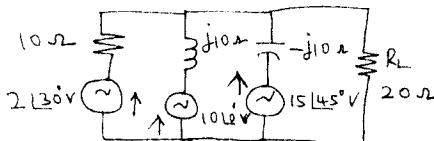
#### Module-2



- 3 a. Using Millman's theorem, find the current through load resistance  $R_L$  for the circuit shown in Fig.Q3(a). (08 Marks)



- b. State the maximum power transfer theorem and also prove that  $P_{max} = \frac{V_{th}^2}{4R_L}$ , where  $V_{th}$  = thevenins voltage. (08 Marks)

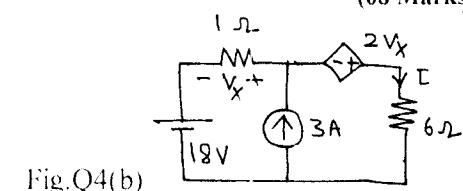
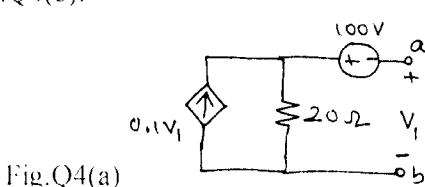
**OR**

- 4 a. Obtain the Thevenin's equivalent of the circuit shown in Fig.Q4(a). (08 Marks)
- b. Using superposition theorem, find the current in  $6\Omega$  resistor in the network shown in Fig.Q4(b). (08 Marks)




Module-3

- 5 a. In the network shown in Fig.Q5(a), the switch is closed at  $t = 0$ , determine  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0$ . (08 Marks)  
 b. For the network shown in Fig.Q5(b), the switch 's' is opened at  $t = 0$  solve for  $V$ ,  $DV$  and  $D^2V$  at  $t = 0$ . (08 Marks)

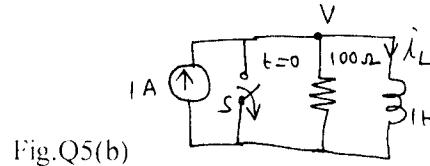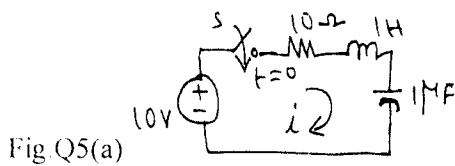
**OR**

- 6 a. Find the Laplace transform of the periodic signal  $x(t)$  shown in Fig.Q6(a). (08 Marks)  
 b. Given the signal  $x(t) = \begin{cases} 3, & t < 0 \\ -2 & 0 < t < 1 \\ 2t - 4 & t > 1 \end{cases}$

Express  $x(t)$  in terms of singularity functions. Also find the Laplace transform of  $x(t)$ . (08 Marks)

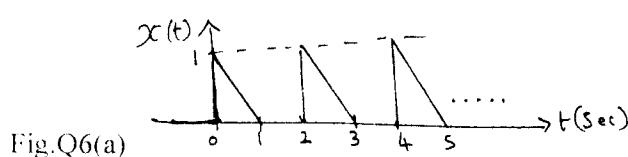Module-4



- 7 a. Derive the expressions of half power frequencies  $W_1$  and  $W_2$  and also bandwidth of a series resonance circuit. (09 Marks)  
 b. Find the values of  $L$  at which the circuit shown in Fig.Q7(b) resonates at a frequency of 500 rad/s. (07 Marks)

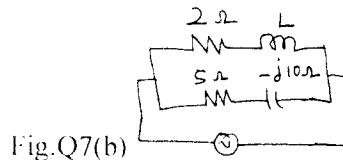**OR**

- 8 a. Derive the expressions of a resonance frequency and dynamic impedance of a parallel resonance circuit. (09 Marks)  
 b. A coil has a  $R = 20\Omega$ ,  $L = 80mH$  and  $C = 100\mu F$  are connected in series. Determine : i) impedance at resonance ii) resonance frequency iii) quality factor iv) circuit current if supply voltage is 50V. (07 Marks)

Module-5

- 9 a. Derive the expression of Z-parameters in term of h-parameter. (07 Marks)  
 b. Find the ABCD – parameters for the network shown in Fig.Q9(b). (09 Marks)

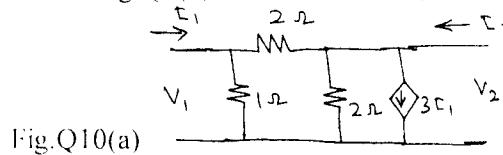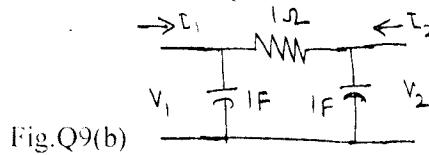**OR**

- 10 a. Find the Y-parameter for the two port network shown in Fig.Q10(a). (08 Marks)  
 b. Obtain the expression of h-parameters in terms of Y-parameters. (08 Marks)

\* \* \* 2 of 2 \* \*