

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, June/July 2023 Network Analysis

Time: 3 hrs.


Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1


- 1 a. Reduce the network shown in Fig. Q1(a) into a single voltage source in series with a resistance using source shift and source transformation. (08 Marks)

Fig. Q1(a)

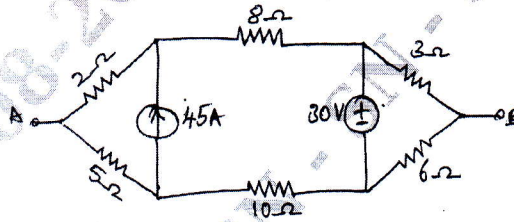

- b. Using Star – delta transformation, determine the resistance between A and B for the network shown in Fig. Q1(b). (08 Marks)


Fig. Q1(b)

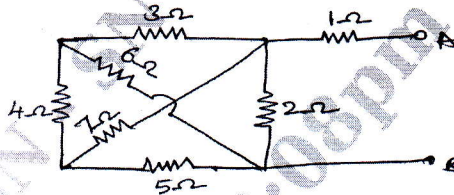

OR


- 2 a. For the network shown in Fig. Q2(a), find the current through 4Ω and 6Ω resistors. (06 Marks)

Fig. Q2(a)

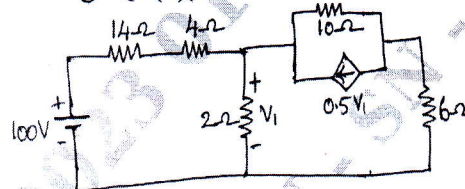


- b. Find the Power delivered by the dependent current source shown in Fig. Q2(b). (06 Marks)

Fig. Q2(b)

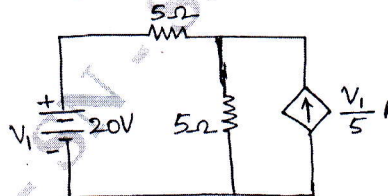


- c. Find i_1 using nodal analysis for the circuit shown in Fig. Q2(c). (04 Marks)

Fig. Q2(c)

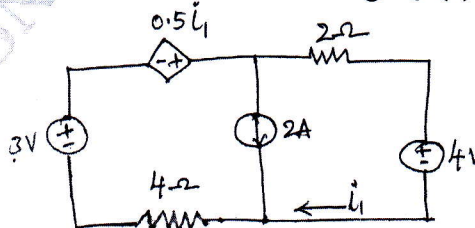

Module-2

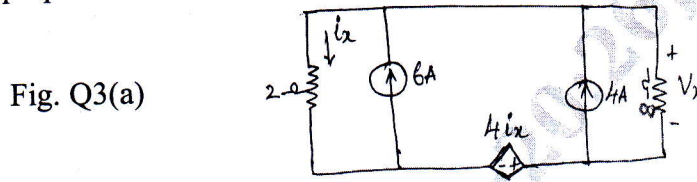
- 3 a. Use Superposition theorem to find V_x in the circuit shown in Fig. Q3(a). (08 Marks)



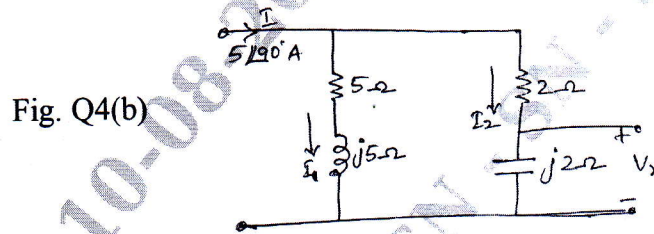- b. State and prove Thevenin's theorem. (08 Marks)

OR


- 4 a. State and prove Millman's theorem. (08 Marks)
 b. For the circuit shown in Fig. Q4(b), find the voltage V_x and verify the Reciprocity theorem. (08 Marks)



Module-3


- 5 a. State and prove Initial value theorem and Final value theorem. (08 Marks)
 b. In the network shown in Fig. Q5(b), switch 'K' is changed from position a to b at $t = 0$.

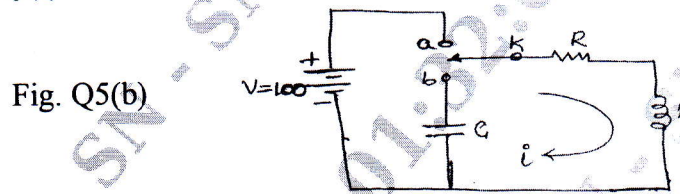Determine $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$. If $R = 1k\Omega$, $\alpha = 1H$, $C = 0.1\mu f$ and $V = 100V$. Assume $V_c(0^-) = 0V$. (08 Marks)




OR

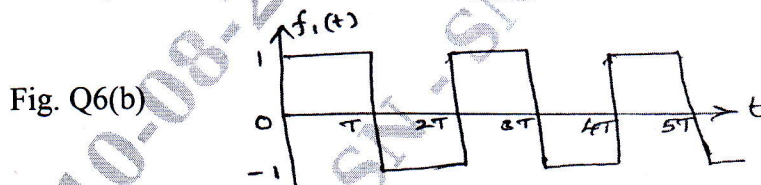- 6 a. Find the Laplace transforms of Unit step and Unit Ramp function. (08 Marks)
 b. Obtain the Laplace transform of the square wave train shown in Fig. Q6(b). (08 Marks)



Module-4

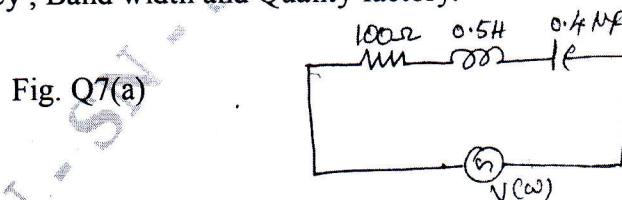- 7 a. For a series RLC circuit shown in Fig. Q7(a), find the Resonant frequency, Half power frequency, Band width and Quality factor. (08 Marks)




- b. Show that Band width of series RLC resonant circuit is $\Delta f = \frac{R}{4\pi L}$ (08 Marks)

OR

- 8 a. A resonant circuit with capacitor is in parallel with series combination of resistance and inductance. Derive the expression for Resonant frequency (f_{ar}). (08 Marks)
 b. For the parallel resonant circuit shown in Fig. Q8(b). Find I_o , I_a , I_c , F_o and dynamic resistance. (08 Marks)


Fig. Q8(b)

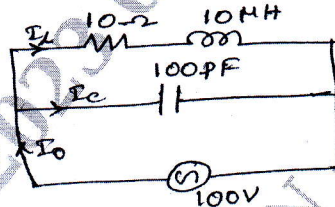

Module-5

- 9 a. Derive the expression for Open circuited impedance parameters. (08 Marks)
 b. Determine Y – parameters for the network shown in Fig. Q9(b). (08 Marks)


Fig. Q9(b)

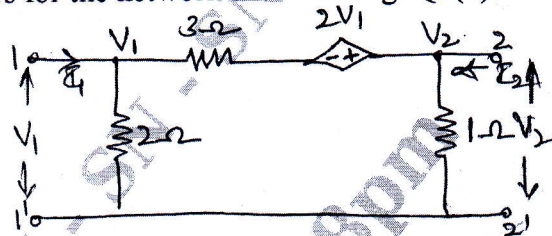

OR

- 10 a. Determine Transmission parameters for the network shown in Fig. Q10(a). (08 Marks)

Fig. Q10(a)

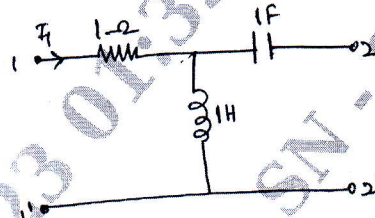

- b. The Z – parameters of a two port network are $Z_{11} = 20\Omega$, $Z_{22} = 30\Omega$, $Z_{12} = Z_{21} = 10\Omega$. Find Y and ABCD parameters of the network. (08 Marks)
