

Third Semester B.E. Degree Examination, Dec.08/Jan.09
Analog Electronic Circuits

Time: 3 hrs.

Max. Marks:100

- Note :** 1. Answer any FIVE full questions selecting at least 2 questions from each part.
 2. Draw equivalent circuit wherever necessary.

PART - A

- 1 a. Explain the different diode equivalent circuits with necessary approximations if any. (06 Marks)
 b. Explain junction capacitance with reference to a PN – diode. (06 Marks)
 c. Sketch the waveform of V_0 for the circuit below. (08 Marks)

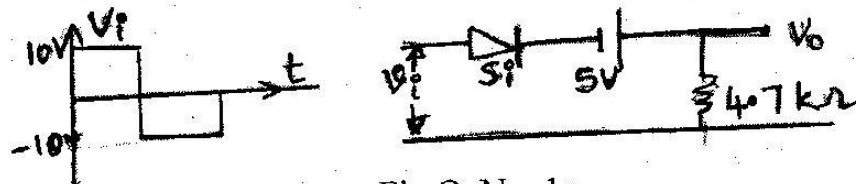


Fig Q. No. 1c.

- 2 a. Explain with help of load line the effect of variation of V_{CC} , I_B on Q-pt of a transistor. (06 Marks)
 b. For the voltage Feedback network below determine I_C , V_{CE} , V_C , V_E . (08 Marks)

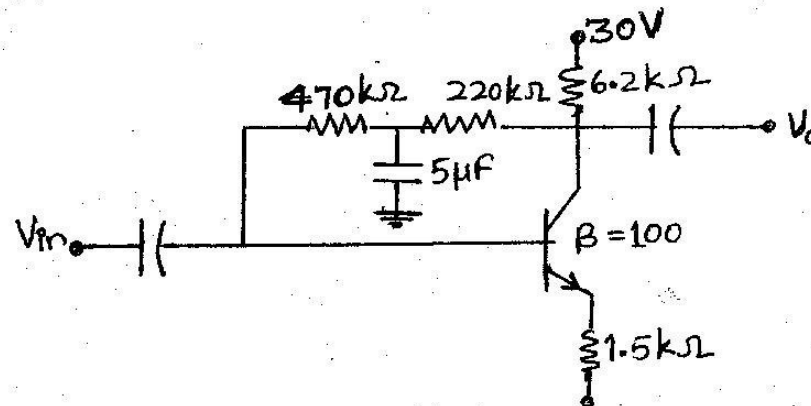


Fig. Q. No. 2b

- c. Derive expression for S_{ICO} for a Voltage Divider bias circuit. (06 Marks)
- 3 a. Draw r_e and h – parameter models of a transistor in CE – mode. Give relation between r_e parameters and h – parameters. (05 Marks)
 b. A voltage divider biased amplifier has $V_{CC} = 20V$, $R_1 = 220k\Omega$, $R_2 = 56k\Omega$, $R_C = 6.8k\Omega$, $R_E = 2.2k\Omega$. The Silicon transistor used has $\beta = 180$ and $r_o = 70k\Omega$.
 Find: i) ac emitter diode resistance, r_e .
 ii) Input impedance.
 iii) Voltage Gain. Draw the r_e -model equivalent circuit. (10 Marks)

c. Given a packaged amplifier below, find

i) Voltage gain with $R_L = 4k\Omega$.

ii) Voltage gain with $R_L = 22k\Omega$.

Comment on the result of Part (i) and (ii)

(05 Marks)

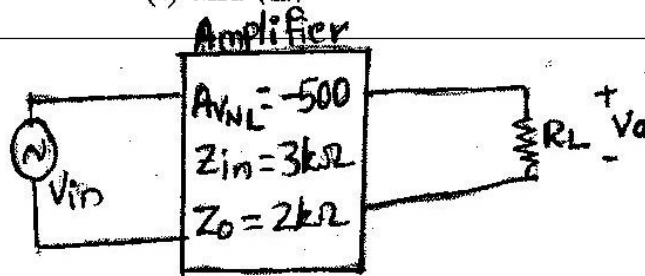


Fig. Q.No. 3c.

4 a. Explain low frequency response of BJT amplifier and give expression for lower cut-off frequency due to C_C , C_E and C_S . (10 Marks)

b. Obtain expression for miller effect input and miller effect output capacitance. (10 Marks)

PART - B

5 a. With necessary equivalent diagram obtain the expression for Z_{in} , A_v , Z_o for a Darlington Emitter follower. (08 Marks)

b. What are the effects of negative feedback? (06 Marks)

c. Obtain expression for Z_{in} , Z_o for a voltage – series feedback. (06 Marks)

6 a. What are the classification of Power Amplifiers based on the location of Q-pt? Also indicate the operating cycle in each case. (06 Marks)

b. Prove that the maximum conversion efficiency in class-B power amplifier is 78.5%. (08 Marks)

c. A power amplifier has harmonic distortions $D_2 = 0.1$, $D_3 = 0.02$, $D_4 = 0.01$, the fundamental current $I_1 = 4A$ and $R_L = 8\Omega$. Calculate the total harmonic distortion, fundamental power and total power. (06 Marks)

7 a. Explain characteristics of a quartz crystal. With a neat diagram explain the crystal oscillator in Parallel – resonant circuits. (10 Marks)

b. Explain how a feedback circuit can be used as oscillator. (04 Marks)

c. Calculate operating frequency of a BJT phase – Shift oscillator for $R = 6k\Omega$, $C = 1500pF$, $R_C = 18k\Omega$. Determine minimum current gain of transistor required for sustained oscillations. (06 Marks)

8 a. Define transconductance g_m . Derive expression for g_m . (06 Marks)

b. A JFET has $g_m = 6mV$ at $V_{GS} = -1V$. Find I_{DSS} if pinch off voltage $V_P = -2.5V$. (04 Marks)

c. With necessary equivalent circuit obtain the expression for A_v , Z_{in} , Z_o for a fixed-biased JFET Amplifier. (10 Marks)