

**Third Semester B.E. Degree Examination, June / July 08**  
**Analog Electronic Circuits**

Time: 3 hrs.

Max. Marks:100

**Note : Answer any FIVE full questions, selecting  
atleast two questions from each part.**

**PART A**

1. a. Differentiate between static and dynamic resistance of a semi conductor diode. (04 Marks)  
 b. Explain with the help of a circuit diagram the working of a Full Wave Rectifier. Derive expressions for i)  $I_{dc}$  ii)  $I_{rms}$  iii)  $V_{dc}$  iv) Ripple factor v) Rectifier efficiency. (10 Marks)  
 c. For the circuit shown, in Fig.Q1(c) write the transfer characteristic equations. Assume diodes are ideal. Plot  $V_o$  against  $V_i$ , indicating all slopes and voltage levels. (06 Marks)

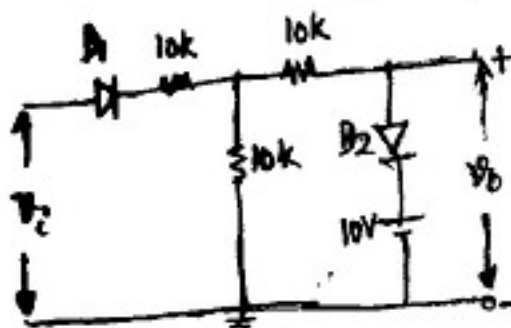


Fig.Q1(c)

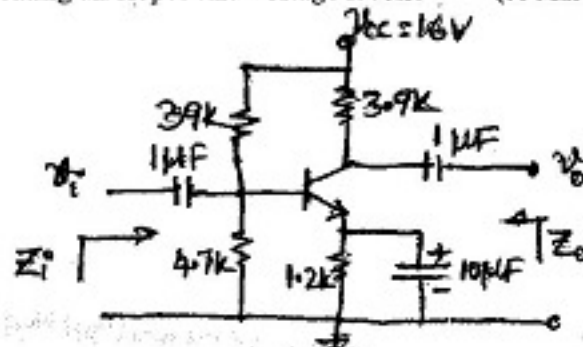


Fig.Q3(a)

2. a. Design a voltage divider bias circuit with  $V_{CC} = 10\text{ V}$ ,  $R_C = 1.5\text{ K ohm}$ ,  $I_C = 2\text{ mA}$ ,  $V_{CE} = 5\text{ V}$ ,  $\beta = 50$ . Assume silicon transistor and stability factor  $S = 5$ . (08 Marks)  
 b. Derive an expression for the stability factor  $S(I_{CO})$  for a voltage divider bias circuit. (08 Marks)  
 c. Determine  $R_B$  and  $R_C$  for the transistor inverter of Fig.Q2(c) if  $I_{Csat} = 10\text{ mA}$ . (04 Marks)

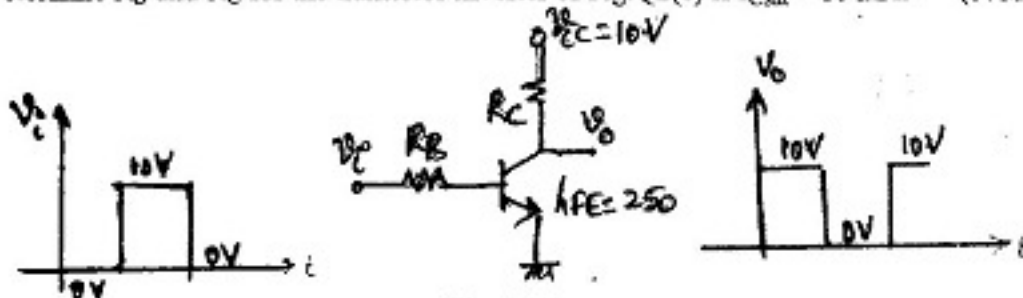


Fig.Q2(c)

3. a. For the network of Fig.Q3(a): i) Determine  $r_e$  ii) Calculate  $Z_i$  and  $Z_o$  iii) Find  $A_v$   
 Given  $\beta = 100$  Si transistor. (08 Marks)  
 b. Draw the emitter follower circuit. Derive expressions for:  
 i)  $Z_i$  ii)  $Z_o$  iii)  $A_v$  using  $r_e$  model. (08 Marks)  
 c. Define h-parameters. Draw the h-parameter model of a transistor. (04 Marks)
4. a. Determine the lower cutoff frequency for the network of Fig.Q4(a). Given  $\beta = 100$ ,  $r_e = x\text{ ohm}$ . Determine the mid band gain. If  $C_{be} = 36\text{ pF}$ ,  $C_{bc} = 4\text{ pF}$ ,  $C_{w_i} = 6\text{ pF}$ ,  $C_{w_o} = 8\text{ pF}$ . Determine  $f_{H_i}$  and  $f_{H_o}$  and sketch the frequency response for low and high frequency regions using the results. (12 Marks)

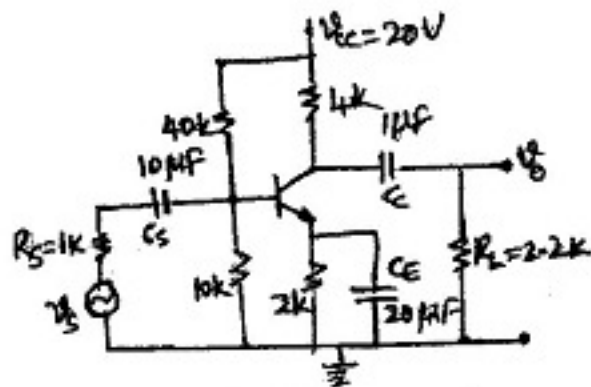


Fig.Q4(a)

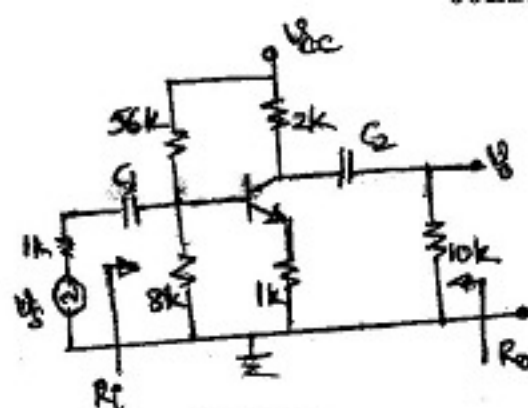


Fig.Q5(b)

- b. Calculate the overall lower 3 db and upper 3 db frequencies for a 3 stage amplifier having an individual  $f_1 = 40$  Hz and  $f_2 = 2$  MHz. (08 Marks)

**PART B**

- 5 a. Draw the cascade configuration and list the advantages of this circuit. (04 Marks)  
 b. Determine  $A_i$ ,  $R_i$ ,  $A_v$  and  $R_o$  for the circuit shown in fig.Q5(b). Given h parameters  $h_{ie} = 1.1$  k ohm,  $h_{re} = 2 \times 10^{-4}$ ,  $h_{oc} = 25 \times 10^{-6} \Omega$ ,  $h_{fe} = 50$ . (08 Marks)  
 c. List the advantages of negative feedback amplifier. Derive expressions for  $Z_{if}$  and  $Z_{of}$  for voltage series feedback amplifier. (08 Marks)
- 6 a. Explain the working of a class B push pull amplifier. Prove that the maximum efficiency is 78.5%. (10 Marks)  
 b. A single transistor amplifier with transformer coupled load produces harmonic amplitudes in the output as  $B_0 = 1.5$  mA,  $B_1 = 120$  mA,  $B_2 = 10$  mA,  $B_3 = 4$  mA,  $B_4 = 2$  mA,  $B_5 = 1$  mA. i) Determine the percentage total harmonic distortion  
 ii) Assume second identical transistor is used along with suitable transformer to provide push pull operation. Using the above harmonic amplitudes, determine the new total harmonic distortion. (10 Marks)
- 7 a. Explain with the help of a circuit diagram, the working of an RC phase shift oscillator. (08 Marks)  
 b. With the help of Barkhausen criterion, explain the working of a BJT crystal oscillator. (08 Marks)  
 Calculate the frequency of a Wien Bridge oscillator circuit when  $R = 12$  k ohm and  $C = 2400$  pf. (04 Marks)
- 8 a. Determine  $Z_i$ ,  $Z_o$  and  $A_v$  for the circuit shown in Fig.Q8(a), if  $Y_{fs} = 3000 \mu S$  and  $Y_{os} = 50 \mu S$ . (06 Marks)

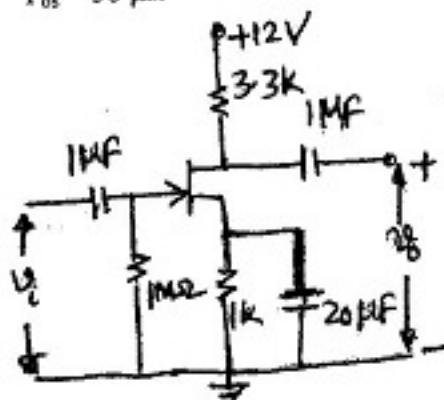


Fig.Q8(a)

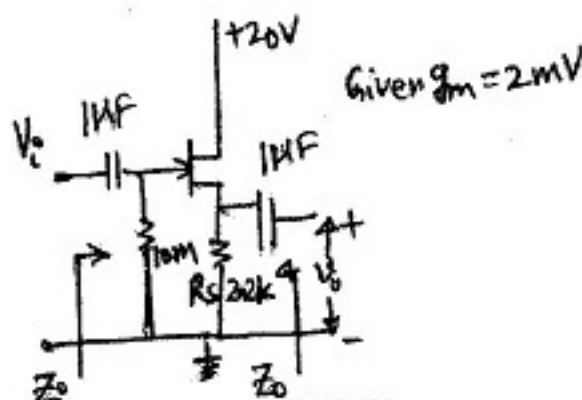


Fig.Q8(b)

- b. Determine  $Z_i$ ,  $Z_o$ , and  $A_v$  if  $r_d = 40$  kΩ for fig.Q8(b). (06 Marks)  
 c. With the help of circuits and equations, show different biasing arrangements for depletion type MOSFET. (08 Marks)

\*\*\*\*\*