

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EE35

Third Semester B.E. Degree Examination, Aug./Sept.2020 Digital System Design

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Convert the following equations into proper canonical form:
- $f(A, B, C) = A + ABC$ into standard SOP form.
 - $f(A, B, C) = A.(A + B + C)$ into standard POS form. (10 Marks)
- b. Reduce the following function using K-Map technique:
 $f(A, B, C, D, E) = \sum m(1, 4, 8, 10, 11, 20, 22, 24, 25, 26) + \sum d(0, 12, 16, 17)$ (10 Marks)

OR

- 2 a. Simplify the following using Quine-McCluskey method:
 $f(A, B, C, D) = \sum m(1, 2, 3, 5, 9, 12, 14, 15) + \sum d(4, 8, 11)$ (10 Marks)
- b. Design a logic circuit with inputs P, Q, R so that output Y is high whenever P is zero or whenever $Q = R = 1$. (10 Marks)

Module-2

- 3 a. i) Implement $f(A, B, C) = \sum m(1, 3, 5, 6)$ using 4:1 multiplexer.
ii) Implement $f(P, Q, R, S) = \sum m(0, 1, 3, 4, 8, 9, 15)$ using 8:1 multiplexer. (10 Marks)
- b. Explain the concept of look ahead adder and hence realize 3 bit parallel adder using Look ahead carry generator. (10 Marks)

OR

- 4 a. Implement full subtractor using 3:8 decoder. (10 Marks)
- b. Design 2-bit magnitude comparator using gates. (10 Marks)

Module-3

- 5 a. Explain the operation of gated S-R flipflop using NAND gates, with truth table. (10 Marks)
- b. Design synchronous MOD-6 counter using S-R flip flop. (10 Marks)

OR

- 6 a. With logic diagram, explain the working of master slave J-K flip flop along with waveforms. Explain about race around condition. (10 Marks)
- b. Design synchronous mod-3 counter using J-K flip flop. (10 Marks)

Module-4

- 7 a. Construct the transition table, state table and state diagram for the given synchronous sequential circuit. (10 Marks)

 


Fig.Q.7(a)

- b. Obtain transition table and excitation table for the given state diagram. (10 Marks)

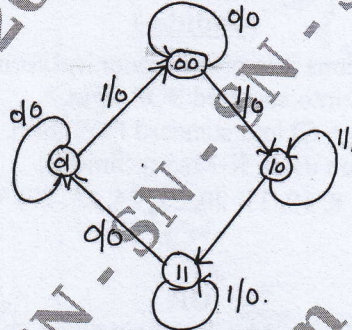


Fig.Q7(b)

OR

- 8 a. Construct the transition table, state table and state diagram for the Moore sequential circuit. (12 Marks)

 


Fig.Q.8(a)

- b. Compare Moore model and Mealy Model. (08 Marks)

Module-5

- 9 a. Write data flow description for full adder in both VHDL and verilog. (10 Marks)
 b. Compare VHDL and verilog. (10 Marks)

OR

- 10 a. Describe different operators in VHDL and verilog. (10 Marks)
 b. Briefly describe different styles of descriptions in VHDL. (10 Marks)
