

CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

15EE35

Third Semester B.E. Degree Examination, Dec.2017/Jan.2018 Digital System Design

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. With basic block diagram, explain the combinational logic circuit. (04 Marks)
b. Reduce the following function using K-map technique and implement using basic gates
i) $f(P, Q, R, S) = \sum m(0, 1, 4, 8, 9, 10) + d(2, 11)$
ii) $f(A, B, C, D) = \pi M(0, 2, 4, 10, 11, 14, 15)$ (12 Marks)

OR

- 2 a. Simplify using the Quine-Mcclusky minimization technique.
 $Y = f(a, b, c, d) = \sum m(0, 2, 8, 10)$ (08 Marks)
b. Simplify the given function using MEV technique.
 $f(a, b, c, d) = \sum(2, 3, 4, 5, 13, 15) + \sum d(8, 9, 10, 11)$. (08 Marks)

Module-2

- 3 a. With the aid of general structure, clearly distinguish between a decoder and encoder. (05 Marks)
b. Implement following multiple output function using one 74LS138 and external gates.
 $F_1(A, B, C) = \sum m(1, 4, 5, 7)$
 $F_2(A, B, C) = \pi M(2, 3, 6, 7)$ (06 Marks)
c. Draw the interfacing diagram of ten keypad interface to a digital system using decimal to BCD encoder (IC 74LS147: Decimal to BCD priority encoder). (05 Marks)

OR

- 4 a. Design a full adder by constructing the truth table and simplify the output equations. (06 Marks)
b. Write a truth table for two-bit magnitude comparator. Write the Karnaugh map for each output of two bit magnitude comparator and the resulting equation. (10 Marks)

Module-3

- 5 a. What is the difference between a flip-flop and a latch? With logic diagram and truth table, explain the operation of gated SR latch. (08 Marks)
b. Explain the operation of Master slave JK Flip-flop along with its circuit diagram. (08 Marks)

OR

- 6 a. Explain the working principle of four bit binary ripple counter, with the help of a logic diagram, timing diagram and counting sequence. (10 Marks)
b. With logic diagram and counting sequence explain Mod – 4 ring counters. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.

Module-4

- 7 a. Distinguish between Moore and Mealy model with necessary block diagrams. (08 Marks)
- b. Give output function, transition table and state diagram by analyzing the sequential circuit shown in Fig. Q7(b). (08 Marks)

 


Fig. Q7(b)

OR

- 8 a. Write the basic recommended steps for the design of a clocked synchronous sequential circuit. (06 Marks)
- b. Design a synchronous counter using J-K flip flops to count the sequence 0, 1, 2, 4, 5, 6, 0, 2. Use state diagram and state table. (10 Marks)

Module-5

- 9 a. Explain brief history of HDL and structure of HDL module. (06 Marks)
- b. List the classification of VHDL data types. Compare the VHDL data types and Verilog data types. (10 Marks)

OR

- 10 a. Explain signal declaration and signal assignment statements with relevant example. (06 Marks)
- b. Write a data flow description VHDL for a system that has three 1-bit inputs a(1), a(2) and a(3) one 1-bit output b. The least significant bit is a(1) ; and b is 1, only when (a(1) a(2) a(3)) = 1, 3, 6 or 7 (all in decimal) otherwise b is 0. Derive a minimized Boolean function of the system and write the data flow description. (10 Marks)
