

CBCS Scheme

USN

| | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|

15EE32

Third Semester B.E. Degree Examination, Dec.2017/Jan.2018

Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Distinguish between i) active and passive elements ii) ideal and practical sources. (04 Marks)
 b. Determine the currents i_1 , i_2 and i_3 in the circuit of Fig.Q1(b), using Mesh current method. (06 Marks)

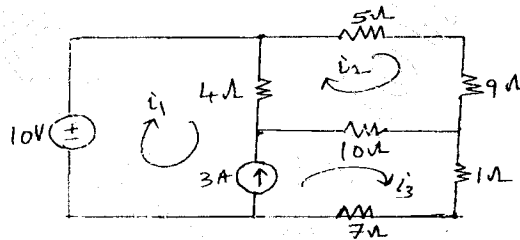


Fig.Q1(b)

- c. Find the node voltages for the circuit of Fig.Q1(c) using nodal analysis. (06 Marks)

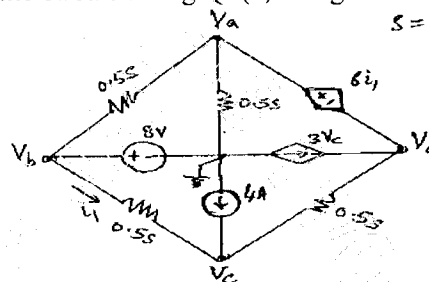


Fig.Q1(c)

OR

- 2 a. Find the equivalent resistance across a – b, of the circuit, of Fig.Q2(a) using delta –star conversion. (04 Marks)

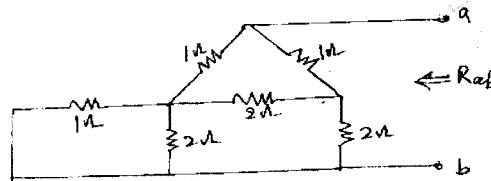


Fig.Q2(a)

- b. A series resonance circuit has $R = 10\Omega$, $L = 5\text{mH}$, and $C = 20\mu\text{F}$. Find the following :
 i) Resonant frequency ii) Q – factor and iii) Current at resonance condition, if the applied voltage is 100V. Hence derive the expressions for the same. (08 Marks)
 c. Draw the dual of the network shown in Fig.Q2(c). (04 Marks)

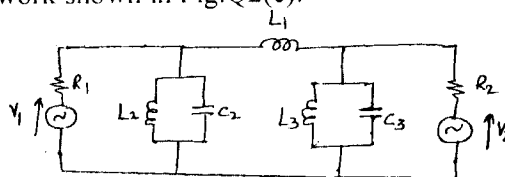


Fig.Q2(c)

1. On consolidation your answers, invariably draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appear to evaluator and/or questions written e.g. 1, 2, 3, etc. will be treated as malpractice.

Module-2

- 3 a. State and explain maximum power transfer theorem for DC circuit [resistive load]. (06 Marks)
 b. Find the Thevenin's and Norton's equivalent circuit for the network shown in Fig.Q3(b), as seen from the terminals a – b. (10 Marks)

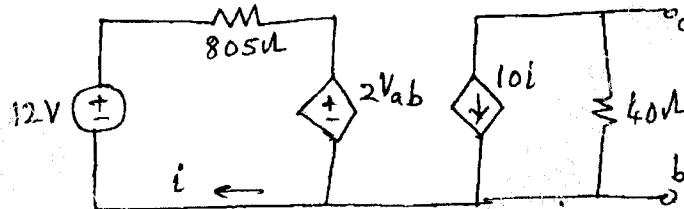


Fig.Q3(b)

OR

- 4 a. State and prove reciprocity theorem. (06 Marks)
 b. Using super position theorem, find the current I in the network shown in Fig.Q4(b). (10 Marks)

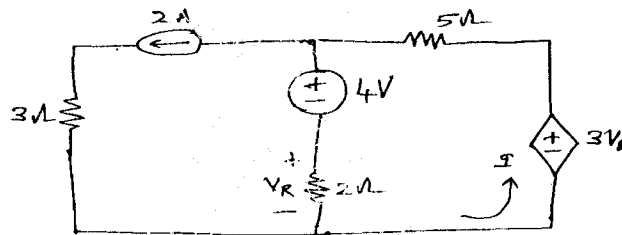


Fig.Q4(b)

Module-3

- 5 a. What are initial conditions and their use in network analysis? (04 Marks)
 b. For the network elements R, L and C, write the equivalent circuits :
 i) At $t = 0^+$ [initial condition]
 ii) At $t = \infty$ [Final condition]. (06 Marks)
 c. In the network shown in Fig.Q5(c), the switch K is closed at $t = 0$ with the capacitor uncharged. Find the values for i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$. (06 Marks)

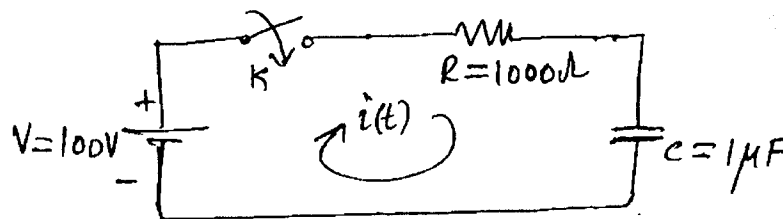


Fig.5Q(c)

OR

- 6 a. In the network of Fig.Q6(a), the switch K is changed from position a to b at $t = 0$. Solve for i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$. Assume steady state condition for K in position 'a'. (08 Marks)

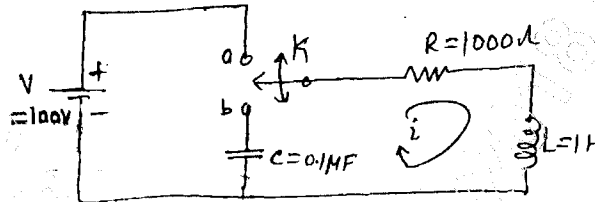


Fig.Q6(a)

- b. The network shown in Fig.Q6(b), has the switch k opened at $t = 0$. Solve for V , $\frac{dV}{dt}$ and $\frac{d^2V}{dt^2}$ at $t = 0^+$. (08 Marks)

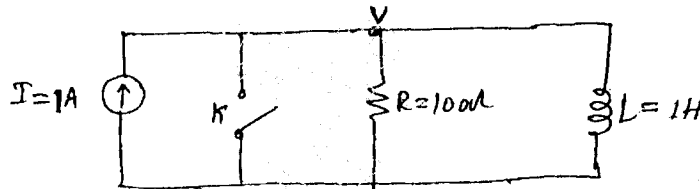


Fig.Q6(b)

Module-4

- 7 a. Obtain the Laplace transform of:
 i) Ramp function $t u(t)$
 ii) Exponential function $e^{-at} u(t)$
 iii) Sinusoidal function $\sin \omega t u(t)$. (06 Marks)
- b. Find the Laplace transform of
 i) $V(t) = 4s(t - 2) - 3t u(t)$ (04 Marks)
 ii) $V(t) = u(t) u(t - 2)$.
- c. In a series RLC circuit, the capacitor is initially charged to voltage $V_0 = 1V$, with the switch K open. Find the circuit $i(t)$ if the switch K is closed at $t = 0$, using Laplace transform method. Refer Fig.Q7(c). (06 Marks)

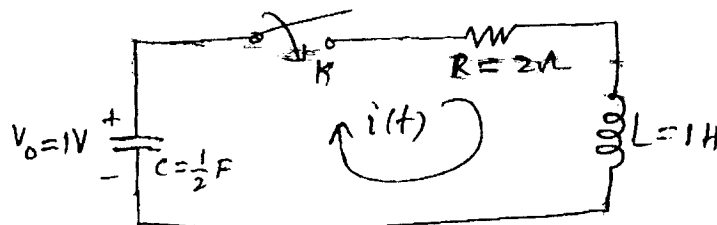


Fig.Q7(c)

OR

- 8 a. State and prove final value theorem. (06 Marks)
 b. Determine the initial value $f(0)$ and final value $f(\infty)$ for the function given by :

$$f(s) = \frac{5s^2 + 10}{2s[s^2 + 3s + 5]}$$

(04 Marks)

- c. Find the Laplace transforms of the following waveforms (Refer Fig.Q8(c)). (06 Marks)

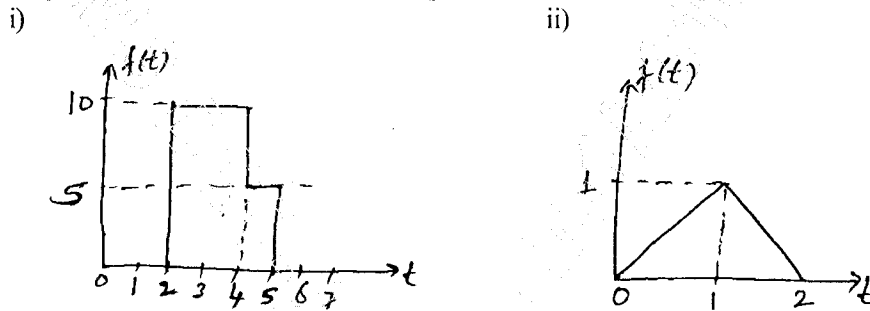


Fig.Q8(c)

Module-5

- 9 a. Define y-parameters and T-parameters of a two – port network. Write the conditions for symmetry and reciprocity. (04 Marks)
 b. Obtain y-parameters in terms of T-parameters. (06 Marks)
 c. Find y-parameters for the network shown in Fig.Q9(c). (06 Marks)

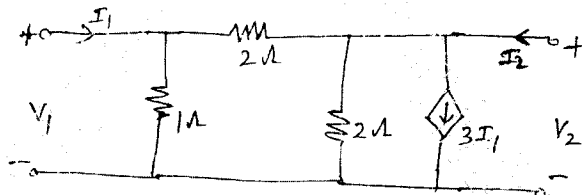


Fig.Q9(c)

OR

- 10 a. Find an expression for driving point impedance $z(s)$ of the R-C ladder network shown in Fig.Q10(a), Also draw the pole-zero diagram. (08 Marks)

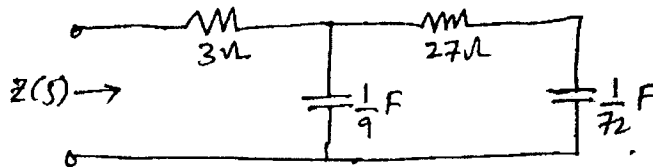


Fig.Q10(a)

- b. Find the effective voltage, effective current and the average power supplied to a passive network if the applied voltage, $V = 200 + 100 \cos [500t + 30^\circ] + 75 \cos [1500t + 60^\circ]$, volts and the resulting current is, $i = 3.53 \cos [500t + 75^\circ] + 3.55 \cos [1500t + 78.45^\circ]$, Amps. (08 Marks)
