

USN

--	--	--	--	--	--	--	--	--	--

10EE35

**Third Semester B.E. Degree Examination, June/July 2017**  
**Electrical and Electronic Measurements and**  
**Instrumentation**

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, selecting  
at least TWO questions from each part.**

**PART – A**

- 1 a. Derive the expression for the measurement of unknown resistance using Kelvin's double bridge. How the effect of connecting lead resistance is eliminated in this arrangement? (10 Marks)  
 b. The expression for the mean torque of an electro dynamometer type wattmeter may be written as :  $T \propto M^p E^q Z^t$ , where  $M$  = mutual inductance between fixed and moving coils,  $E$  = applied voltage and  $Z$  = impedance of the load circuit. determine the values of  $p$ ,  $q$  and  $t$  after deriving the dimensions of  $T$ ,  $M$ ,  $E$  and  $Z$ . (10 Marks)
- 2 a. Obtain the balance equation for Maxwell's inductance–capacitance bridge used for measurement of unknown inductance. Draw the phasor diagram at balance condition. (10 Marks)  
 b. The four arms of a bridge are :  
 Arm ab : an imperfect capacitor  $C_1$  with an equivalent series resistance of  $r_1$   
 Arm bc : a non inductive resistance  $R_3$   
 Arm cd : a non inductive resistance  $R_4$   
 Arm da : an imperfect capacitor  $C_2$  with an equivalent series resistance of  $r_2$  in series with a resistance  $R_2$ .  
 A supply of 450 Hz is given between terminal a and c and the detector is connected between b and d. At balance  $R_2 = 4.8\Omega$ ,  $R_3 = 200\Omega$ ,  $R_4 = 2850\Omega$ ,  $c_2 = 0.5\mu F$ ,  $r_2 = 0.4\Omega$ . Calculate the value of  $c_1$  and  $r_1$  and also the dissipating factor of this capacitor. (10 Marks)
- 3 a. Derive an expression for ratio and phase angle errors of C.T. with neat sketch. (10 Marks)  
 b. A CT has turns ratio 1 : 399 and is rated as 2000/5 A. The core loss component is 3A and magnetizing component is 8A, under full load conditions. Find the phase and ratio errors under full load conditions, if secondary circuit pf is 0.8 leading. (10 Marks)
- 4 a. Explain with the help of neat sketch, the construction, theory and working principle of an energy meter. (10 Marks)  
 b. With neat phasor diagram, explain the measurement of real power in 3 $\phi$  circuits. (08 Marks)  
 c. What is creeping? (02 Marks)

**PART – B**

- 5 a. Explain with neat figure, Weston frequency meter. (10 Marks)  
 b. Explain with block diagram the true RMS voltmeter. (08 Marks)  
 c. What is Q meter? (02 Marks)
- 6 a. Explain with block diagram, the working of dual trace oscilloscope. (10 Marks)  
 b. Explain with block diagram, the working of digital storage oscilloscope. (10 Marks)

- 7** a. What is transducer? Briefly explain the procedure for selecting a transducer. **(06 Marks)**  
b. Explain the principle of operating of LVDT in translating a linear motion into an electrical signal. **(08 Marks)**  
c. Briefly explain photo conductive and photo voltaic cells. **(06 Marks)**
- 8** a. Explain with block diagram, the essential functional operations of a digital data acquisition system. Compare the digital and analog forms of data acquisition systems. **(08 Marks)**  
b. Explain the working and application of an x-y recorder. **(08 Marks)**  
c. Write a note on display devices. **(04 Marks)**

\* \* \* \* \*