

Third Semester B.E. Degree Examination, Dec. 07 / Jan. 08
Electronic Circuits

Time: 3 hrs.

Max. Marks:100

Note : Answer any FIVE full questions.

- 1 a. Discuss voltage doubler circuit. (05 Marks)
 b. Define regulation and derive equation for a fullwave circuit. (07 Marks)
 c. In the Fig.1(c) the diodes are ideal. Write the transfer characteristic equations (V_o , V_s , V_i). Plot V_o , V_s , V_i . Indicate all intercepts, slopes and voltage levels.

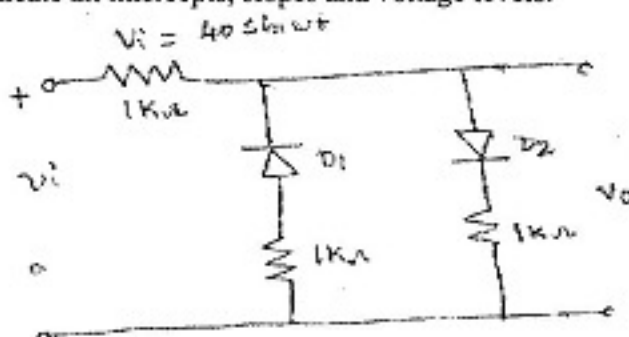


Fig.1(c)

Repeat for the case when $V_r = 1$ V $V_i = 40 \sin \omega t$ (08 Marks)

- 2 a. Define three stability factors. For a self bias circuit derive the expression for S_v and S_β . (10 Marks)
 b. For the circuit shown in Fig.2(b) $V_{cc} = 24$ V, $R_c = 10$ k Ω , $R_e = 270$ Ω , $\beta = 45$. Silicon transistor is used under operating condition $V_{ce} = 5$ V find
 i) R ii) Stability factor S

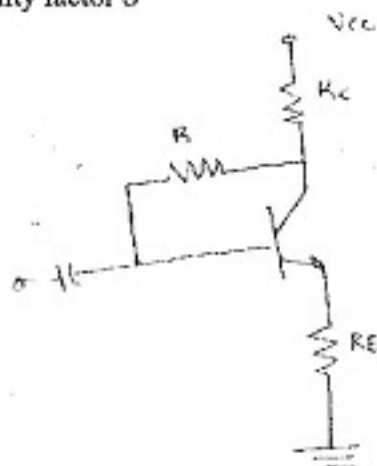


Fig.2(b)

- c. Briefly discuss how do you provide operating point stability using compensation technique. (04 Marks)
- 3 a. Using small signal low frequency hybrid model for the CE amplifier with a load of Z_L and source resistance R_S derive expression for A_t , A_v , Z_i and Z_o . (10 Marks)
 b. For a transistor amplifier in CB configuration find A_t , A_v , Z_{in} , Z_{out} , A_{VS} and A_{IS} given that $h_{ib} = 22$ Ω , $h_{ob} = 2.9 \times 10^{-4}$, $h_{fb} = -0.98$, $1/h_{ob} = 2.04$ m Ω . (06 Marks)
 c. State and Prove Miller's theorem. (04 Marks)

- 4 a. Draw small signal high frequency CE model for transistor and explain the significance of even component in the model and prove that $h_{fe} = g_m r_b' e$. (08 Marks)
 b. Discuss the various types of distortion in amplifier. (06 Marks)
 c. With suitable RC circuit calculate low frequency response of an amplifier. (06 Marks)
- 5 a. Explain the advantages of negative feed back circuit. (06 Marks)
 b. Draw and explain different feed back amplifier topologies. (08 Marks)
 c. An amplifier with open loop voltage gain $A_V = 1000 \pm 100$ is available. It is necessary to have an amplifier whose voltage gain varies by no more than $\pm 0.1\%$.
 i) Find the reverse transmission factor β of the feed back network
 ii) Find gain with feedback. (06 Marks)
- 6 a. Show that the maximum conversion efficiency of class-B push pull amplifier is 78.5%. (06 Marks)
 b. Discuss why even harmonics are not present in push-pull amplifier. (06 Marks)
 c. Explain :
 i) Input bias current compensation in OPAMP.
 ii) Input offset voltage compensation for inverting and non inverting configuration. (08 Marks)
- a. Design a single pole LPF with a cut off frequency of 10 kHz and mid band gain of 1.5. Draw the circuit diagram. (05 Marks)
 b. With a neat diagram and relevant waveforms explain the following OPAMP circuits :
 i) Peak detector and clamper
 ii) Schmitt trigger
 iii) Instrumentation amplifier (10 Marks)
 c. Explain sample and hold act. (05 Marks)
- a. With a neat diagram and relevant waveforms, explain the working of an astable modulator circuit using 555 timer. Obtain the expression for the time period. (12 Marks)
 b. Discuss the specifications of a DAC circuit. (08 Marks)