

Third Semester B.E. Degree Examination, Dec.08 / Jan.09
Electronic Circuits

Time: 3 hrs.

Max. Marks:100

Note : Answer any FIVE full questions.

- 1 a. Define clipping circuit. Mention a few applications. (04 Marks)
 b. For the clipping circuit shown in figure Q1 (b), sketch the output and transfer characteristics. (06 Marks)

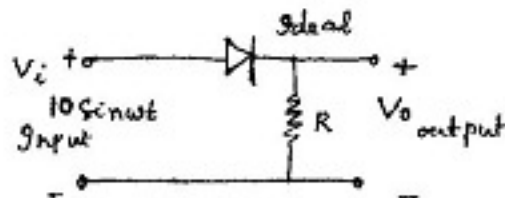
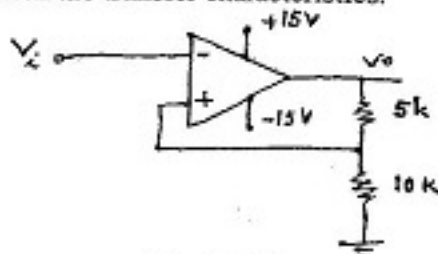


Fig. Q1 (b)

- c. Explain the working of C-filter and derive expression for the ripple factor for a full wave rectifier fitted with C-filter. (10 Marks)
- 2 a. What is biasing of a transistor and what are its requirements? (04 Marks)
 b. Explain 'emitter bias'. (06 Marks)
 c. Derive expression for voltage gain (A_v) and current gain (A_i) of an amplifier circuit using BJT in CE configuration using approximated hybrid parameter model. (10 Marks)
- 3 a. Explain the working of single stage R-C coupled amplifier using BJT. (12 Marks)
 b. A three stage amplifier has these power gains $G_1 = 10$, $G_2 = 100$ and $G_3 = 1000$. What is the total power gain? What is the Bel power gain of each stage? What is the bel power gain of the 3 stage amplifier? (08 Marks)
- 4 a. Explain the concept of 'feed back' in amplifiers. (08 Marks)
 b. Explain the working of any one type of feedback amplifier and list its characteristics. (12 Marks)
- 5 a. What are power amplifiers and how do they differ from small signal voltage amplifier. (04 Marks)
 b. Explain the working of a push-pull amplifier and derive expression for its efficiency. (12 Marks)
 c. Define class A and Class B type of amplification. (04 Marks)
- 6 a. For an operational amplifier define the following parameters: (12 Marks)
 i) Slew rate.
 ii) CMRR (Common Mode Rejection Ratio)
 iii) Input offset voltage.
 iv) Output offset voltage
 v) Open loop voltage gain
 vi) Input bias current
- b. What are active filters? List the advantages of active filters over passive filters. (04 Marks)
- c. For the inverting mode Schmitt trigger shown in figure Q6 (c) calculate upper and lower threshold voltages and sketch the transfer characteristics. (04 Marks)

Fig. Q6 (c)
1 of 2

- 7 a. Explain the working of a 3-bit DAC using R-2R ladder network. (08 Marks)
 b. What are the specifications of a DAC? (04 Marks)
 c. Sketch the output V_o of the following comparator circuits. (08 Marks)

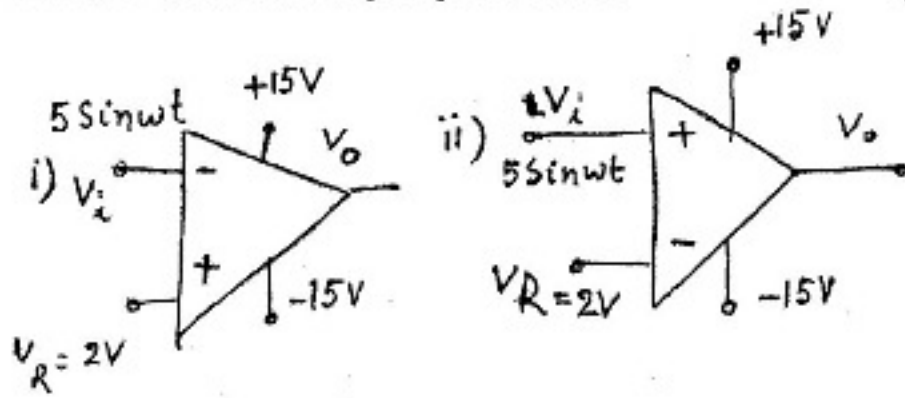


Fig. Q7 (c)

- 8 a. Give pin configuration of timer IC 555. (05 Marks)
 b. Explain the working of astable multivibrator using timer IC 555 and derive expression for time period (T)/ frequency of oscillation. (15 Marks)
