

--	--	--	--	--	--	--	--	--	--

NEW SCHEME

Third Semester B.E. Degree Examination, July 2007
EC/TE/EE/BM/ML/IT/CS/IS
Electronic Circuits

Time: 3 hrs.]

[Max. Marks:100

Note : Answer any FIVE full questions.

- 1 a. Define diffusion capacitance. Derive an expression for the same. (05 Marks)
 b. Draw the piece wise linear V-I characteristics of a P-N junction diode. Give the circuit model for the ON state and OFF state. (05 Marks)
 c. The input voltage V_i to the two-level clipper circuit as shown in fig.1(c) varies linearly from 0 to 150 V. Sketch the output voltage V_o to the time scale. Assume diodes as ideal. (10 Marks)

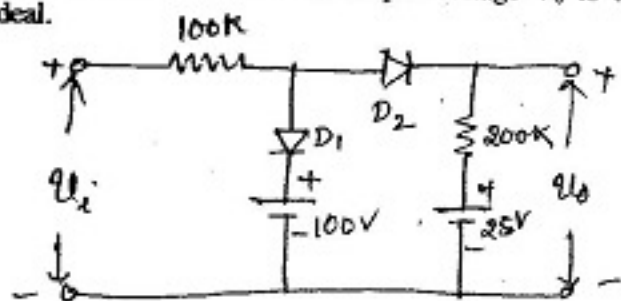


Fig.1(c)

- 2 a. With necessary circuit and waveforms, explain a bridge rectifier circuit with capacitor filter. Derive an expression for the ripple factor. (10 Marks)
 b. Design a full wave rectifier filter to meet the following requirements. DC output voltage = 15 V, load resistance = 1 K, rms ripple voltage on capacitor < 1 % of dc output voltage. The AC supply voltage is 230 V at 50 Hz. (10 Marks)
- 3 a. What is the need for bias compensation? Explain the compensation techniques used for V_{BE} and I_{CBO} . (10 Marks)
 b. The circuit shown in fig.3(b) uses silicon transistor with $\beta = 45$, $V_{CC} = 24$ V, $R_C = 10$ K, $R = 10$ K, $R_E = 0.27$ K. If $V_{CE} = 5$ V under quiescent conditions, find the value of 'R' and the stability factor $S(I_{C0})$. (06 Marks)

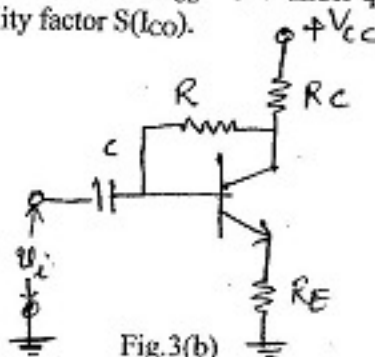


Fig.3(b)

- c. What do you mean by thermal runaway of a transistor? Explain. (04 Marks)

(04 Marks)
 Contd.... 2

- a. Obtain an expression in terms of 'h' parameters for a transistor as a two-port network. Using the above developed equations obtain the hybrid model of CE, CC and CB configurations. (08 Marks)
- b. State and explain Millers theorem. (04 Marks)
- c. A transistor is connected as a common emitter amplifier driving a load of $10\text{ k}\Omega$. It is supplied by a source of $1\text{ k}\Omega$ internal resistance. The 'h' parameters are $h_{ie} = 1.1\text{ k}\Omega$, $h_{fe} = 50$, $h_{re} = 2.5 \times 10^{-4}$, $h_{oe} = \frac{1}{40\text{ k}\Omega}$. Find: i) Current gain ii) Voltage gain iii) Input impedance iv) Output impedance. (08 Marks)
- a. Derive an expression for: i) Input conductance ($g_{b'e}$) ii) Output conductance (g_{cc}) for a transistor at high frequency. (06 Marks)
- b. Give the classification of multistage amplifier. Explain the various distortions in amplifiers. (08 Marks)
- c. Discuss the general characteristics of a negative feedback amplifier. (06 Marks)
- a. Derive an expression for input and output resistance of a voltage shunt feedback amplifier. (06 Marks)
- b. Explain the different types of power amplifiers. (08 Marks)
- c. An ideal class B- pushpull amplifier with input and output transformers, has $V_{CC} = 20\text{ V}$, $N_2 = 2N_1$ and $R_L = 10\ \Omega$. The transistors have $h_{FE} = 20$. Let the input be sinusoidal. For the maximum output signal $V_m = V_{cc}$. Determine: i) The output signal power ii) Collector power dissipation iii) Conversion efficiency. (06 Marks)
- a. Obtain an expression for the closed loop gain of a non-inverting amplifier. (07 Marks)
- b. With necessary sketch and characteristic curves explain the operation of a Schmitt trigger. (08 Marks)
- c. What do you mean by precision rectifiers? Explain full wave precision rectifier. (05 Marks)
- a. Explain the working of SAR ADC. (06 Marks)
- b. Explain the working R - 2R ladder DAC. (07 Marks)
- c. Explain the applications of astable multivibrator as:
 i) Square wave generator ii) To achieve variable duty cycle control. (07 Marks)