



- (c) State and prove Millers theorem. (5 Marks)
4. (a) Derive expressions for transistor input conductance  $g_{b'e}$  and feedback conductance  $g_{b'c}$  (10 Marks)
- (b) Explain different types of distortions in amplifiers. (5 Marks)
- (c) How are amplifiers classified? Explain them briefly. (5 Marks)
5. (a) Discuss the general characteristics of negative feedback amplifiers. (9 Marks)
- (b) Derive an expression for the input resistance of a voltage series feedback topology. (5 Marks)
- (c) An amplifier without feedback gives a fundamental output of 36V with 7 percent second harmonic distortion when the input voltage is 0.028V.
- i) If 1.2 percent of the output is fed back into the input in a negative voltage series feedback circuit, what is the output voltage?
- ii) If the fundamental output is maintained at 36V but the second harmonic distortion is reduced to 1 percent, what is the input voltage? (6 Marks)
6. (a) Discuss how rectification may take place in a power amplifier. (5 Marks)
- (b) Show that the maximum conversion efficiency of the idealized class B push pull amplifier is 78.5 %. (9 Marks)
- (c) Calculate the peak power dissipated in each transistor of a class B pushpull power amplifier if  $V_{CC} = 15V$  and  $R'_L = 5\Omega$ . (6 Marks)
7. (a) Explain how to measure the differential input resistance  $R_i$  of an op.amp. (7 Marks)
- (b) What are the advantages of active filters over passive ones? Design a first order high pass filter at a cutoff frequency of 400Hz and a pass band gain of 2. (7 Marks)
- (c) Draw an op-amp Schmitt trigger circuit and explain its operation. (6 Marks)
8. (a) Draw a 4-bit D/A converter using R/2R resistors and explain its working. (7 Marks)
- (b) Draw and explain the working of a sample and hold circuit. (5 Marks)
- (c) Draw the circuit diagram of an A.M.V. using 555 timer and explain its operation. (8 Marks)

\*\* \* \*\*