

USN

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, Dec.08/Jan.09
Logic Design

Time: 3 hrs.

Max. Marks:100

- Note:1. Answer any FIVE full questions, choosing at least two questions from each part A & B.**
2. Missing data be suitably assumed.

Part A

- 1 a. Convert the given boolean function $f(x,y,z)=[x+\bar{x}\bar{z}(y+\bar{z})]$ into maxterm canonical formula and hence highlight the importance of canonical formula. (05 Marks)
- b. Distinguish the prime implicants and essential prime implicants. Determine the same of the function $f(w,x,y,z)=\sum m(0,1,4,5,9,11,13,15)$ using K-map and hence the minimal sum expression. (05 Marks)
- c. Design a combinational logic circuit, which converts BCD code into Excess-3 code and draw the circuit diagram. (10 Marks)
- 2 a. Using Quine-Mcluskey method and prime implicant reduction table, obtain the minimal sum expression for the Boolean function $f(w,x,y,z)=\sum m(1,4,6,7,8,9,10,11,15)$. (12 Marks)
- b. Obtain the minimal product of the following Boolean functions using VEM technique:
 $f(w,x,y,z)=\sum m(1,5,7,10,11)+dc(2,3,6,13)$ (08 Marks)
- 3 a. Realize the following functions expressed in maxterm canonical form in two possible ways using 3-8 line and decoder:
 $f_1(x_2,x_1,x_0)=\pi M(1,2,6,7)$
 $f_2(x_2,x_1,x_0)=\pi M(1,3,6,7)$ (10 Marks)
- b. What are the problems associated with the basic encoder? Explain, how can these problems be overcome by priority encoder, considering 8 input lines. (10 Marks)
- 4 a. Implement the function $f(w,x,y,z)=\sum m(0,1,5,6,7,9,10,15)$ using a 4 : 1 MUX with w, x as select lines: (08 Marks)
- b. The 1-bit comparator had 3 outputs corresponding to $x > y$, $x = y$ and $x < y$. It is possible to code these three outputs using two bits S_1S_0 such as $S_1, S_0 = 00, 10, 01$ for $x = y, x > y$ and $x < y$ respectively. This implies that only two-output lines occur from each 1-bit comparator. However at the output of the last 1-bit comparator, an additional network must be designed to convert the end results back to three outputs. Design such a 1-bit comparator as well as the output converter network. (12 Marks)

Part B

- 5 a. What is a Flip Flop? Discuss the working principle of SR Flip Flop with its truth table. Also highlight the role of SR Flip Flop in switch debouncer circuit. (08 Marks)
- b. With neat schematic diagram of master slave JK-FF, discuss its operation. Mention the advantages of JK-FF over master-slave SR-flip-flop. (12 Marks)

- 6 a. Design a 4-bit universal shift register using positive edge triggered D flip-flops to operate as shown in the table below Q6 (a) (12 Marks)

Select line	Data line selected	Register operation
S_0 S_1		
0 0	I_0	HOLD
0 1	I_1	Shift RIGHT
1 0	I_2	Shift LEFT
1 1	I_3	Parallel load

Table Q6 (a)

- b. Explain the working principle of a mod-8 binary ripple counter, configured using positive edge triggered T-FF. Also draw the timing diagram. (08 Marks)
- 7 a. Distinguish between Moore and Mealy model with necessary block diagrams. (08 Marks)
- b. Give output function, excitation table and state transition diagram by analyzing the sequential circuit shown in figure Q7 (b) (12 Marks)

 


Fig. Q7 (b)

- 8 a. Construct Moore and Mealy state diagram that will detect input sequence 10110, when input pattern is detected, z is asserted high. Give state diagrams for each state. (10 Marks)
- b. Design a cyclic mod 6 synchronous binary counter using JK flip-flop. Give the state diagram, transition table and excitation table. (10 Marks)