

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, Dec.09/Jan.10
Logic Design

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting at least TWO questions from each part.

PART – A

- 1 a. Show that $y = f(ABCD) = \sum (0, 2, 5, 7, 8, 10, 13, 15)$ is the complement of $y = f(ABCD) = \pi(1, 3, 4, 6, 9, 11, 12, 14)$. Illustrate your answer using Karnaugh map to show the complement nature of the two equations. Realize both the functions using 7486 IC chip [Exclusive OR gates] only. (12 Marks)
- b. Design a logic circuit that controls the passage of a signal 'A' according to the following requirement.
- Output 'X' will equal 'A' when control inputs B and C are the same.
 - 'X' will remain 'HIGH' when B and C are different
- Implement the circuit using suitable gates. (08 Marks)

- 2 a. Simplify the following expression using Quine- McClusky technique. Implement the simplified circuit using basic gates: $f(ABCD) = \sum (1, 3, 4, 5, 6, 9, 11, 12, 13, 14)$. (12 Marks)
- b. Simplify the following Boolean expression using VEM technique. [3 variable map].
 $f(ABCD) = \sum m(0, 4, 5, 6, 13, 14, 15) + dc(2, 7, 8, 9)$

A	B	C	D	f	A	B	C	D	f
0	0	0	0	1	1	0	0	0	ϕ
0	0	0	1	0	1	0	0	1	ϕ
0	0	1	0	ϕ	1	0	1	0	0
0	0	1	1	0	1	0	1	1	0
0	1	0	0	1	1	1	0	0	0
0	1	0	1	1	1	1	0	1	1
0	1	1	0	1	1	1	1	0	1
0	1	1	1	ϕ	1	1	1	1	1

ϕ = don't care term.

(08 Marks)

- 3 a. Design a logic circuit using a 3 to 8 logic decoder that has active low data inputs, an active HIGH enable and active low data outputs. Use such a decoder to realize the full adder circuit. (08 Marks)
- b. Design a suitable BCD adder circuit using 74LS83 and a provision has to be made for self correction in case if the sum is not a valid BCD number format. (12 Marks)
- 4 a. Implement the following Boolean function using 4 :1 MUX
 $y(ABCD) = \sum m(0, 1, 2, 4, 6, 9, 12, 14)$. (10 Marks)
- b. Design a circuit that accepts 2 unsigned 4 bit numbers and provides 3 outputs. The inputs are $A_3 A_2 A_1 A_0$ and $B_3 B_2 B_1 B_0$. Outputs are $A = B$, $A > B$ and $A < B$. Draw the logic diagram. (10 Marks)

Important Note: 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42+8=50, will be treated as malpractice.

PART - B

- 5 a. Explain the following:
- Switch debouncing and its elimination
 - Race around problem and its elimination.
- (14 Marks)
- b. Obtain the characteristic equation for the following flip flops:
- JK flip flop
 - SR flip flop.
- (06 Marks)
- 6 a. With the help of a diagram, explain the following with respect to shift register:
- Parallel in and serial out
 - Ring counter and twisted ring counter.
- (08 Marks)
- b. Design a Mod - 5 synchronous counter using JK flip flop. (12 Marks)
- 7 a. With a suitable example, explain Mealy and Moore model in a sequential circuit analysis. (10 Marks)
- b. A sequential circuit has one input and one output. The state diagram is as shown in Fig.7(b). Design a sequential circuit with 'T' flip flop. (10 Marks)

 


Fig.7(b).

- 8 a. Analyse the following sequential circuit shown in Fig.8(a) and obtain:
- Flip flop input and output equations.
 - Transition equation
 - Transition table
 - State table
 - Draw the state diagram.
- (12 Marks)

 


Fig.8(a).

- b. With a suitable example and appropriate state diagram, explain how to recognize a particular sequence. Ex: 1011. (Any sequence can be assumed). (08 Marks)
