

USN

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, January/February 2004  
Common to BM/EC/EE/TE/ML/IT/CS/IS  
**Logic Design**

Time: 3 hrs.]

[Max.Marks : 100

Note: 1. Answer any FIVE full questions.  
2. All questions carry EQUAL marks.

- Explain the principle of duality. (4 Marks)
  - Mention two categories of Boolean expressions based on their structure. Write these forms for any give three - variable function  $T(x, y, z)$ . (8 Marks)
  - Give the Shanon's expansion theorem. (4 Marks)
  - Explain the exclusive-or-function. (4 Marks)
- Design an odd parity bit generator using gates for the decimal digits 0 to 9 represented in 84.21 BCD. Give the necessary truth table and draw the logic diagram. Explain. (8 Marks)
  - What code is used to label the row headings and column headings of a Karnaugh map and why? (4 Marks)
  - Using K-map obtain the minimal sum of products and the minimal product of sums form of the functon  $f(a, b, c, d) = \sum m(1, 2, 3, 5, 6, 7, 8, 13)$  (8 Marks)
- Mention one advantage and one disadvantage of the Quine-McCluskey method for obtaining the prime implicants of a given Boolean function. Obtain all the prime implicants of the function.  
 $f(v, w, x, y, z) = \sum m(4, 5, 9, 11, 12, 14, 15, 27, 30) + dc(1, 17, 25, 26, 31)$   
Use Quinne-McCluskey method. Do you have any essential prime implicants. (12 Marks)
  - In what way MEV-K-map differs from the conventional K-maps? Simplify the function  
 $f(a, b, c, d) = \sum m(2, 3, 4, 5, 13, 15) + dc(8, 9, 10, 11)$   
using a two variable MEV-K-map. (8 Marks)
- With the aid of a neat circuit diagram explain the operation of a 2-input TTL nand gate with totem output. (8 Marks)
  - Discuss how a resistor could be constructed using MOSFET. Give the resistor characteristics. (6 Marks)
  - Draw the NMOS as well as PMOS circuit diagrams to realise a NAND gate. Give the relevant truth tables. (6 Marks)
- Explain a 4 bit parallel adder with the carry look ahead scheme. Clearly indicate how this scheme improves the performance of the operation. (10 Marks)
  - With the aid of block diagrams clearly distinguish between a decoder and encoder. (4 Marks)
  - Give a 4-to-1 MUX implementation of the three variable function  
 $f = \sum m(1, 4, 5, 7)$  (6 Marks)


6. (a) Illustrate how a PLA can be used for combinational logic design with reference to the functions.

$$f_1(a, b, c) = \sum m(0, 1, 3, 4)$$

$$f_2(a, b, c) = \sum m(1, 2, 3, 4, 5)$$

Realize the same assuming, that a  $3 \times 4 \times 2$  PLA is available. (10 Marks)

 - (b) Give the details of a master slave S-R flip flop. Draw the logic diagram. Explain the flip flop action during the control signal. Also give the function table. (10 Marks)
7. (a) Draw the block diagram of a mod-7 twisted ring counter and explain its operation. Give the count sequence table and the decoding logic used to identify the various states. (10 Marks)
- (b) Construct the excitation table, transition table and state diagram for the Moore sequential circuit given below: (10 Marks)



8. Write notes on:
- 1 - bit comparator
  - Fan - in and Fan out
  - Integration levels of IC's
  - Binary full subtractor.

(4 × 5 = 20 Marks)

\*\* \* \*\*