

NEW SCHEME
------------

**Third Semester B.E. Degree Examination, July 2007**  
**CS / IS / EE / EC / IT / TC / BM / ML**  
**Logic Design**

Time: 3 hrs.]

[Max. Marks:100

Note : Answer any FIVE full questions.

- 1 a.** Using the theorems of Boolean algebra, simplify the following:
- $y_1 = D(\overline{A+B}) + \overline{B}(C+AD)$
  - $y_2 = \overline{AB} + ABC + A(\overline{B+AB})$
  - $y_3 = \overline{ABC} + \overline{ABC} + \overline{ABC} + \overline{ABC}$  (09 Marks)
- b.** Express the following expressions in canonical form:
- $y_1 = (A-B)(A+C)(B+\overline{C})$
  - $y_2 = AC + AB + BC$  (06 Marks)
- c.** Give the implementation of EXOR gate using minimum number of NAND gates only. (05 Marks)
- 2 a.**
- Express the following min term expression in POS form:  
 $y(A, B, C, D) = \Sigma m(1, 3, 5, 6, 7, 9, 10, 12, 15)$
  - Express the following max term expression in SOP form:  
 $y(A, B, C) = \Pi M(0, 3, 5, 6)$ . (06 Marks)
- b.**
- What are the advantage, disadvantages of K map?
  - Simplify the following function in SOP form using K Map:  
 $f(A, B, C, D) = \overline{ABC} + AD + BD + CD + AC$  (08 Marks)
- c.** Simplify the following function in POS form using K map:  
 $f(A, B, C, D) = \Pi M(0, 1, 2, 5, 8, 9, 10)$ . (03 Marks)
- d.** Simplify the following function in SOP form using K map:  
 $y(w, x, y, z) = \Sigma m(1, 2, 3, 5, 9, 12, 14, 15) + \Sigma d(4, 8, 11)$ . (03 Marks)
- 3 a.** Minimize the expression using Quine Mc Cluskey method.  
 $y(A, B, C, D) = \Sigma m(1, 2, 3, 5, 9, 12, 14, 15) + \Sigma d(4, 8, 11)$ . (10 Marks)
- b.** Simplify the following using VEM technique. Reduce 4 variables to 3 variables.  
 $y = \overline{ABCD} + \overline{ABCD} + \overline{ABCD} + \overline{ABCD} + \overline{ABCD} + \overline{ABCD} + \overline{ABCD} + \overline{ABCD}$  (05 Marks)
- c.** Realize a full adder using minimum number of 2 input NAND gates. Write the truth table, relevant expressions and logic diagram. (05 Marks)
- 4 a.** Define the following:
- Fan in and fan out
  - Noise margin
  - Propagation delay. (06 Marks)
- b.** Explain the operation of basic TTL NAND gate circuit with relevant diagram. (07 Marks)
- c.** Draw and explain the circuit of 2 input CMOS NOR gate. (07 Marks)

- 5 a. What is a magnitude comparator? Design a 2 bit digital comparator by writing the truth table, the relevant expression, and logic diagram. (10 Marks)
- b. Implement the following Boolean function using 8:1 MUX: (06 Marks)  
 $F(A, B, C, D) = \sum m(1, 2, 5, 9, 10, 14)$
- c. Write the truth table of the following flip flops: (04 Marks)  
 D, T, SR, JK.
- 6 a. Write the excitation table of SR flip flop. Design a synchronous MOD-6 counter using SR flip flop for the following count sequence 0, 1, 3, 2, 6, 4 and repeat. Write the transition table, logic diagram. (10 Marks)
- b. What is a look-ahead carry adder? Explain the circuit and operation of a 4 bit binary adder with look-ahead carry. (10 Marks)
- 7 a. Realize a 3 bit binary synchronous up counter using JK flip flop. Write the excitation table, transition table and logic diagram. Include preset, clear option. (10 Marks)
- b. Explain the different types of shift register. SISO, SIPO, PIPO, PISO with relevant circuit diagram. (10 Marks)
- 8 a. A combinational circuit is defined by the functions:  
 $F_1 = \sum m(3, 5, 7)$   
 $F_2 = \sum m(4, 5, 7)$   
 Implement the circuit with a PLA having 3 inputs, 3 product terms and 2 outputs. (08 Marks)
- b. A sequential network has one input and one output. The state diagram is shown in fig.8(b). Design the sequential circuit with T flip flop. (12 Marks)

 


Fig.8(b)