

NEW SCHEME

Third Semester B.E. Degree Examination, Dec. 06 / Jan. 07

EE / TC / EC / IT / BM / ML

Network Analysis

Time: 3 hrs.]

[Max. Marks:100

Note : Answer any FIVE full questions.

- 1 a. Derive expression for i) Y to Δ and ii) Δ to Y transformations. (10 Marks)
- b. In the circuit of Fig.1(b), find I through loop analysis

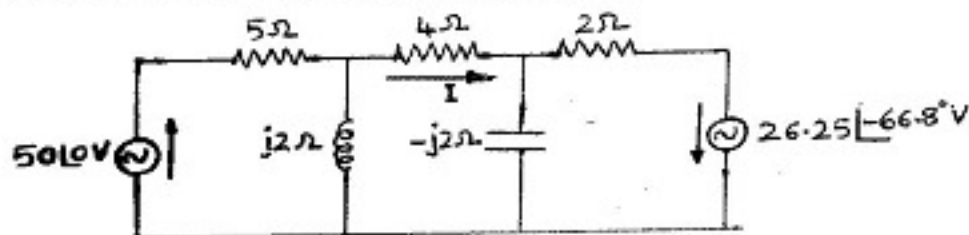


Fig.1(b)

(10 Marks)

- 2 a. Define with examples
i) Oriented graph ii) Tree iii) Fundamental cut set iv) Fundamental tie set (08 Marks)
- b. In the circuit of Fig.2(b) the ohmic values also represent the branch numbers. Form a tree using 4 Ω , 5 Ω , and 6 Ω branches and find the branch currents using cut set matrix.

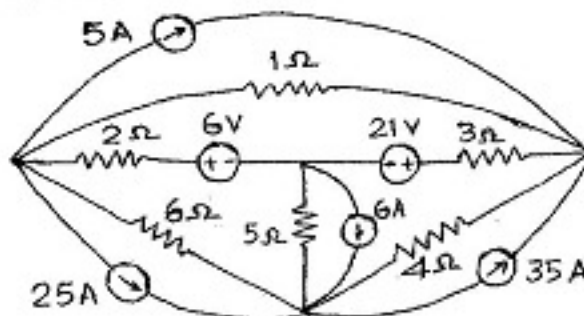


Fig.2(b)

(12 Marks)

- 3 a. State and prove maximum power transfer theorem for AC circuits. (08 Marks)
- b. In the circuit of Fig.3(b) obtain I by Thevenin's theorem.

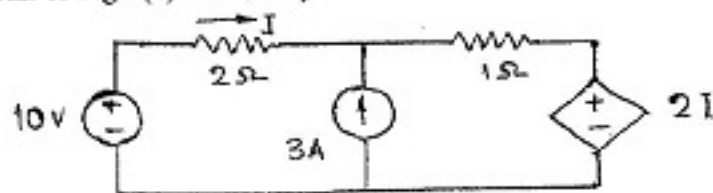


Fig.3(b)

(12 Marks)

- 4 a. Define i) Bandwidth ii) Selectivity. (08 Marks)
- Derive an expression for bandwidth.
- b. A coil is connected in series with a variable capacitor across $v(t) = 10 \cos 1000t$. The capacitor is varied and the current is maximum when $C = 10 \mu\text{F}$. When $C = 12.5 \mu\text{F}$, the current is 0.707 times the maximum value. Find L, R and Q of the coil. (12 Marks)

Contd.... 2

- 5 a. In the circuit of Fig.5(a) switch K is changed from 1 to 2 at $t = 0$, steady state having been attained in position 1. Find the values of i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0$. (10 Marks)
- b. In the circuit of Fig.5(b), switch K is kept open for a very long time. On closing K, after 10 ms, $V_c = 80$ V. Then the switch K is kept closed for a long time. When the switch is opened again, $V_c = 90$ V after half second. Calculate values of R and C. (10 Marks)

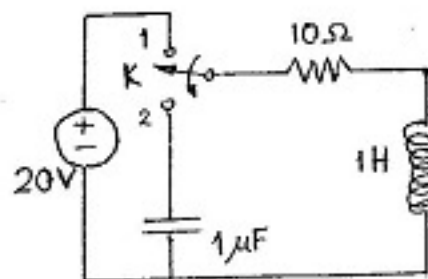


Fig.5(a)

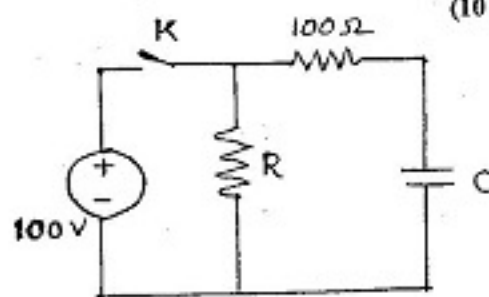


Fig.5(b)

- 6 a. In the circuit of Fig.6(a), the source voltage is $V(t) = 50 \sin 250t$. Using Laplace transforms, determine the current when switch K is closed at $t = 0$. (10 Marks)
- b. In the circuit of Fig.6(b), the switch is closed at $t = 0$. Derive an expression for $V(t)$ after the switch closes. (10 Marks)

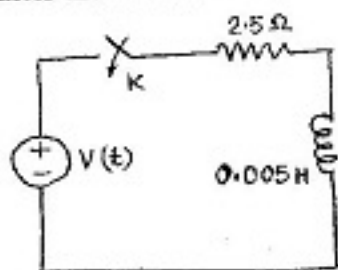


Fig.6(a)

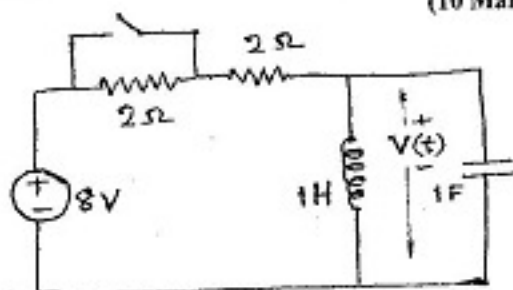


Fig.6(b)

- 7 a. Derive the Z-parameters in terms of Y parameters. (08 Marks)
- b. Find the Y-parameters for the circuit shown in Fig.7(b). Then use the parameter relationship to find the ABCD parameters.

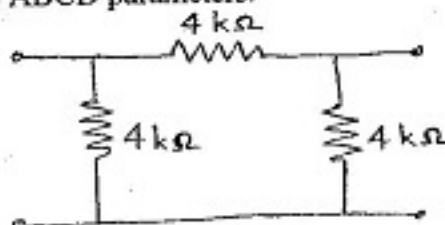


Fig.7(b)

(12 Marks)

- 8 a. Construct the dual of the network shown in Fig.8(a). (10 Marks)
- b. What should be the value of a pure resistance to be connected across the terminals a and b in the circuit of Fig.8(b), so that max power is transferred to the load. What is the max power? (10 Marks)

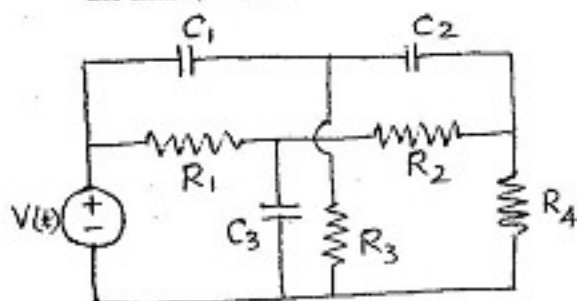


Fig 8(a)

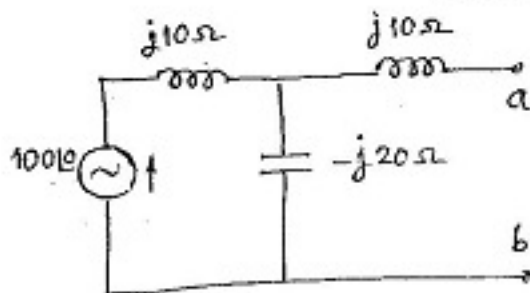


Fig 8 b