

Fig. Q4 (a)

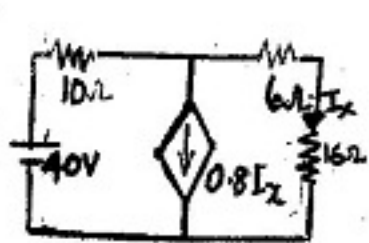


Fig. Q4 (b)

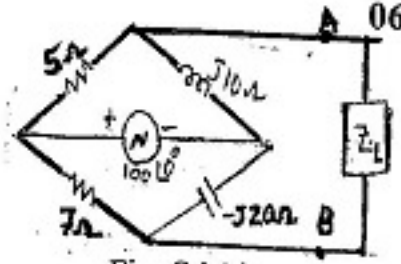


Fig. Q4 (c)

- b. State Norton's theorem and find the current through 16 ohm resistor using Norton's theorem in figure Q4 (b). (07 Marks)
- c. Find the value of  $Z_L$  for which maximum power is transferred to the load  $Z_L$  from the network in figure Q4 (c). (06 Marks)
- 5 a. A series RLC circuit has  $R = 50 \Omega$ ,  $L = 0.01 \text{ H}$  and  $C = 0.04 \mu\text{F}$  and is connected to ac source of 100 V. Find the i) resonant frequency ii) Circuit impedance at resonant frequency iii) Maximum value of voltage across capacitance and the frequency at which it occurs iv) Voltage across inductance at resonance. (06 Marks)
- b. For the network shown in figure Q5 (b) determine the following: i)  $f_0$  ii)  $Q$  iii) half power frequencies iv) Band width. (07 Marks)

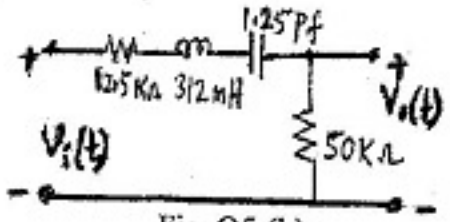


Fig. Q5 (b)

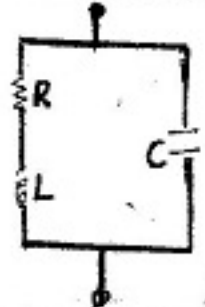


Fig. Q5 (c)

- c. Derive the expression for resonant frequency for the parallel resonant circuit shown in figure Q5 (c). If  $R = 25 \Omega$ ,  $L = 0.5 \text{ H}$  and  $C = 5 \mu\text{F}$ , find  $W_0$ ,  $Q$  and bandwidth for the circuit. (07 Marks)
- 6 a. For the network shown in figure Q6 (a), find  $i_1$ ,  $i_2$ ,  $\frac{di_1}{dt}$ ,  $\frac{di_2}{dt}$ ,  $\frac{d^2 i_2}{dt^2}$  at  $t = 0^+$ . The circuit was in steady state before the closure of the switch. Assume all initial conditions zero. (10 Marks)

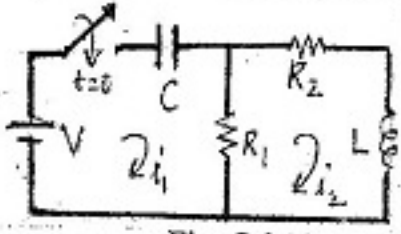


Fig. Q6 (a)

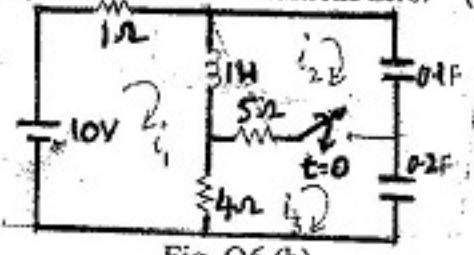


Fig. Q6 (b)

- b. The network shown in figure Q6 (b) was in steady state before  $t = 0$ . The switch is closed at  $t = 0$ . Determine the three mesh currents  $i_1$ ,  $i_2$ ,  $i_3$  at  $t = 0^+$ . (10 Marks)
- 7 a. The network shown in figure Q7 (a) was in steady state before  $t = 0$ . The switch is opened at  $t = 0$ . Find  $i(t)$  for  $t > 0$  using Laplace transform. (10 Marks)

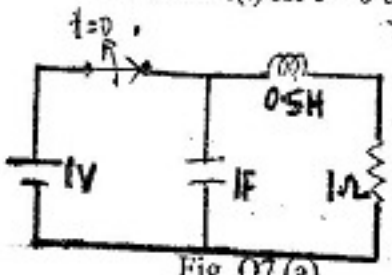


Fig. Q7 (a)

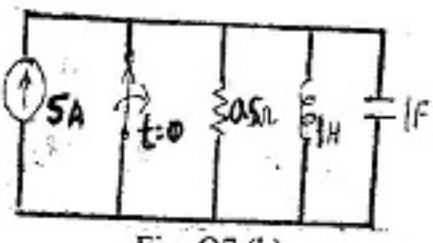


Fig. Q7 (b)

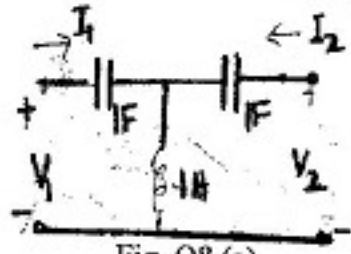


Fig. Q8 (a)

- b. For the network shown in figure Q7 (b) find the voltage across 0.5 ohm resistor, when the switch is opened at  $t = 0$ . Assume all initial conditions zero. (10 Marks)
- 8 a. Determine the h-parameters for the network shown in figure Q8 (a). (10 Marks)
- b. Z-parameters of a network are obtained from an experiment. Explain how Y-parameters and transmission parameters can be computed from the experimental data. (10 Marks)