

Third Semester B.E. Degree Examination, Dec.08 / Jan.09
Network Analysis

3 hrs.

Max. Marks:100

Note : Answer any FIVE full questions.

- 1 a. Define the following with examples: i) Graph ii) Oriented graph iii) Tree
iv) Cut set v) Tie set (10 Marks)
- b. Write the cut set and tie set schedule for network shown in figure Q1 (b). (10 Marks)

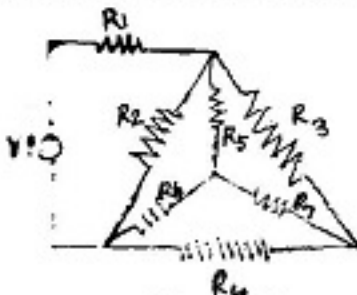


Fig. Q1 (b)

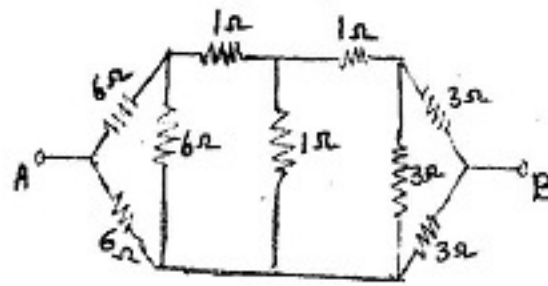


Fig. Q2 (a)

- 2 a. Find the resistance between point A and B of figure Q2 (a) using star-delta transformation. (10 Marks)
- b. Find the value of the resistance R_L which receives maximum power of the circuit of Figure Q2 (b) and find this power. (10 Marks)

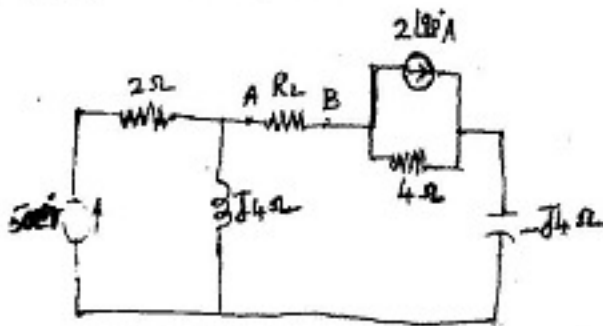


Fig. Q2 (b)

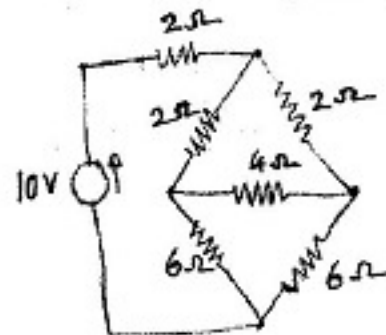


Fig. Q3 (b)

- 3 a. State and explain reciprocity theorem and Millmans theorem. (10 Marks)
- b. Find the current in 4Ω using Thevenins theorem for the circuit of figure Q3 (b). (10 Marks)
- 4 a. Find the current in 24Ω resistance using mesh current analysis in figure Q4 (a). (10 Marks)

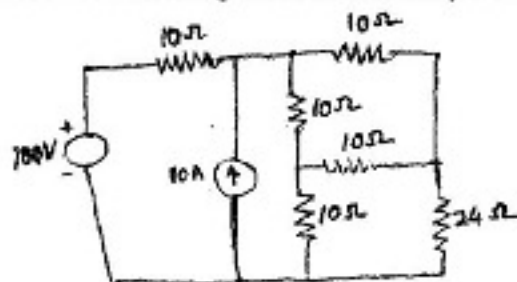


Fig. Q4 (a)

- b. Find current in 24Ω of figure Q4 (a) using node voltage analysis. (10 Marks)

- 5 a. Obtain the expressions for the following in a series RLC circuit: i) Resonant frequency ii) Q factor iii) Half power frequencies iv) Band width. (10 Marks)
- b. A series circuit has $R = 10\Omega$, $L = 5 \text{ mH}$, $C = 20 \mu\text{F}$. Find i) fr ii) Q factor iii) half power frequency and iv) current at resonance if applied voltage is 100 V. (10 Marks)
- 6 a. Explain why we study initial conditions. (04 Marks)
- b. In the Network shown in figure Q6 (b), K is closed at $t = 0$, find V_1 , $\frac{dV_1}{dt}$, $\frac{d^2V_1}{dt^2}$ at $t=0+$. (10 Marks)
- c. If $I(s) = \frac{10}{s(s+1)}$, find $i(0)$ and $i(\infty)$ using initial and final value theorems. (06 Marks)

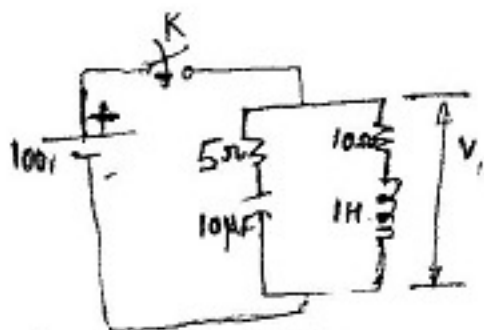


Fig. Q6 (b)

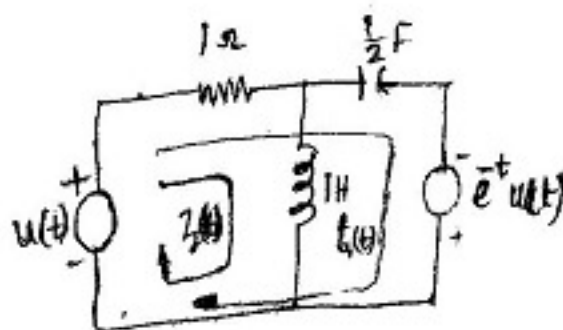


Fig. Q7 (a)

- 7 a. In the figure Q7 (a) all initial conditions are zero. Find $i_1(t)$ and $i_2(t)$ using Laplace transformation. (10 Marks)
- b. State and prove convolution theorem. (05 Marks)
- c. Find L.T of waveform shown in figure. Q7 (c). (05 Marks)

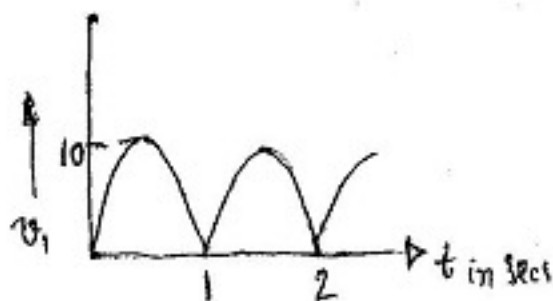


Fig. Q7 (c)

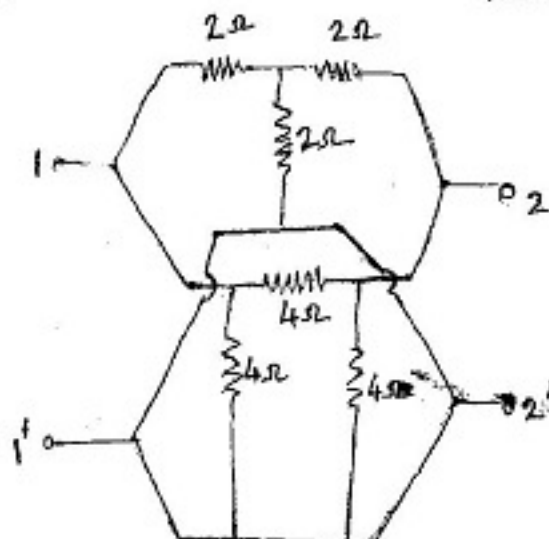


Fig. Q8 (b)

- 8 a. Obtain z parameters in terms of transmission parameters. (08 Marks)
- b. Find y and h parameters for the network shown in figure Q8 (b). (12 Marks)