

PART - B

- 5 a. Define the following terms: (04 Marks)
 (i) Resonance (ii) Selectivity (iii) B. W. (iv) Q-factor.
 b. Derive the expression for a resonant frequency for a parallel circuit having R in series with L only. (06 Marks)
 c. Two coils; one of $R_1=0.51\Omega$, $L_1= 32\text{mH}$ & other coil of $R_2=1.3\Omega$, $L_2= 15\text{mH}$ are in series and are in series with a capacitor of $25\ \mu\text{F}$ & $62\ \mu\text{F}$ and a series resistor of resistance $0.24\ \Omega$. Determine the following:
 (i) Resonant frequency (ii) Q-factor of the circuit (iii) B.W.
 (iv) Power dissipated in the circuit at resonant frequency (10 Marks)
- 6 a. For the network shown in Fig.6(a), the switch is moved from position 1 to position 2 at $t=0$ the steady state has been reached before switching. Calculate i , di/dt , d^2i/dt^2 at $t=0^+$ (10 Marks)

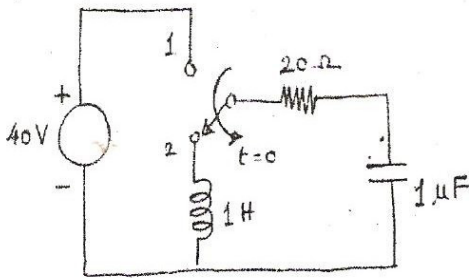


Fig.6(a)

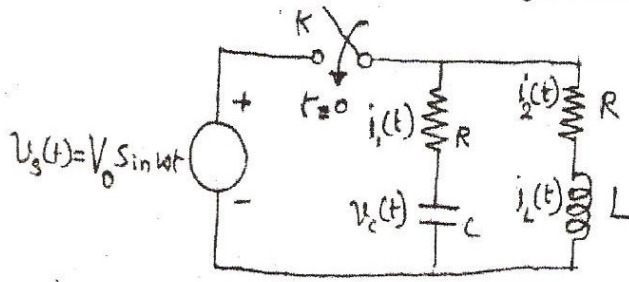


Fig.6(b)

- b. For the network shown in Fig.6(b), find out $\frac{di_1(0^+)}{dt}$ & $\frac{di_2(0^+)}{dt}$ when the switch K is closed at $t=0$. Assume the circuit was not activated before $t=0$. (10 Marks)

- 7 a. Define the impulse function & obtain its L.T. (04 Marks)
 b. For a series RL circuit shown in Fig.7(b), the switch K is closed at time $t=0$, find the current $i(t)$ using Laplace transform. (06 Marks)

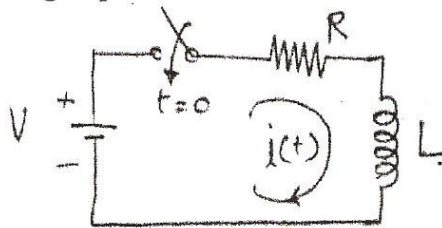


Fig.7(b)

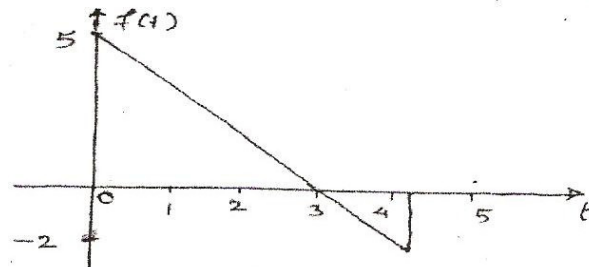


Fig.7(c)

- c. Obtain the Laplace transform of $F(t)$ for the waveform shown in Fig.7(c). (10 Marks)

- 8 a. Define Z-parameters. (04 Marks)
 b. Obtain the relationship between T & h parameters i.e. T parameters in terms of h parameters. (06 Marks)
 c. Obtain the Y-parameters of the two port network shown in Fig.8(c). (10 Marks)

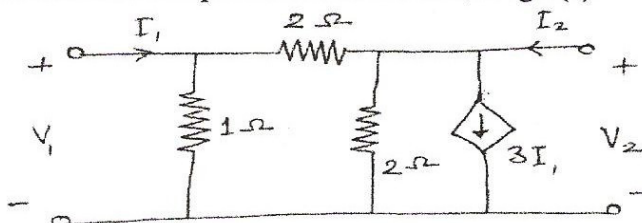


Fig.8(c)
