

NEW SCHEME

USN

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, January/February 2005

Electrical & Electronics Engineering


Network Analysis

Time: 3 hrs.]

[Max.Marks : 100

Note: Answer any FIVE full questions.

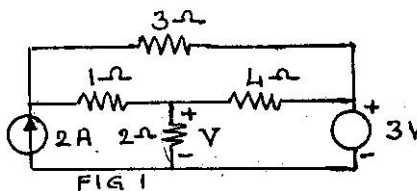1. (a) Obtain expressions for a set of equivalent
 - i) Y connected impedances to replace a set of Δ connected impedances
 - ii) Δ connected admittances to replace a set of Y connected admittances. (10 Marks)
- (b) For the network shown in Fig.1, determine the voltage V using source shift and / or source transformation techniques only. Then verify by node equations. (10 Marks)



2. (a) Under what conditions do you consider topology for network analysis? For the graph shown in Fig.2, for a co-tree (4, 5, 7, 8), write tie set and cut set matrices. (10 Marks)

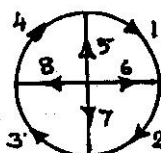


FIG 2.

- (b) For the network shown in Fig. 3, draw its dual. Write in integro differential form i) mesh equations for the given network ii) node equations for the dual. $V(t) = 10\sin 40t$. (10 Marks)

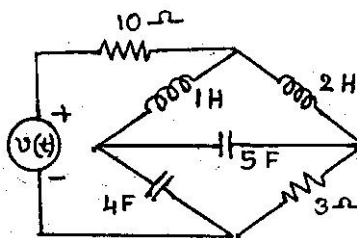


FIG 3

3. (a) Use mesh current method to determine the current in the capacitor of 6Ω of the bridge network shown in Fig.4 (10 Marks)



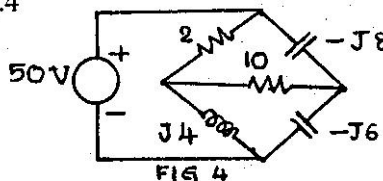
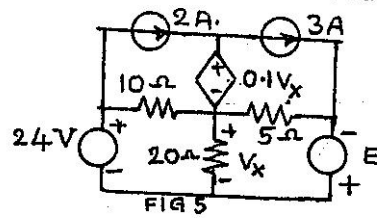


FIG 4


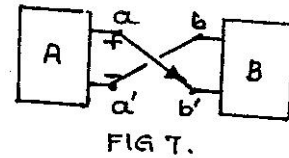
- (b) Use node equations to determine what value of 'E' will cause V_x to be zero, for the network shown in fig. 5. (10 Marks)



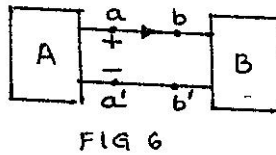4. (a) State and explain i) Reciprocity theorem ii) Millmann's theorem. (10 Marks)
 (b) When two networks A and B are connected as shown in fig. 6, $I_{ab} = 1A$ and $V_{aa'} = \sqrt{2} \angle -45^\circ V$. When the same networks are connected as in Fig. 7, $I_{ab'} = 3A$ and $V_{aa'} = \sqrt{2} \angle 45^\circ V$. Find the Thevenin's equivalents of each of these networks. (10 Marks)



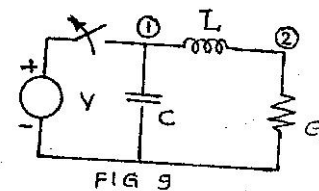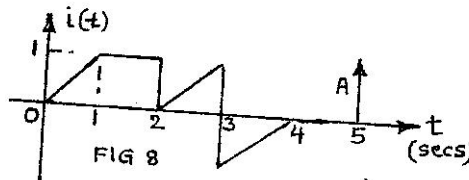5. (a) Define Q of a series resonant circuit. Obtain half power frequencies in terms of Q and show that the resonant frequency is the geometric mean of half power frequencies. (10 Marks)
 (b) In a parallel resonant circuit R, L and C are all in parallel. Half power frequencies are 103 and 118 r/s respectively. The magnitude of impedance at 105 r/s is 10Ω . Find R, L and C. (10 Marks)
6. (a) $R = 1\Omega$, $L = 1H$ and $C = \frac{1}{2}F$ are in series with a switch across C 2V is applied to the circuit. At $t = 0^-$ the switch is in closed position. At $t = 0$ the switch is opened. Find at $t = 0+$, the voltage across the switch, its first and second derivatives. (10 Marks)
 (b) State and prove (i) initial value theorem and (ii) final value theorem as applied to L transform. What are the limitations of each theorem? (10 Marks)
7. (a) The current function $i(t)$ shown in fig 8 is impressed on a capacitor C. What should be the strength A of the impulse so that the voltage across the C becomes zero for $t > 5secs$ (10 Marks)



- (b) In the circuit shown in fig. 9, the switch is opened at $t = 0$, with $V = 1V$, $C = 1F$, $L = \frac{1}{2}H$, $G = 1\Omega$ find the node voltages $V_1(t)$ and $V_2(t)$ by L transform method. (10 Marks)
8. (a) Define h and T parameters and derive expressions for [h] in terms of [T]. (10 Marks)
 (b) Find [z] and [y] for the two port network shown in fig.10. (10 Marks)

