

Reg. No.



Third Semester B.E. Degree Examination, January/February 2006
EC/TE/EE/IT/ML/BM
Network Analysis

Time: 3 hrs.)


(Max.Marks : 100)

Note: Answer any FIVE full questions.

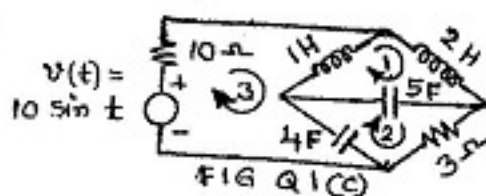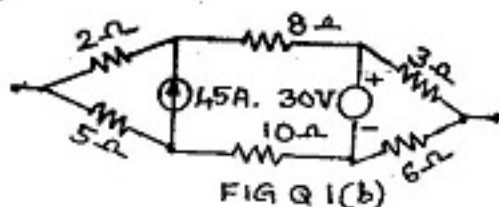
1. (a) Three impedances are connected in delta. Obtain expressions for their star connected equivalents. (6 Marks)
- (b) Reduce the network shown in fig Q. 1(b) to a single voltage source in series with a resistance using source shift and source transformations. (6 Marks)



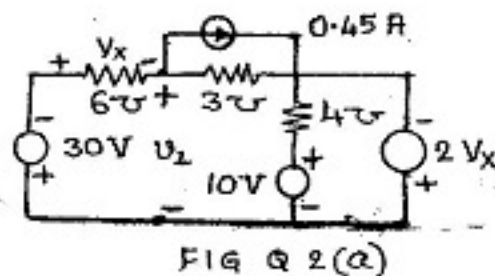- (c) For the network shown in Fig Q. 1(c), write the mesh equations, for the meshes indicated, in time domain. Draw the dual network and write its node equations. (8 Marks)
2. (a) Find V_2 through the use of nodal analysis, of the network shown in fig Q. 2(a). Also find V_x . (6 Marks)



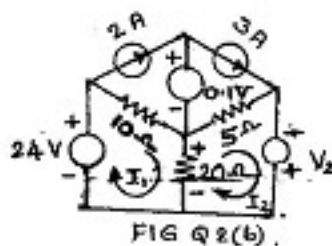- (b) Use mesh analysis to determine what value of V_2 in the network shown in fig Q 2(b) causes $v = 0$. v is the voltage across 20Ω . (6 Marks)



- (c) For the network shown in fig Q 2(c), perform source shifts, draw a graph, select tree with branches 1, 2 and 3 and obtain tie set and cut set matrices. (8 Marks)

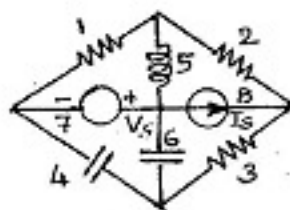


FIG Q 2(c).

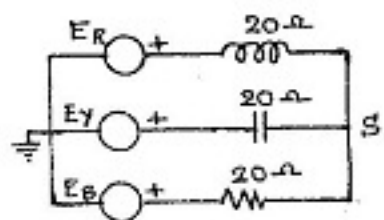


FIG Q 3(a).

3. (a) Use Millmann's theorem to determine the voltage V_s of the network shown in Fig Q 3(a) given that $E_R = 230 \angle 0^\circ V$, $E_Y = 230 \angle -120^\circ V$, and $E_B = 230 \angle 120^\circ V$. (6 Marks)
- (b) Prove that an alternating voltage source transfers maximum power to a load when the load impedance is the conjugate of the source impedance. (6 Marks)
- (c) A linear time invariant network when terminated with $R = 1\Omega$, the current is $5 \angle -45^\circ A$ ii) $X_C = 1\Omega$, the current is $10 \angle -45^\circ A$. Find the Thevinin's equivalent of the network. What will be the current if it is terminated with $X_L = 1\Omega$? (8 Marks)
4. (a) A series resonant circuit includes $1\mu F$ capacitor and a resistance of 16Ω . If the band width is $500 rad/sec$, determine i) ω_r ii) Q and iii) L . (6 Marks)
- (b) A two branch antiresonant circuit contains $L = 0.4 H$ and $C = 40 \mu F$. Resonance is to be achieved by variation of R_L and R_C . Calculate the resonance frequency for the following cases :
- $R_L = 120\Omega$, $R_C = 80\Omega$
 - $R_L = 80\Omega$, $R_C = 0$
 - $R_L = R_C = 100\Omega$ (6 Marks)
- (c) In the case of a series resonant circuit with frequency variation, obtain expressions for
- ω_C at which maximum voltage occurs across C
 - ω_L at which maximum voltage occurs across L and show that $\omega_L > \omega_C$ (8 Marks)
5. (a) Why do we need to study initial conditions? Write the equivalent form of the elements in terms of the initial condition of the element. (6 Marks)
- (b) A parallel R - L circuit is energised by a current source of 1 A. The switch across the source is opened at $t = 0$. Solve for v , Dv and D^2v all at $t = 0+$ if $R = 100\Omega$ and $L = 1H$. (6 Marks)
- (c) A series R - C branch with $R = 20\Omega$ and $C = 1\mu F$ is shunted by an inductor of resistance 20Ω and inductance $1H$. This is supplied by a D.C. source of $100V$ through a series resistance of 10Ω . There is a switch across 10Ω which is closed at $t = 0$. Solve for the currents in L and C and their derivatives at $t = 0+$. (8 Marks)
6. (a) State and prove i) initial value theorem and ii) final value theorem as applied to L transformation. (6 Marks)

- (b) Determine the Thevenin's equivalent $V_{ab}(s)$ and $Z_{ab}(s)$ for the network shown in Fig Q. 6 (b) for zero initial conditions. (6 Marks)

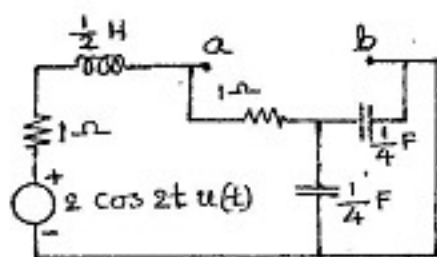


FIG Q 6(b)

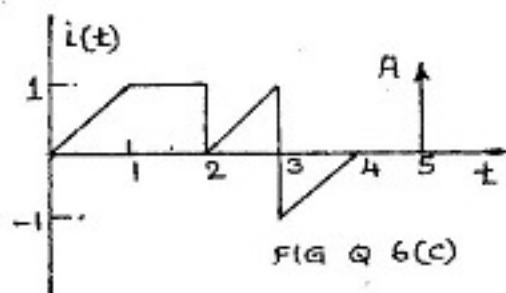


FIG Q 6(c)

- (c) The current $i(t)$ shown in fig. Q 6(c) is impressed upon a capacitor C . What should be the value of A of the impulse so that the voltage across the C becomes zero for $t > 5$ sec? (8 Marks)
7. (a) Explain the application of convolution integral in the analysis of linear systems. (6 Marks)
- (b) A network has a transfer function $H_1(s)$ and the impulse response of the system is a gate function of height 1 and spanning from 0 to 1 sec. Three of these networks are connected such that the overall transfer function is $H_3(s) = [H_1(s)]^3$. Using convolution or otherwise find the impulse response of the new system $h_3(t)$. (6 Marks)
- (c) For the circuit shown in fig Q. 7(c) the switch is opened at $t = 0$. If $L = \frac{1}{2}H$, $G = 1 \text{ mho}$, $C = 1F$ and $V = 1V$, find the node voltages $v_1(t)$ and $v_2(t)$

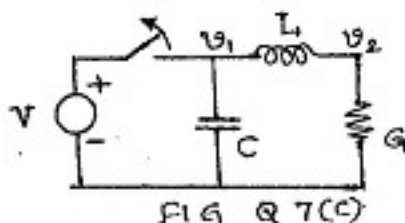


FIG Q 7(c)

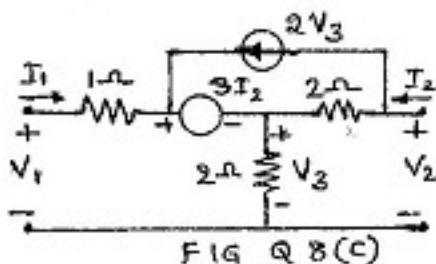


FIG Q 8(c)

- (8 Marks)
8. (a) A two port network, in terms of z parameters is said to be symmetric if $z_{11} = z_{22}$ and reciprocal if $z_{12} = z_{21}$. Obtain the corresponding conditions in terms of
- h parameters
 - T parameters, using the relationship between different two port parameters. (6 Marks)
- (b) Two 2 port networks are connected in cascade. Obtain T parameters of the interconnected network in terms of the T parameters of the individual networks. (6 Marks)
- (c) For the two port network shown in fig Q. 8(c). obtain z parameters. (8 Marks)