

Third Semester B.E. Degree Examination, June / July 08
Network Analysis

Time: 3 hrs.

Max. Marks: 100

Note : Answer any FIVE full questions.

- 1 a. Convert the network in Fig. Q 1(a) in to a single voltage source by source transformation. (06 Marks)
 b. Determine the equivalent resistance at terminals AB in the network in Fig. Q 1(b). (07 Marks)
 c. Find the voltage 'V' across 3Ω using nodal technique, in the network in Fig. Q 1(c). (07 Marks)

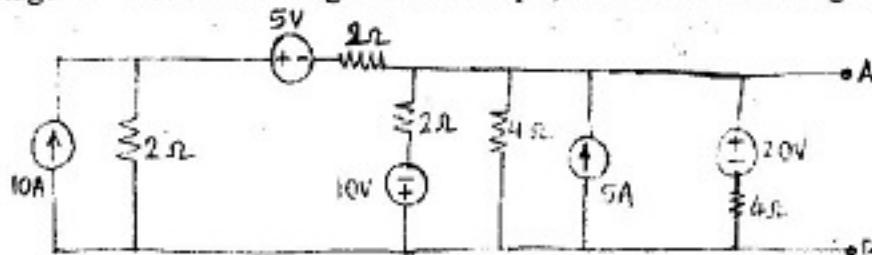


Fig. Q 1(a)

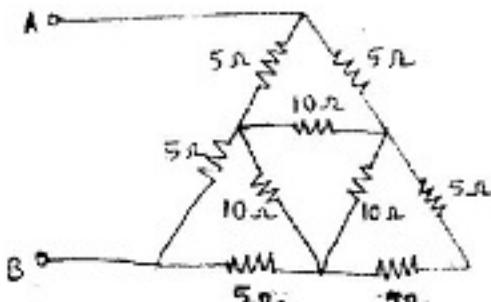


Fig. Q 1(b)

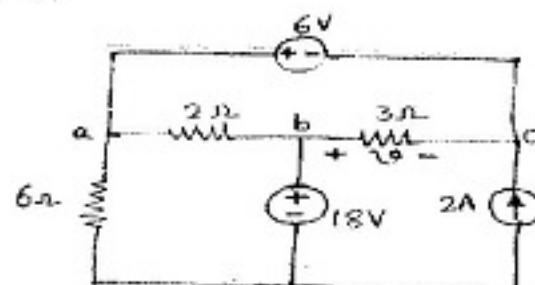


Fig. Q 1(c)

- 2 a. Find the branch currents using Tie – set schedule for the network in Fig. Q 2(a). (10 Marks)

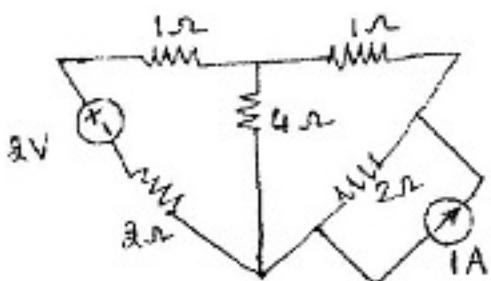


Fig. Q 2(a)

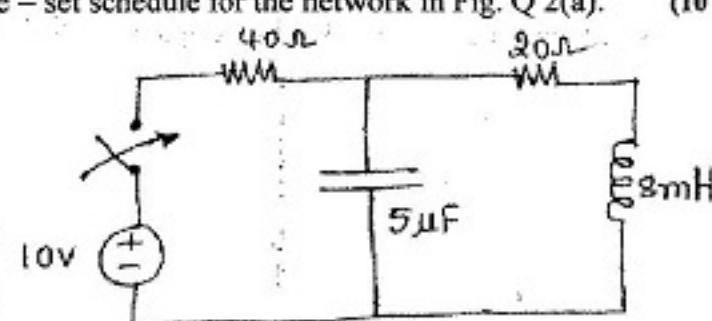


Fig. Q 2(b)

- b. Explain Duality in electric networks. Draw the dual of the network in Fig. Q 2(b). Write mesh equation for the given network and Nodal equations for the dual networks. (10 Marks)
 3 a. State superposition theorem. Find V_x using superposition principle in the network in Fig. Q 3(a). (10 Marks)

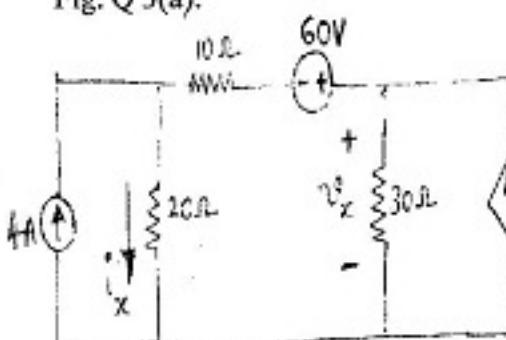


Fig. Q 3(a)

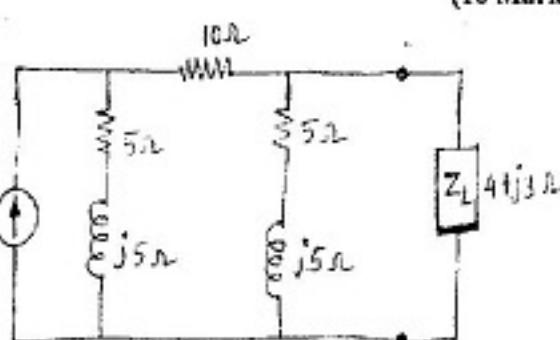


Fig. Q 3(b)

- b. Find the current in Z_L using Thevenin's theorem in the network in Fig. Q 3(b). State Thevenin's theorem. (10 Marks)

- 4 a. State Reciprocity theorem. Find the current through $5\ \Omega$ resistor and verify Reciprocity theorem in the network in Fig. Q 4(a). (10 Marks)

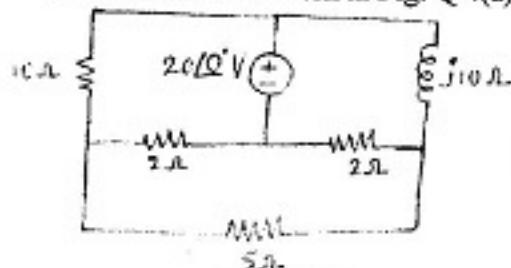


Fig. Q 4(a)

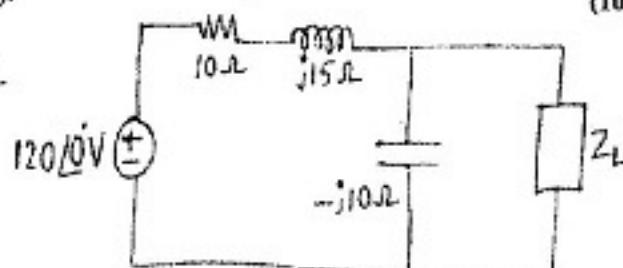


Fig. Q 4(b)

- 5 a. State maximum power transfer theorem. Find the value of Z_L for which it receives the maximum power in the network in fig 4(b). Find the maximum power. (10 Marks)
- b. In a $R - L - C$ series circuit, determine the expression for the resonant frequency and expressions for half power frequencies and bandwidth. (10 Marks)
- b. in the network in Fig. Q 5(b) find i) Resonant frequency ii) quality factor iii) bandwidth iv) Half power frequencies v) maximum power dissipated at resonance. (10 Marks)

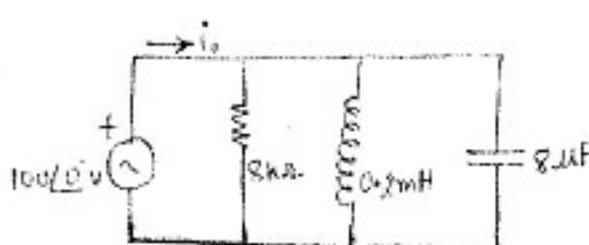


Fig. Q 5(b)

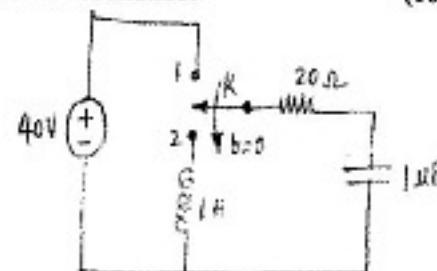


Fig. Q 6(b)

- 6 a. Explain the behaviour of network elements during switching, both at $t = 0^+$ and $t = \infty$. (10 Marks)
- b. In the network in Fig. Q 6(b) the switch is moved from position 1 to 2 at $t = 0$, steady state having reached before switching. Calculate i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$. (10 Marks)

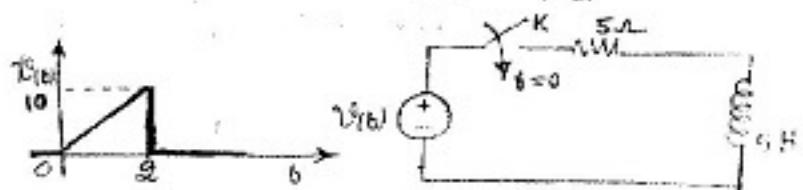


Fig. Q 7(c)

- 7 a. State and prove Initial and Final value theorem. (06 Marks)
- b. Find the Initial and final values of $i(t)$ if $I(s) = \frac{s+1}{(s+1)^2 + 9}$. (04 Marks)
- c. Find the current $i(t)$ for $t > 0$ when an input voltage signal $V(t)$ of the form shown in Fig. Q 7(c) is applied to the network. Assume zero Initial condition. (10 Marks)
- 8 a. Define Z parameters. Find Z parameters for the network shown in Fig. Q 8(a) and there from find Y parameters. (10 Marks)

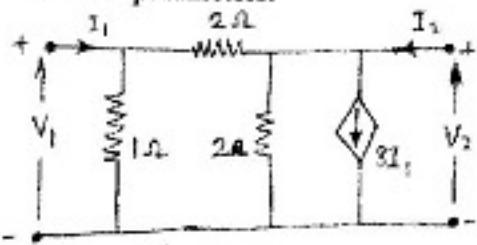


Fig. Q 8(a)

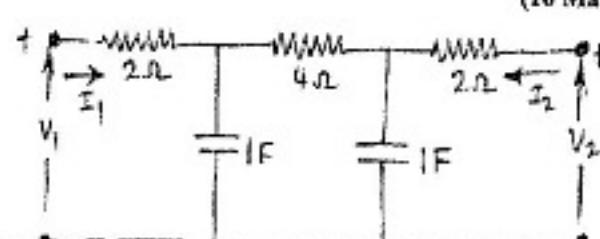


Fig. Q 8(b)

- b. Define Hybrid parameters. Find h parameters for the 2 port network in Fig. Q 8(b). (10 Marks)
