

CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

15NT34

Third Semester B.E. Degree Examination, Dec.2016/Jan.2017 MOSFETS and Digital Circuits

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. Discuss the type of MOS. (06 Marks)
b. What is JFET? Discuss the construction of JFET with neat diagram. (04 Marks)
c. Write a short note on second order effects in MOS. (06 Marks)

OR

- 2 a. Discuss the construction and characteristics of depletion type JFET. (07 Marks)
b. Discuss the VI characteristics of MOSFET. (05 Marks)
c. With the neat diagrams, explain twin well process. (04 Marks)

Module-2

- 3 a. Draw and explain realization of CMOS NOR gate and NAND gate. (08 Marks)
b. Discuss the delay parameters in CMOS. (04 Marks)
c. Write a note on AOI gate. (04 Marks)

OR

- 4 a. Explain the power dissipation equation for CMOS. (06 Marks)
b. Sketch and explain complementary CMOS gate computing $Y = \overline{(A + B + C)} \cdot D$. (05 Marks)
c. Write a note on MOSFET scaling and its impacts. (05 Marks)

Module-3

- 5 a. With a neat diagram, explain the operation of JK flipflop. (06 Marks)
b. Write a short comparison on latch versus registers. (04 Marks)
c. Define and explain the following terminologies setup time, hold time, clock to q delay, maximum clock frequency. (06 Marks)

OR

- 6 a. Explain CMOS master-slave register. (06 Marks)
b. Write a note on mux based latch. (06 Marks)
c. With neat diagram, explain the operation of D latch. (04 Marks)

Module-4

- 7 a. Define registers. Explain SISO and PIPO shift registers. (05 Marks)
b. Write a note on ring counter. (05 Marks)
c. Explain modulus-8 synchronous up/down counter with neat logic diagram. (06 Marks)

OR

- 8 a. Write a note on Johnson counter. (05 Marks)
b. Explain and design a mod-6 synchronous up counter using T flip-flop. (07 Marks)
c. Explain modulus-8 synchronous up counter with neat logic diagram. (04 Marks)

Module-5

- 9 a. Draw neatly and define Mealy and Moore machine model. (06 Marks)
 b. Design a Mod-8 synchronous counter using JK flipflop to count number of occurrence of an input i.e. number of times it is 1. (10 Marks)

OR

- 10 a. Design a Mealy state diagram for the sequence 1101. (06 Marks)
 b. Compare Mealy and Moore machine model and explain. (06 Marks)
 c. Construct a state table for the following state diagram of Fig.Q10(c). (04 Marks)

 


Fig.Q10(c)

* * * * *