

CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

15NT34

Third Semester B.E. Degree Examination, Dec.2017/Jan.2018 MOSFETs & Digital Circuits

Time: 3 hrs.

Max. Marks: 80

Note: Answer FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. Define JFET. Discuss the construction of JFET with a neat diagram. (05 Marks)
- b. Discuss the V-I characteristics of MOSFET. (05 Marks)
- c. Write a short note on second order effects in MOS. (06 Marks)

OR

- 2 a. With neat diagrams, explain n-well MOS transistor fabrication process. (10 Marks)
- b. Discuss the types of MOS and draw the input and output characteristics of NMOS transistor. (06 Marks)

Module-2

- 3 a. Explain with neat diagram the CMOS inverter voltage transfer characteristics and mention the regions of operation? (05 Marks)
- b. Explain the power dissipation equation for CMOS. (06 Marks)
- c. Write a short note on AOI gate and how it is constructed using CMOS circuits. (05 Marks)

OR

- 4 a. Draw and explain realization of CMOS NOR gate and NAND gate. Verify its functionality. (08 Marks)
- b. Discuss the delay parameters in CMOS. (04 Marks)
- c. Write a short note on MOS modeling. (04 Marks)

Module-3

- 5 a. Define sequential circuits. What are the types of sequential circuits? With neat diagram, neither explains the operation of CMOS SR latch using NOR gate. (10 Marks)
- b. With a neat diagram, explain the operation of D latch. With timing diagram. (06 Marks)

OR

- 6 a. With a neat diagram, explain the operation of JK flipflop. (07 Marks)
- b. Compare latch with registers. (04 Marks)
- c. Briefly explain ring oscillator and how in ring oscillator used for on chip clock generation. (05 Marks)

Module-4

- 7 a. Define registers. Explain PISO and SIPO shift registers. (08 Marks)
- b. Write a note on Johnson counter. (04 Marks)
- c. Write a note on Ring counter. (04 Marks)

OR

- 8 a. Explain Modulus-8 synchronous up/down counter with a neat diagram. (06 Marks)
- b. Using JK flip flop, design synchronous counter with the sequence 1, 3, 5, 2, 0, 7. (10 Marks)

Important Note - 1 On completing your answers, immediately fill in the required details in the space provided for the identification of the candidate's name. Any leakage of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

Module-5

- 9 a. Explain Mealy and Moore machine models. (08 Marks)
 b. Design a Mealy state diagram for the sequence 1101. (08 Marks)

OR

- 10 a. Design a Mod-8 synchronous counter using JK flip flop to count number of occurrence of an input, i.e. No. of times it is 1. (12 Marks)
 b. Construct a state table for the following state diagram. (04 Marks)

 


Fig. Q10 (b)
