

USN

--	--	--	--	--	--	--	--	--	--

10EC45

Fourth Semester B.E. Degree Examination, December 2012
Fundamentals of HDL

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART – A

- 1 a. Write switch level description in VHDL for the inverter circuit with nmos and pmos. Explain the advantages of this type description over the other types. (08 Marks)
b. Write the result of all shift and rotate operations in VHDL after applying them to a 7-bit vector A = 1001010 for one position. (06 Marks)
c. Explain verilog data types. (06 Marks)
- 2 a. Design 2 × 2 unsigned combinational array multiplier and write the VHDL code for the same. (08 Marks)
b. Draw the block diagram of a 3-bit carry-look ahead adder and write data flow description for its Boolean functions in verilog. (08 Marks)
c. Explain signal declaration and assignment with examples. (04 Marks)
- 3 a. Write the behavioural description for a half adder using verilog. (04 Marks)
b. Write the VHDL description for SR flip-flop using case statement and variable declaration. (06 Marks)
c. Explain Booth algorithm with flow chart. Write VHDL description to multiply two 4-bit numbers -5 and 7. (10 Marks)
- 4 a. Write gate level diagram and verilog structural description for D-latch. (08 Marks)
b. What is binding? Discuss binding between.
i) Entity and architecture.
ii) Library and component. (08 Marks)
c. What are the advantages of HDL structural description? (04 Marks)

PART – B

- 5 a. Write a VHDL function to find the greater of two signed numbers. (06 Marks)
b. Write HDL description to convert signed binary to the integer using task. (08 Marks)
c. What is the significance of procedure, task and function? Differentiate between them. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- 6 a. Describe the development of HDL code for an arithmetic logic unit and write the verilog code for 16-bit ALU to perform 8 operations. (08 Marks)
- b. Write the block diagram and function table of a 3SRAM. Using this write a verilog description for 16×8 SRAM. (08 Marks)
- c. How to attach a package to the VHDL module? Explain with example. (04 Marks)
- 7 a. Write mixed language description of a JK flip-flop with clear, invoking VHDL entity from verilog module. (08 Marks)
- b. Describe full adder using two half adder invoking verilog module from VHDL entity. (08 Marks)
- c. Explain the necessity of mixed language description. (04 Marks)
- 8 a. What is synthesis? With a neat flow chart, explain the steps involved in a synthesis process. (06 Marks)
- b. Design gate level synthesis and write VHDL description for the information given below:

Inputs		Output
a	b	z
00	0 – 7	$z = b$
01	0 – 7	$z = b + 4$
10	0 – 7	$z = b/2$
11	x x	$z = 15$
x x	8 – 15	$z = 15$

(14 Marks)

* * * * *