

Fourth Semester B.E. Degree Examination, Dec.2013/Jan.2014
Fundamentals of HDL

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting
at least TWO questions from each part.**

PART – A

- 1 a. Explain VHDL and verilog? Evaluate the expression $E = (A \text{ and not } B \text{ or } C \text{ or } 2 \text{ and } D)$ where $A = "11"$, $B = "1111"$, $C = "011000"$, $D = "111011"$ (07 Marks)
- b. Explain the following data-types:
 - i) Physical data types
 - ii) User-defined data type
 - iii) Array type
 - iv) Nets and
 - v) Parameters. (10 Marks)
- c. Write a verilog code for the circuit given in Fig. Q1 (c), using switch level description. (03 Marks)

 


Fig. Q1 (c)

- 2 a. Explain concurrent execution. (03 Marks)
- b. Write a verilog code in data flow description for a 2-bit magnitude comparator with the help of truth table and simplified Boolean expressions. (10 Marks)
- c. Write a VHDL code for 3-bit parallel subtractor using 1-bit full adder in data flow modeling style. (07 Marks)
- 3 a. Compare signal with variable. Give an example for each. (04 Marks)
- b. Using Booth algorithm, find the product of two signed 4-bit numbers -3 and 5. Write a verilog code using behavioral style of description. (10 Marks)
- c. Write a VHDL code to determine the number of one's in an 8-bit vector. The output of the detector must be '0' for even number of one's, while '1' for odd number of one's. (06 Marks)
- 4 a. Explain binding between library and module. (02 Marks)
- b. Write a verilog code to implement S-R latch in structured description. (06 Marks)
- c. Define state machine using the state machine concept, showing all the details design a counter, which counts 0, 2, 3, 5, 7. Write the VHDL code for the same. (Use JK flip-flop). (12 Marks)

PART – B

- 5 a. What are the significance of procedure, task and functions? Bring out the difference between procedure, task and function with an example. (08 Marks)
- b. Write a code to convert the fraction binary (4-bit) to real using procedure. (08 Marks)
- c. Write a note on verilog file processing. (04 Marks)

- 6 a. With syntax, explain package declaration and package body. (04 Marks)
- b. Write a verilog code to find the greatest element of an array. (06 Marks)
- c. Write a VHDL code to describe the finite sequential state machine given in Fig.Q6 (c). (10 Marks)

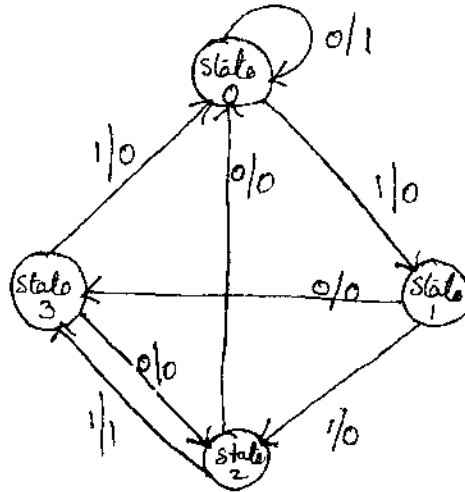


Fig. Q6 (c)

- 7 a. Write mixed-language description of a master slave D flip flop invoking VHDL entity from a verilog module. (10 Marks)
- b. Write mixed-language description of a simple JK flip flop with active low clear. (10 Marks)
- 8 a. Define synthesis. Synthesize the VHDL code given in the Fig. Q8 (a)

```

entity Ex is
    Port (a : in natural range 0 to 7;
          Y : out integer range 0 to 15);
end Ex;
architecture Ex_1 of Ex is
begin
    Process (a)
        Variable temp : integer range 0 to 15;
    begin
        if (a<3) then temp := 15;
        elseif (a >= 5) then temp := 0;
        else
            temp := a * (-5) + 25;
        end if;
    end process;
end Ex_1;
    
```

Fig. Q8 (a)

(10 Marks)

- b. Write verilog code for signal assignment statement $y = 2 * x + 3$. Show the synthesized logic symbol and gate level diagram. (10 Marks)