

--	--	--	--	--	--	--	--	--	--

Fourth Semester B.E. Degree Examination, December 2011

Linear ICs and Applications

Time: 3 hrs.

Max. Marks:100

**Note: 1. Answer any FIVE full questions, selecting at least TWO questions from each part.
2. Justify any assumptions made.**

PART – A

1.
 - a. Explain input offset current and state a typical input offset current level for an operational amplifier. Discuss offset nulling. (07 Marks)
 - b. Sketch the complete circuit of an op-amp non-inverting amplifier. Write equations for determining suitable values for each resistor :
 - i) using a bipolar op-amp and ii) using a BIFET op-amp. (07 Marks)
 - c. Design a differential amplifier for a gain of 100. If the input voltage, $V_1 = 10V$ and $V_2 = 10.01$ to $10.1V$. Calculate impedances at V_1 , V_2 , common mode and differential. Use 741 op-amp. (06 Marks)

2.
 - a. Explain how to determine the capacitor values for a high input impedance capacitor coupled inverting amplifier. (06 Marks)
 - b. Explain how exactly the circuit of a non-inverting ac amplifier is modified to be used with single supply op-amps. (06 Marks)
 - c. Design a capacitor-coupled inverting amplifier to operate with a +20V supply. The minimum input signal level is 50 mV, the voltage gain is to be 68, the load resistance is 500Ω , and the lower cut-off frequency is to be 200 Hz, using 741 op-amp. (08 Marks)

3.
 - a. With a neat sketch, explain Z_{in} MOD method of frequency compensation. Write the equation for the feedback factor. (09 Marks)
 - b. Define gain bandwidth product of an op-amp and explain its significance. (05 Marks)
 - c.
 - i) Calculate the cut-off frequency limited rise time for a voltage follower circuit using 741 op-amp. Also determine the slew-rate limited rise time if the output amplitude is to be 5V, and cut-off frequency is equal to $800 K\Omega$.
 - ii) Determine the maximum undistorted pulse output amplitude for the 741 voltage follower if the output rise time is not to exceed $1 \mu s$. (06 Marks)

4.
 - a. Draw the circuit of a current source using an op-amp and a power MOSFET. Indicate typical voltage levels throughout the circuit and explain its operation. (06 Marks)
 - b. Sketch the circuit of a two output half wave precision rectifier. Draw the input and output waveforms and explain the circuit operation. (06 Marks)
 - c. Design a voltage source to provide a constant output voltage of 6V using Zener diode $V_Z = 6.3V$. The load resistance has a minimum value of 150Ω and the available supply voltage is $\pm 12V$. Assume $I_Z = 20 mA$, $h_{fe(min)} = 20$, $I_{c(max)} > 42 mA$ and $V_{cc(max)} > V_{cc}$. Draw the circuit diagram and insert the designed values. (08 Marks)

PART – B

- 5 a. Sketch a precision rectifier peak detector circuit, draw the input and output waveforms and explain the circuit operation. Write the equation for calculating the capacitor value for a peak detector circuit. (06 Marks)
- b. With a neat circuit diagram and waveforms, explain the operation of triangular/rectangular wave generator. (08 Marks)
- c. Using a 741 op-amp with a supply of $\pm 12V$, design a phase-shift oscillator to have an output frequency of 3.5 kHz. (06 Marks)
- 6 a. Explain the operation of an op-amp based monostable multivibrator. Use relevant waveforms. (06 Marks)
- b. With a neat circuit diagram and waveforms, explain the operation of inverting Schmitt trigger. (06 Marks)
- c. Design a 2nd order high pass active filter to have a cutoff frequency of 12 kHz. Use a 715 op-amp and estimate the highest signal frequency that will be passed. (08 Marks)
- 7 a. What is the principle of switch-mode power supplies? Discuss their advantages and disadvantages. (06 Marks)
- b. Explain the functional block-diagram of IC 723 regulator. (06 Marks)
- c. Design a voltage regulator using IC 723 to meet the following specifications :
 $V_o = 5V$, $I_o = 100 \text{ mA}$, $V_{in} = 15 \pm 20\%$, $I_{sc} = 150 \text{ mA}$, $V_{sense} = 0.7V$. (08 Marks)
- 8 Explain the following with neat diagrams and waveforms :
- a. 555 timer as astable multivibrator (07 Marks)
- b. 566 voltage controlled oscillator (07 Marks)
- c. Successive approximation ADC (06 Marks)

* * * * *