

--	--	--	--	--	--	--	--	--	--

Fourth Semester B.E. Degree Examination, Dec.2015/Jan.2016

Linear IC's and Applications

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART – A

- 1 a. Define the following:
 - i) Differential amplifier
 - ii) CMRR
 - iii) Slew rate
 - iv) PSRR
 - v) Input offset voltage and current

(10 Marks)
- b. With the help of neat diagram, design a direct coupled non-inverting amplifier to have a voltage gain of approximately 66. The signal amplitude is to be 15 mV.
Given: $I_{B(max)} = 600 \text{ nA}$. **(10 Marks)**
- 2 a. Write short notes on:
 - i) Setting up the upper cutoff frequency for an inverting amplifier.
 - ii) Use of single polarity supply in voltage follower. **(10 Marks)**
- b. Design a capacitor coupled non-inverting amplifier using 741 op-amp, with the following specification:
 - i) With a +24V supply
 - ii) Voltage gain of 100
 - iii) Output amplitude of 5V
 - iv) Lower cut-off frequency of 75 Hz
 - v) $R_{L(min)} = 5.6 \text{ K}\Omega$. **(10 Marks)**
- 3 a. Define: i) loop gain, ii) loop phase shift, iii) unity gain BW. **(06 Marks)**
- b. What is frequency compensation? Explain phase lag compensation network. **(06 Marks)**
- c. Calculate the slew rate-limited cutoff frequency for a voltage follower circuit using 741 op-amp if the peak of sine wave output is to be 5 V.
 - i) Determine maximum peak value of sinusoidal output voltage that will allow the 741 voltage follower CFT to operate at 800 kHz unity-gain cut off frequency.
 - ii) Calculate maximum peak value of sine wave output voltage that can be produced by the amplifier if frequency is 8 kHz. Given slew rate $S = 0.5 \text{ V}/\mu\text{s}$. **(08 Marks)**
- 4 a. With the help of neat diagram, explain Zener diode peak clipper. **(08 Marks)**
- b. With the help of neat CFT diagram, design an instrumentation amplifier to have an overall voltage gain of 900. The input signal amplitude is 15 mV, 741 op-amps are to be used and supply is $\pm 15 \text{ V}$. Assume $I_2 = 50 \mu\text{A}$ and 15 (100 I_{Bmax}) **(12 Marks)**

PART – B

- 5 a. With the help of neat circuit diagram, explain the working of sample and hold circuit. **(08 Marks)**
- b. Derive, $V_{0, \text{comp}} = \left(1 + \frac{R_2}{R_{TC}}\right) \frac{KT}{q} \ln\left(\frac{v_i}{V_{ref}}\right)$ for an log amplifier, where $R_2 =$ feedback resistance of last op-amp stage $R_{TC} =$ temperature sensitive resistance with positive co-efficient of temperature. **(12 Marks)**

- 6 a. Draw the circuit diagram of an inverting Schmitt trigger using op-amp with UTP and LTP = $\pm xV > 0V$. Draw the output, input waveforms. Explain clearly the operations. (06 Marks)
- b. Design an astable multivibrator to have a $\pm xV$ output with a frequency of 1 kHz. $|UTP| = |LTP| = 0.5 V$.

 


Fig.Q6(b)

- c. Design a first-order active low pass filter to have a cut off frequency of 1 kHz using $\mu A 741$ op-amp. $I_{B(max)} = 500 nA$. (09 Marks)
(05 Marks)
- 7 a. Sketch the circuit of a regulated power supply and explain its operation. (08 Marks)
- b. List and briefly explain the characteristics of 3 terminal IC regulators. What are the limitations of these regulators? (07 Marks)
- c. Define and explain the following terms with respect to voltage regulator:
i) Line regulation
ii) Load regulation (05 Marks)
- 8 a. A 555 astable multivibrator has $R_A = 2.2 K\Omega$, $R_B = 3.9 K\Omega$, $C = 0.1 \mu F$. Calculate:
i) t_{high}
ii) t_{low}
iii) free running frequency f_0 and % duty cycle
Draw the circuit diagram. (07 Marks)
- b. Explain the following for a PLL:
i) Lock in range
ii) Capture range
iii) Pull in time (06 Marks)
- c. With the help of neat diagram, explain the operation of R-2R ladder DAC. (07 Marks)

* * * * *