

--	--	--	--	--	--	--	--	--	--

Fourth Semester B.E. Degree Examination, June/July 2014
Linear ICs and Applications

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting
at least TWO questions from each part.**

PART – A

- 1 a. Define the following parameters and mention its practical values for op-Amp 741.
(i) CMRR (ii) Slew-rate (iii) PSRR (iv) Output offset voltage. (08 Marks)
- b. Explain direct-coupled two I/P-Inverting summing amplifier with neat diagram and necessary design steps. (06 Marks)
- c. A non-inverting amplifier is to amplify a 100 m.V signal to a level to 5 V. Using a 741 op-Amp, design a suitable circuit. (06 Marks)
- 2 a. Sketch the circuit of a high Z_{in} - capacitor –coupled voltage follower and design its steps. (06 Marks)
- b. A capacitor coupled non-inverting amplifier using 741 op-Amp has $A_v = 100$ & $V_o = 5$ V. The load resistance is 10 k Ω and the lower cut-off frequency is to be 100 Hz. Design a suitable circuit. (08 Marks)
- c. Explain inverting A.C. Amplifier with neat diagram and mention its design steps using only single-supply op-Amp. (06 Marks)
- 3 a. Explain phase lead and phase lag compensation methods along with frequency response. (08 Marks)
- b. Consider a 741 op-Amp with slew rate of 0.6 V/ μ s is used as a voltage follower. Calculate (i) The slew rate limited cut-off frequency if the sine wave o/p is 6V. (ii) Calculate the maximum peak value of the sinusoidal o/p voltage, if the circuit operator with unity gain cut-off frequency of 800 kHz. (iii) Calculate the maximum peak value of the o/p voltage, if the upper cut-off frequency is 8 kHz. (06 Marks)
- c. List the precautions that should be used for op-Amp circuit stability. (06 Marks)
- 4 a. Draw the circuit of an instrumentation amplifier and explain how the voltage gain can be varied? (10 Marks)
- b. Discuss the operation of precision full wave rectifier circuit using bipolar op-Amp. (10 Marks)

PART – B

- 5 a. Explain the operation of op-Amp sample and hold circuit with signal, control and output waveforms. (08 Marks)
- b. Draw a neat sketch and explain the working of wein bridge oscillator circuit. (06 Marks)
- c. Explain frequency doubler technique using op-Amp. (06 Marks)
- 6 a. Sketch the circuit of a second order low pass filter and explain its working. (07 Marks)
- b. An INV Schmitt trigger circuit is to have UTP = 0 V and LTP = 2.5 V. Design a suitable circuit using a bipolar op-Amp with ± 15 V supply. (06 Marks)
- c. Sketch the circuit of an op-Amp astable multivibrator and show the voltage waveforms at various points and explain its operation. (07 Marks)

- 7 a. Explain the terms line, load regulation and ripple rejection for a dc voltage regulator. (06 Marks)
b. Design a voltage regulator using IC723 to get a voltage o/p of 25 V. (08 Marks)
c. Mention the salient features of a 723 regulator. (06 Marks)
- 8 a. Explain Mono-stable multi-vibrator using 555 Ic ? (06 Marks)
b. With a neat sketch, explain the working of a R-2R ladder network. (08 Marks)
c. With block diagram, explain successive approximation ADC. (06 Marks)

* * * * *