

Fourth Semester B.E. Degree Examination, June/July 2016
Linear IC's and Applications

Time: 3 hrs.

Max. Marks:100

- Note: 1. Answer FIVE full questions, selecting at least TWO questions from each part.**
2. Missing data if any may be suitably assumed.

PART - A

- 1 a. Explain the following terms with reference to OPAMP:
 i) Input off-set voltage
 ii) Input bias current
 iii) Slew rate (12 Marks)
- b. Design a noninverting amplifier circuit shown in Fig.Q1(b) to meet the following specifications. Use 741 OPAMP voltage gain = 50, signal amplitude = 10 mV. I_{Bmax} for 741 OPAMP = 500 nA. (From data sheet)

 


Fig.Q1(b)

(08 Marks)

- 2 a. Briefly discuss the upper cutoff frequency of an OPAMP circuit and show, how the cutoff frequency can be set for inverting, non-inverting and difference amplifier. (12 Marks)
- b. A capacitor coupled voltage follower is to be designed to have a lower cutoff frequency of 120 Hz. The load resistance is 8.2 K Ω and the OPAMP used has a maximum input bias current of 600 nA. Design a suitable circuit. (08 Marks)
- 3 a. Show how the slew rate of an OPAMP can produce distortion in a sinusoidal output waveform. Also, explain how the slew rate can limit the amplitude of the distortion free sinewave output for a given OPAMP cutoff frequency. (12 Marks)
- b. i) Calculate the cutoff frequency limited rise time for a voltage follower circuit using a 741 OPAMP. Also determine the slew rate limited rise time if the output amplitude is to be 5V and cutoff frequency $f_c = 800$ KHz.
 ii) Determine the max undistorted pulse output amplitude for the 741 voltage follower, if the output rise time is not to exceed 1 μ sec.
 iii) Calculate the min rise time and the max pulse amplitude at that rise time for a 741 amplifier with an upper cutoff frequency of 100 kHz. (08 Marks)
- 4 a. Sketch the complete circuit of an instrumentation amplifier. Discuss the characteristics of the circuit and show how the voltage gain can be varied. (10 Marks)
- b. With a neat diagram, explain the working of a sample and hold circuit. Discuss the hold time and acquisition time. (10 Marks)

PART – B

- 5 a. With the help of a neat circuit diagram, explain the working of a fullwave precision rectifier circuit. Mention its advantage. (12 Marks)
- b. Design a RC phase shift oscillation using 741 IC chip. For an oscillating frequency of 2 kHz. The supply voltage = $\pm 15V$. (08 Marks)
- 6 a. With a neat circuit diagram and relevant waveforms (at pin no 2, 3 and 6 of 741 OPAMP), explain the working of a monostable multivibrator circuit using OPAMP. (12 Marks)
- b. An Astable multi-vibrator using 555 timer is connected with $R_a = 2.2 K\Omega$, $R_b = 6.8 K\Omega$, $c = 0.1 \mu f$, calculate:
- t_{high}
 - t_{low}
 - free running frequency
 - duty cycle. (08 Marks)
- 7 a. Write notes on:
- Phase locked loop
 - 723 regulator (12 Marks)
- b. Design a bandwidth filter (Bpf) with the suitable contribution of Lpf and Hpf (1st order) to meet the following specifications: Passband = 5 kHz to 15 kHz. (08 Marks)
- 8 a. Explain the following terms with reference to D/A converter:
- Resolution
 - Accuracy
 - Linearity (10 Marks)
- b. With the help of a block diagram, explain the working of a successive approximation type of A/D converter. (10 Marks)

* * * * *