

--	--	--	--	--	--	--	--	--	--

Fourth Semester B.E. Degree Examination, June/July 2015
Linear IC's and Applications

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting
at least TWO questions from each part.**

PART – A

1.
 - a. Draw the basic circuit diagram of an op-Amp ; Identify all the terminals and briefly explain how the circuit operates. (06 Marks)
 - b. Explain the following parameters of an op-Amp with a suitable diagram : -
 i) Input off set current ii) OFF SET NULLING iii) Input inpendance (06 Marks)
 - c. The difference of two input signals is to be amplified by a factor of 37. Each input has an amplitude of approximately 50 milli volts. Using an LF 353 op Amp, design and draw a suitable circuit. Also calculate the differential and common mode input resistances. (08 Marks)

2.
 - a. Draw the circuit of high input impedance capacitor coupled non inverting amplifier. Briefly explain the circuit operation. (10 Marks)
 - b. Design and draw a capacitor coupled non-inverting amplifier using a single polarity supply voltage circuit.
 Given : Supply voltage = + 24 V
 Voltage gain = 100
 Output Amplitude = 5V
 Lower cut off frequency = 75Hz
 Minimum load resistance = 5.6 kΩ
 Op Amp = 741
 [From 741 data sheet $I_{Bmax} = 500$ n Amp] (10 Marks)

3.
 - a. Explain the working of the following with a neat diagram.
 i) Phase lead compensation Network.
 ii) Miller – effect compensation using
 1) Transistor 2) op-Amp (12 Marks)
 - b. i) Calculate the cut off frequency limited rise time for a voltage follower circuit using a 741 op Amp. Also determine the slew-rate limited rise time if the ouput amplitude is to be 5 volts.
 ii) Detetmine the miximum undistorted pulse output amplitude for the 741 voltage follower if the output rise time is not to exceed 1μs.
 iii) Calculate minimum output rise time and the maximum pulse amplitude at that rise time for a 741 amplifier with an upper cut-off frequency of 100 KHz. [The typical slew-rate for 741 op-Amp] S = 0.5 volts per μs (08 Marks)

4.
 - a. Draw the circuit of a current source using op-Amp for a floating load and explain its operation. (05 Marks)
 - b. Draw & compare the performance of a difference amplifier with that of a differential input and output amplifier. (05 Marks)
 - c. Design and draw precision fullwave rectifier circuit to produce 2 volts peak output from a sine wave input with a peak value of 0.5v and a frequency of 1MHz. Use bi-polar op-Amps with a supply voltage of ± 15 v. (10 Marks)

PART – B

- 5 a. Explain the operation of a precision clamping circuit using op-amp. Draw the input and output wave forms. Show how the out voltage can be biased to any desired level. (08 Marks)
- b. Draw a basic multiplier schematic symbol and identify the terminals. Show how two analog voltages are multiplied by using log-antilog signal? List out the applications of multiplier. (06 Marks)
- c. Draw a practical wien bridge oscillator circuit with a negative feed back, explain its operation. (06 Marks)
- 6 a. Draw the circuit of an op-amp astable multivibrator. Show the voltage waveforms at various points in the circuit. Explain its operation and design procedure. (10 Marks)
- b. With a neat sketch explain the operation of
- 1st order Low pass Active filter
 - 2nd order High pass Active filter
- (10 Marks)
- 7 a. Draw the series op-amp regulator power supply using discrete components, and explain its operation. (05 Marks)
- b. Explain the following terms :-
- Line regulation
 - load regulation and
 - ripple rejection for a D.C voltage regulator
- (06 Marks)
- c. What are the limitations of three terminal regulator? Draw & explain the functional block diagram of 723 regulator. (09 Marks)
- 8 a. Explain the following for PLL
- Lock-in-range
 - Capture range
 - Pull-in-time
- (06 Marks)
- b. A 555 A stable multi vibrator has $R_A = 6.8 \text{ k}\Omega$, $R_B = 3.3 \text{ k}\Omega$ and $c = 0.1 \text{ }\mu\text{F}$ calculate
- t_{high}
 - t_{low}
 - Free running frequency
 - Duty cycle
- Draw the connection diagram. (10 Marks)
- c. Calculate the value of LSB, MSB and full scale output for an 8 bit DAC for 0 to 10 Volts range
- 0110 (For a 4 bit DAC)
 - 10111100 (For a 8 bit DAC)
- (04 Marks)

* * * * *