

--	--	--	--	--	--	--	--	--	--

Fourth Semester B.E. Degree Examination, June/July 2015
Linear Integrated Circuits and Applications

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, selecting
atleast TWO questions from each part.**

PART – A

- 1
 - a. Explain the working of a basic operational amplifier circuit with $R_c = 7.5 \text{ K}\Omega$, $R_E = 3.8 \text{ K}\Omega$ and powered by $\pm 12\text{V}$ supply. (08 Marks)
 - b. Design a bias-current compensated inverting amplifier to amplify a dc input of 150 mV by a factor of 40. Use a bipolar op-amp with $I_{B_{max}} = 500 \text{ nA}$. (06 Marks)
 - c. Derive an expression to relate the input and output common mode voltage (V_{icm} and V_{ocm}) of a non-inverting amplifier. (06 Marks)

- 2
 - a. Explain the realization of a C-coupled voltage follower for AC amplifier applications, discussing cut-off frequency design concept. (06 Marks)
 - b. Design a BIFET op-amp based high input impedance C-coupled non-inverting amplifier for a lower cut-off frequency of 120 Hz. Given: $V_{in} = 20 \text{ mV}$, $V_o = 5\text{V}$ and $R_{L_{min}} = 10\text{K}\Omega$. (08 Marks)
 - c. Explain the concept and construction of a C-coupled inverting amplifier using a single-polarity supply ($+V_{cc}$). (06 Marks)

- 3
 - a. Considering the frequency and phase responses of an uncompensated op-amp with a three-stage model, discuss the concept of circuit stability. (10 Marks)
 - b. Explain frequency compensation based on Miller effect, also explaining the capacitance-amplification principle. (06 Marks)
 - c. A voltage follower is to operate at a unity gain bandwidth of 1 MHz, and the op-amp has a slew rate of 0.75 V/ μs . Determine the permissible peak output voltage, and the cut-off frequency related rise time. (04 Marks)

- 4
 - a. Design a current source to produce an output of 150 mA to a grounded load of maximum value 30 Ω . Use an op-amp with $\pm 12\text{V}$ supply and a power MOSFET with $R_{D_{on}} = 6\Omega$ as the current booster. (08 Marks)
 - b. Derive an expression for the differential gain of an instrumentation amplifier. (06 Marks)
 - c. Explaining the operation briefly, design a non-saturating half wave precision rectifier to produce a 3 Volt peak output from an input of peak value 0.25 V, and frequency of 5 kHz. Use a bipolar op-amp with $\pm 15\text{V}$ power supply. (06 Marks)

PART – B

- 5
 - a. Explain the operation of a voltage follower peak detector circuit, discussing capacitor selection procedure. (08 Marks)
 - b. Design an RC-phase shift oscillator to generate sustained oscillations at a frequency of 1.5 kHz. Use a 741 op-amp and $\pm 12\text{V}$ power supply. (06 Marks)
 - c. Deriving an expression, discuss the fundamental log-amplifier circuit. (06 Marks)

- 6 a. Explain the operation of an inverting Schmitt trigger circuit with the help of waveforms and transfer characteristics. (08 Marks)
- b. Design an op-amp based monostable multivibrator to generate a pulse of width $PW = 2\text{ms}$. The trigger is a pulse of amplitude 3V and duration $150\ \mu\text{s}$. Use a bipolar op-amp and a supply of $\pm 12\text{V}$. (08 Marks)
- c. Design a first order high pass active filter for a cut-off frequency of $2\ \text{kHz}$. (04 Marks)
- 7 a. Briefly explain the operation of a series voltage regulator. (06 Marks)
- b. Design a voltage regulator circuit using LM723 to obtain $V_0 = 5\text{V}$, and $I_0 = 2\text{A}$. (06 Marks)
- c. Explain the basic principle of operation of switching regulators. Also list any four merits. (08 Marks)
- 8 a. Design an astable multivibrator using 555 timer to obtain a square wave of frequency $5\ \text{kHz}$ at 50% duty cycle. (06 Marks)
- b. Discuss the operating principle of PLLS and define the lock-in and capture ranges. (08 Marks)
- c. Explain the binary weighted technique of digital to analog conversion. What is its major disadvantage? (06 Marks)

* * * * *