

CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

15EE46

Fourth Semester B.E. Degree Examination, June/July 2017 Operational Amplifiers and Linear Integrated Circuits

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. Define and explain the following terms : input offset voltage, input offset current and input bias current. (06 Marks)
- b. For the noninverting amplifier configuration, obtain expressions for closed loop gain. A_f from basic concepts, show that difference input voltage is zero ideally and hence gain A_f from this concept and input resistance R_{if} with feedback. (10 Marks)

OR

- 2 a. For the noninverting ac amplifier using single supply $R_{ia} = 50\Omega = R_0$, $C_i = C_1 = 0.1\mu\text{F}$, $R_1 = R_2 = R_3 = 100\text{k}\Omega$, $R_F = 1\text{M}\Omega$, $V_{cc} = +15\text{V}$, gain $A_f = 11$, $u\text{GB} = 1\text{MHz}$. Calculate bandwidth of amplifier and maximum output voltage swing. Draw the circuit diagram. (06 Marks)
- b. What is an instrumentation amplifier? For instrumentation amplifier using transducer bridge obtain an expression for output voltage V_o in terms of change in resistance ΔR of the transducer. Draw the circuit diagram. (10 Marks)

Module-2

- 3 a. For the II order lowpass filter, show that the pass band voltage gain is equal to 1.586 and also obtain an expression for high cut off frequency f_H . Draw the circuit diagram. (10 Marks)
- b. Explain the working and design of opamp voltage follower regulator. (06 Marks)

OR

- 4 a. Design a wide band pass filter with $f_a = 200\text{Hz}$, $f_H = 1\text{KHz}$ and pass band gain = 4. Assume capacitor value for high pass section = $0.05\mu\text{F}$ and for low pass section = $0.01\mu\text{F}$. Also calculate the value of Q-factor for the filter and center frequency. Draw the circuit diagram. (06 Marks)
- b. An LM 317 regulator is to provide a 6V output from 15V supply. The load current is 200mA. Design the circuit, calculate the power dissipation. Draw the circuit diagram. Select $I_1 = 1\text{mA}$, $V_{ref} = 1.25\text{V}$. (05 Marks)
- c. Explain the working of notch filter. Draw its frequency response. State its common application. (05 Marks)

Module-3

- 5 a. Explain the working of Schmitt trigger in inverting mode. Draw its hysteresis curve. (06 Marks)
- b. Draw and explain triangular wave generator using square wave generator and integrator method. Draw the required waveforms. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any remaining or unutilized portion of evaluation, applied to evaluation, will not be taken as interpretation.

OR

- 6 a. Explain the circuit of noninverting comparator. Draw the different waveforms when V_{REF} is positive and negative. (06 Marks)
- b. Design a RC phase shift oscillator using opamp. Assume $C = 0.1\mu F$ frequency of oscillations = 200 Hz. Draw the circuit diagram. (06 Marks)
- c. Explain the working of voltage to converter with grounded load. (04 Marks)

Module-4

- 7 a. What is the major limitation of conventional rectifier? Explain working of precision positive and negative half wave rectifier using noninverting type. (10 Marks)
- b. Draw and explain working of dual slope ADC. (06 Marks)

OR

- 8 a. Explain the working of R – 2R ladder DAC. Assume that binary input is 001. (05 Marks)
- b. Draw and explain the circuit of peak detector. Draw the waveforms. (06 Marks)
- c. An 8-bit DAC has an output voltage range of 0 – 2.55 V. Define the resolution in at least 2 ways. (05 Marks)

Module-5

- 9 a. Explain operating principle of PLL. Hence define lock range, capture range, and pull in time. (08 Marks)
- b. An astable multivibrator is to be designed for getting rectangular waveform for $t_{ON} = 0.6ms$. Total time period = 1ms. Assume $C = 0.1\mu F$ Draw the circuit diagram. (08 Marks)

OR

- 10 a. Explain the function of various pins of IC 555 timer. (08 Marks)
- b. Explain PLL IC565 application as frequency multiplier and frequency synthesizer. (08 Marks)

* * * * *